

ECE 3300 – Lab 4 Report
Switch to 7 Segment Display
Team Name: Group V
Date: July 11, 2025

Group Members

Nathan Marlow, Khristian Chan

1. Objective

The objective of this lab was to implement a 7 segment display interface that utilized 16 switches as input, and a pair of 4 digit 7 segment displays (8 total). Every 4 switches (bits) will correspond to two 7 segment displays of the 8 (1 and 5, 2 and 6, 3 and 7, 4 and 8). Given a 7 segment driver module, we were tasked to create a top module and create a testbench.

2. Verilog Code

Top Module:

```
`timescale 1ns / 1ps
module seg7_top(
    input clk,
        input rst_n,
        input [15:0] SW,
        output wire [6:0] Cnode,
        output dp,
        output [7:0] AN,
        output wire[15:0] LED
    );

    wire [31:0] sw_in;
) assign sw_in = {SW, SW};
) assign LED = SW;

    seg7_driver driver(
        .clk(clk),
        .rst_n(rst_n),
        .SW(sw_in),
        .Cnode(Cnode),
        .dp(dp),
        .AN(AN)
    );
endmodule
```

7Seg Driver:

```
module seg7_driver (
    input clk,
    input rst_n,
    input [31:0] SW,
    output reg [6:0] Cnode,
    output dp,
    output [7:0] AN
);

// Display decimal point off
assign dp = 1'b1;

// Temporary counter for display multiplexing
reg [19:0] tmp;
reg [3:0] digit;

// 7-segment encoding
always @ (digit) begin
    case (digit)
        4'd0: Cnode = 7'b0000001;
        4'd1: Cnode = 7'b1001111;
        4'd2: Cnode = 7'b0010010;
        4'd3: Cnode = 7'b0000110;
        4'd4: Cnode = 7'b1001100;
        4'd5: Cnode = 7'b0100100;
        4'd6: Cnode = 7'b0100000;
        4'd7: Cnode = 7'b0001111;
        4'd8: Cnode = 7'b0000000;
        4'd9: Cnode = 7'b0001100;
        4'd10: Cnode = 7'b0001000;
        4'd11: Cnode = 7'b1100000;
        4'd12: Cnode = 7'b0110001;
        4'd13: Cnode = 7'b1000010;
        4'd14: Cnode = 7'b0110000;
        4'd15: Cnode = 7'b0111000;
        default: Cnode = 7'b1111111;
    endcase
end

// 20-bit counter for scanning speed
always @ (posedge clk or negedge rst_n) begin
    if (!rst_n)
        tmp <= 0;
    else
        tmp <= tmp + 1;
    end

    // Select digit based on counter bits
    wire [2:0] s = tmp[19:17];

    always @ (s, SW) begin
        case (s)
            3'd0: digit = SW[3:0];
            3'd1: digit = SW[7:4];
            3'd2: digit = SW[11:8];
            3'd3: digit = SW[15:12];
            3'd4: digit = SW[19:16];
            3'd5: digit = SW[23:20];
            3'd6: digit = SW[27:24];
            3'd7: digit = SW[31:28];
            default: digit = 4'b0000;
        endcase
    end

    // Select active display (AN low-active)
    reg [7:0] AN_tmp;

    always @ (s) begin
        case (s)
            3'd0: AN_tmp = 8'b11111110;
            3'd1: AN_tmp = 8'b11111101;
            3'd2: AN_tmp = 8'b11111011;
            3'd3: AN_tmp = 8'b11110111;
            3'd4: AN_tmp = 8'b11101111;
            3'd5: AN_tmp = 8'b11011111;
            3'd6: AN_tmp = 8'b10111111;
            3'd7: AN_tmp = 8'b01111111;
            default: AN_tmp = 8'b11111111;
        endcase
    end

    assign AN = AN_tmp;
endmodule
```

We map our top module switches twice to our 7 segment driver module. We do this so we can give a 32 bit input to our 7 segment driver. Additionally, we added the LED functionality.

3. Implementation Results

After synthesizing and simulating the design in Vivado, the following results were observed:


Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs	14	0	0	63400	0.02
LUT as Logic	14	0	0	63400	0.02
LUT as Memory	0	0	0	19000	0.00
Slice Registers	20	0	0	126800	0.02
Register as Flip Flop	20	0	0	126800	0.02
Register as Latch	0	0	0	126800	0.00
F7 Muxes	0	0	0	31700	0.00
F8 Muxes	0	0	0	15850	0.00

* Warning! LUT value is adjusted to account for LUT combining.

Total On-Chip Power (W)	0.125
Design Power Budget (W)	Unspecified*
Power Budget Margin (W)	NA
Dynamic (W)	0.028
Device Static (W)	0.097
Effective TJA (C/W)	4.6
Max Ambient (C)	84.4
Junction Temperature (C)	25.6
Confidence Level	Low
Setting File	---
Simulation Activity File	---
Design Nets Matched	NA

Simulation Results:

 Since the simulation would take a very long time to go through all possible values, we decided to just simulate one switch input. The testbench is able to validate our fpga code.



```

module seg7_tb(

);
  reg clk;
  reg rst_n;
  reg [15:0]SW;
  wire[6:0]Cnode;
  wire[7:0]AN;
  wire dp;

  sec7_top DUT(
    .clk(clk),
    .rst_n(rst_n),
    .SW(SW),
    .Cnode(Cnode),
    .AN(AN),
    .dp(dp)
  );
  always #5 clk = ~clk;
  initial begin

    clk = 0;
    rst_n = 0;
    SW = 16'b0;
    #10;
    SW = 16'b1111000111100011;

    #200000;
    $finish;
  end
endmodule

```

6. Demonstration Video

<https://youtu.be/tcdEHrQKYs8>

Contributions:

Khristian Chan- 50%: Testbench, Simulation, Report, Demo

Nathan Marlow- 50%: Implementation, XDC, Report