

**CALIFORNIA STATE POLYTECHNIC
UNIVERSITY, POMONA
COLLEGE OF ENGINEERING**

LAB 2

**4x16 Decoder Design on Nexys A7-100T FPGA
ECE 3300L Summer 2025**

Digital Circuit Design using Verilog

Professor Mohamed Aly

By: Clay Kim and Changwe Musonda

Objective

Design, simulate, and implement a 4-to-16 decoder with an enable input. Once enabled, exactly one of the 16 outputs goes HIGH based on the 4-bit input and when disabled, all outputs are LOW. This lab will allow us to practice structural coding, behavioral coding, writing a self-

checking testbench, reading Vivado's resource utilization, and documenting work clearly in a beginner friendly report.

Hardware Components

Nexys A7-100T Kit

- Inputs: SW3...SW0 → 4-bit input A[3:0]
- Enable: SW4 → enable signal E
- Outputs: LD0...LD15 → 16-bit output Y[15:0]

Verilog Code

Gate-Level Implementation

```
module decoder4x16_gate(  
    input wire [3:0] A,  
    input E,  
    output wire [15:0] Y  
);  
    assign Y[0] = E&~A[3]&~A[2]&~A[1]&~A[0];  
    assign Y[1] = E&~A[3]&~A[2]&~A[1]&A[0];  
    assign Y[2] = E&~A[3]&~A[2]&A[1]&~A[0];  
    assign Y[3] = E&~A[3]&~A[2]&A[1]&A[0];  
    assign Y[4] = E&~A[3]&A[2]&~A[1]&~A[0];  
    assign Y[5] = E&~A[3]&A[2]&~A[1]&A[0];  
    assign Y[6] = E&~A[3]&A[2]&A[1]&~A[0];  
    assign Y[7] = E&~A[3]&A[2]&A[1]&A[0];  
    assign Y[8] = E&A[3]&~A[2]&~A[1]&~A[0];  
    assign Y[9] = E&A[3]&~A[2]&~A[1]&A[0];  
    assign Y[10] = E&A[3]&~A[2]&A[1]&~A[0];  
    assign Y[11] = E&A[3]&~A[2]&A[1]&A[0];  
    assign Y[12] = E&A[3]&A[2]&~A[1]&~A[0];  
    assign Y[13] = E&A[3]&A[2]&~A[1]&A[0];  
    assign Y[14] = E&A[3]&A[2]&A[1]&~A[0];
```

```
    assign Y[15] = E&A[3]&A[2]&A[1]&A[0];  
endmodule
```

Behavioral Implementation

```
module decoder4x16_behavioral(  
    input wire[3:0] A,  
    input E,  
    output reg [15:0] Y  
);  
    always @(*) begin  
        if(E) begin //enable check  
            case (A)  
                4'h0: Y = 16'b0000_0000_0000_0001; //map first switch to first LED  
                4'h1: Y = 16'b0000_0000_0000_0010; //map second switch to second LED  
                4'h2: Y = 16'b0000_0000_0000_0100; //map third switch to third LED  
                4'h3: Y = 16'b0000_0000_0000_1000; //map fourth switch to fourth LED  
                4'h4: Y = 16'b0000_0000_0001_0000; //map fifth switch to fifth LED  
                4'h5: Y = 16'b0000_0000_0010_0000; //map sixth switch to sixth LED  
                4'h6: Y = 16'b0000_0000_0100_0000; //map seventh switch to seventh LED  
                4'h7: Y = 16'b0000_0000_1000_0000; //map eighth switch to eighth LED  
                4'h8: Y = 16'b0000_0001_0000_0000; //map ninth switch to ninth LED  
                4'h9: Y = 16'b0000_0010_0000_0000; //map tenth switch to tenth LED  
                4'hA: Y = 16'b0000_0100_0000_0000; //map eleventh switch to eleventh LED  
                4'hB: Y = 16'b0000_1000_0000_0000; //map twelvth switch to twelvth LED  
                4'hC: Y = 16'b0001_0000_0000_0000; //map thirteenth switch to thirteenth LED  
                4'hD: Y = 16'b0010_0000_0000_0000; //map fourteenth switch to fourteenth LED  
                4'hE: Y = 16'b0100_0000_0000_0000; //map fifteenth switch to fifteenth LED  
                4'hF: Y = 16'b1000_0000_0000_0000; //map sixteenth switch to sixteenth LED  
            endcase  
        end  
    else begin
```

```

        Y = 16'h0; //reset
    end

end

endmodule

```

Testbench

```

module tb_decoder4x16(
);
    reg [3:0] A;
    reg E;
    wire [15:0] Y;
    integer i;
    decoder4x16_gate TB_TESTING(.A(A), .Y(Y), .E(E));
    reg [15:0] expectedY [0:15];
    initial begin
        expectedY[0] = 16'h0001;
        expectedY[1] = 16'h0002;
        expectedY[2] = 16'h0004;
        expectedY[3] = 16'h0008;
        expectedY[4] = 16'h0010;
        expectedY[5] = 16'h0020;
        expectedY[6] = 16'h0040;
        expectedY[7] = 16'h0080;
        expectedY[8] = 16'h0100;
        expectedY[9] = 16'h0200;
        expectedY[10] = 16'h0400;
        expectedY[11] = 16'h0800;
        expectedY[12] = 16'h1000;
        expectedY[13] = 16'h2000;
        expectedY[14] = 16'h4000;
        expectedY[15] = 16'h8000;
    end
endmodule

```

```

E = 1'b1;

$display("ENABLE HIGH");

for(i=0; i<16; i=i+1) begin

    A=i;

    #20;

    $display("INPUT: %04b | EXPECTED: %04h | RESULT: %04h (%s)", A, expectedY[i], Y, (expectedY[i] ==
Y) ? "PASSED" : "FAILED");

end

E = 1'b0;

$display("ENABLE LOW");

for(i=0; i<16; i=i+1) begin

    A=i;

    #20;

    $display("INPUT: %04b | EXPECTED: %04h | RESULT: %04h (%s)", A, 16'h0000, Y, (16'h0000 == Y) ?
"PASSED" : "FAILED");

end

$finish;

end

endmodule

```

XDC Snippets

Clock signal

```

set_property -dict { PACKAGE_PIN E3  IOSTANDARD LVCMOS33 } [get_ports { CLK100MHZ }];
#IO_L12P_T1_MRCC_35 Sch=clk100mhz

create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {CLK100MHZ}];

```

##Switches

```

set_property -dict { PACKAGE_PIN J15  IOSTANDARD LVCMOS33 } [get_ports { A[0] }];
#IO_L24N_T3_RS0_15 Sch=sw[0]

set_property -dict { PACKAGE_PIN L16  IOSTANDARD LVCMOS33 } [get_ports { A[1] }];
#IO_L3N_T0_DQS_EMCCLK_14 Sch=sw[1]

```

```

set_property -dict { PACKAGE_PIN M13  IOSTANDARD LVCMOS33 } [get_ports { A[2] }];
#IO_L6N_T0_D08_VREF_14 Sch=sw[2]

set_property -dict { PACKAGE_PIN R15  IOSTANDARD LVCMOS33 } [get_ports { A[3] }];
#IO_L13N_T2_MRCC_14 Sch=sw[3]

set_property -dict { PACKAGE_PIN R17  IOSTANDARD LVCMOS33 } [get_ports { E }];
#IO_L12N_T1_MRCC_14 Sch=sw[4]

#set_property -dict { PACKAGE_PIN T18  IOSTANDARD LVCMOS33 } [get_ports { y[2] }];
#IO_L7N_T1_D10_14 Sch=sw[5]

#set_property -dict { PACKAGE_PIN U18  IOSTANDARD LVCMOS33 } [get_ports { y[1] }];
#IO_L17N_T2_A13_D29_14 Sch=sw[6]

#set_property -dict { PACKAGE_PIN R13  IOSTANDARD LVCMOS33 } [get_ports { y[0] }];
#IO_L5N_T0_D07_14 Sch=sw[7]

#set_property -dict { PACKAGE_PIN T8   IOSTANDARD LVCMOS18 } [get_ports { c_in }]; #IO_L24N_T3_34
Sch=sw[8]

#set_property -dict { PACKAGE_PIN U8   IOSTANDARD LVCMOS18 } [get_ports { SW[9] }]; #IO_25_34
Sch=sw[9]

#set_property -dict { PACKAGE_PIN R16  IOSTANDARD LVCMOS33 } [get_ports { SW[10] }];
#IO_L15P_T2_DQS_RDWR_B_14 Sch=sw[10]

#set_property -dict { PACKAGE_PIN T13  IOSTANDARD LVCMOS33 } [get_ports { SW[11] }];
#IO_L23P_T3_A03_D19_14 Sch=sw[11]

#set_property -dict { PACKAGE_PIN H6   IOSTANDARD LVCMOS33 } [get_ports { SW[12] }];
#IO_L24P_T3_35 Sch=sw[12]

#set_property -dict { PACKAGE_PIN U12  IOSTANDARD LVCMOS33 } [get_ports { SW[13] }];
#IO_L20P_T3_A08_D24_14 Sch=sw[13]

#set_property -dict { PACKAGE_PIN U11  IOSTANDARD LVCMOS33 } [get_ports { SW[14] }];
#IO_L19N_T3_A09_D25_VREF_14 Sch=sw[14]

#set_property -dict { PACKAGE_PIN V10  IOSTANDARD LVCMOS33 } [get_ports { SW[15] }];
#IO_L21P_T3_DQS_14 Sch=sw[15]

```

LEDs

```

set_property -dict { PACKAGE_PIN H17  IOSTANDARD LVCMOS33 } [get_ports { Y[0] }];
#IO_L18P_T2_A24_15 Sch=led[0]

set_property -dict { PACKAGE_PIN K15  IOSTANDARD LVCMOS33 } [get_ports { Y[1] }];
#IO_L24P_T3_RS1_15 Sch=led[1]

set_property -dict { PACKAGE_PIN J13  IOSTANDARD LVCMOS33 } [get_ports { Y[2] }];
#IO_L17N_T2_A25_15 Sch=led[2]

```

```

set_property -dict { PACKAGE_PIN N14  IOSTANDARD LVCMOS33 } [get_ports { Y[3] }];
#IO_L8P_T1_D11_14 Sch=led[3]

set_property -dict { PACKAGE_PIN R18  IOSTANDARD LVCMOS33 } [get_ports { Y[4] }];
#IO_L7P_T1_D09_14 Sch=led[4]

set_property -dict { PACKAGE_PIN V17  IOSTANDARD LVCMOS33 } [get_ports { Y[5] }];
#IO_L18N_T2_A11_D27_14 Sch=led[5]

set_property -dict { PACKAGE_PIN U17  IOSTANDARD LVCMOS33 } [get_ports { Y[6] }];
#IO_L17P_T2_A14_D30_14 Sch=led[6]

set_property -dict { PACKAGE_PIN U16  IOSTANDARD LVCMOS33 } [get_ports { Y[7] }];
#IO_L18P_T2_A12_D28_14 Sch=led[7]

set_property -dict { PACKAGE_PIN V16  IOSTANDARD LVCMOS33 } [get_ports { Y[8] }];
#IO_L16N_T2_A15_D31_14 Sch=led[8]

set_property -dict { PACKAGE_PIN T15  IOSTANDARD LVCMOS33 } [get_ports { Y[9] }];
#IO_L14N_T2_SRCC_14 Sch=led[9]

set_property -dict { PACKAGE_PIN U14  IOSTANDARD LVCMOS33 } [get_ports { Y[10] }];
#IO_L22P_T3_A05_D21_14 Sch=led[10]

set_property -dict { PACKAGE_PIN T16  IOSTANDARD LVCMOS33 } [get_ports { Y[11] }];
#IO_L15N_T2_DQS_DY_CSO_B_14 Sch=led[11]

set_property -dict { PACKAGE_PIN V15  IOSTANDARD LVCMOS33 } [get_ports { Y[12] }];
#IO_L16P_T2_CSI_B_14 Sch=led[12]

set_property -dict { PACKAGE_PIN V14  IOSTANDARD LVCMOS33 } [get_ports { Y[13] }];
#IO_L22N_T3_A04_D20_14 Sch=led[13]


set_property -dict { PACKAGE_PIN V12  IOSTANDARD LVCMOS33 } [get_ports { Y[14] }];
#IO_L20N_T3_A07_D23_14 Sch=led[14]

set_property -dict { PACKAGE_PIN V11  IOSTANDARD LVCMOS33 } [get_ports { Y[15] }];
#IO_L21N_T3_DQS_A06_D22_14 Sch=led[15]

```

Synthesis and Implementation

Screenshot:

 

Group Video

<https://youtu.be/2DiERelA0Ic>

Reflections

This lab provided an effective hands-on experience in learning Verilog coding for implementation of a 4-to-16 decoder onto the Nexys A7 Board. It also solidified the difference between gate level versus behavioral coding and their associated advantages and disadvantages for hardware implementation. Being able to create a testbench for my decoder put me in the mindset of verification and validation when dealing with FPGAs. Experiencing timing reports and resource utilization review via the Vivado implementation of my projects exposed me to the necessity of proper efficiency and optimization awareness within a design. This all adds to my future efforts in the field with digital logic design and FPGA usage for future complex embedded systems.