

ECE 3300L.01 - Lab 5

BCD Up/Down Counter on  
7-Segment Display

Professor Mohamed Aly  
Group Q: Kevin Tang(015429622) &  
Jared Mocling(015215057)

July 21th, 2025

**Objective:**

- Design a two-digit BCD up/down counter in Verilog-HDL.
- Implement a clock-divider with a 32-bit counter + 32×1 Mux and 5 SW speed select.
- Control counting direction via BTN1 (Up/Down) and reset via BTN0.
- Drive a dual-digit 7-segment display using multiplexing.
- Deploy on Nexys A7: simulate, synthesize, program, and test.

**Design:****Clock divider:**

```
module clock_divider(  
    input clk,  
    output reg [31:0] cnt = 0  
);  
    always @(posedge clk)  
        cnt <= cnt + 1;  
endmodule
```

**Mux32x1:**

```
module mux32x1(  
    input [31:0] cnt,  
    input [4:0] sel,  
    output clk_out  
);  
    assign clk_out = cnt[sel];  
endmodule
```

**BCD Up/Down Counter:**

```

module bcd_up_down_counter(
    input clk_out,
    input rst_n,
    input dir, // 1 for up, 0 for down
    output reg [3:0] digit1, // tens
    output reg [3:0] digit0 // units
);
    always @(posedge clk_out or negedge rst_n) begin
        if (!rst_n) begin
            digit0 <= 0;
            digit1 <= 0;
        end else if (dir) begin
            // Count Up
            if (digit0 == 9) begin
                digit0 <= 0;
                if (digit1 == 9)
                    digit1 <= 0;
                else
                    digit1 <= digit1 + 1;
            end else begin
                digit0 <= digit0 + 1;
            end
        end else begin
            // Count Down
            if (digit0 == 0) begin
                digit0 <= 9;
                if (digit1 == 0)
                    digit1 <= 9;
                else
                    digit1 <= digit1 - 1;
            end else begin
                digit0 <= digit0 - 1;
            end
        end
    end
end
endmodule

```

### **7 Segment Display:**

```
module seg7_scan(
    input clk,
    input [3:0] digit1,
    input [3:0] digit0,
    output reg [7:0] AN,
    output reg [6:0] SEG
);

    reg [15:0] refresh_counter = 0;
    wire sel;
    reg [3:0] current_digit;

    always @(posedge clk) begin
        refresh_counter <= refresh_counter + 1;
    end

    assign sel = refresh_counter[15];

    always @(*) begin
        case (sel)
            1'b0: begin
                AN <= 8'b11111110; // Activate digit0
                SEG <= seg_decoder(digit0);
            end
            1'b1: begin
                AN <= 8'b11111101; // Activate digit1
                SEG <= seg_decoder(digit1);
            end
        endcase
    end

    function [6:0] seg_decoder;
        input [3:0] num;
        case (num)
            4'd0: seg_decoder=7'b0000001;
            4'd1: seg_decoder=7'b1001111;
            4'd2: seg_decoder=7'b0010010;
            4'd3: seg_decoder=7'b0000110;
            4'd4: seg_decoder=7'b1001100;
```

```

        4'd5: seg_decoder=7'b0100100;
        4'd6: seg_decoder=7'b0100000;
        4'd7: seg_decoder=7'b0001111;
        4'd8: seg_decoder=7'b0000000;
        4'd9: seg_decoder=7'b0001100;
        default: seg_decoder = 7'b1111111; // off
    endcase
endfunction
endmodule

```

### **Top Module:**

```

module top_lab5(
    input clk,
    input [4:0] SW,
    input [1:0] BTN,
    output [7:0] AN,
    output [6:0] SEG,
    output [12:0] LED
);

    wire [31:0] cnt;
    wire clk_out;
    wire [3:0] digit0, digit1;

    assign rst_n = ~BTN[0];

    //clock divider
    clock_divider cd (
        .clk(clk),
        .cnt(cnt)
    );

    // Mux
    mux32x1 mux (
        .cnt(cnt),
        .sel(SW),
        .clk_out(clk_out)
    );

    // BCD counter

```

```
bcd_up_down_counter bcd (  
    .clk_out(clk_out),  
    .rst_n(rst_n),  
    .dir(BTN[1]),  
    .digit0(digit0),  
    .digit1(digit1)  
);
```


```
// 7-segment scan  
seg7_scan scan (  
    .clk(clk),  
    .digit0(digit0),  
    .digit1(digit1),  
    .AN(AN),  
    .SEG(SEG)  
);
```

```
assign LED[4:0] = SW;  
assign LED[8:5] = digit0;  
assign LED[12:9] = digit1;
```


```
endmodule
```

### **Testbench Waveform:**

Clock Divider

 


Mux 32x1

 





## BCD Counter

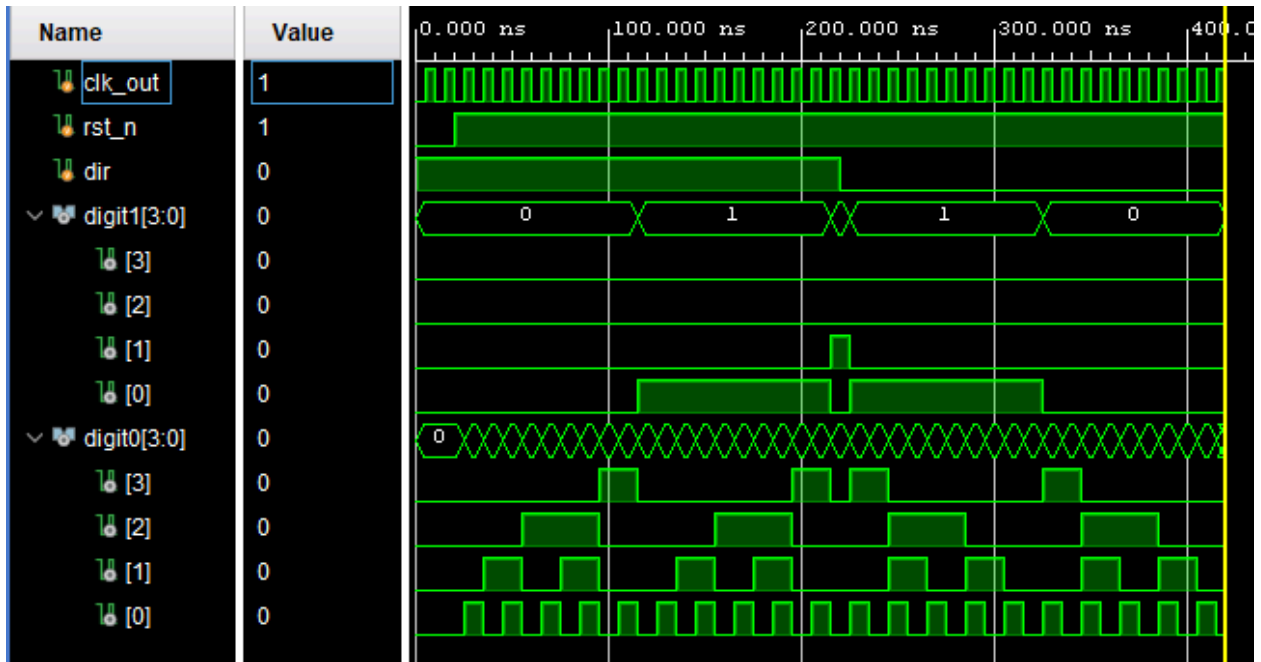

## 7 Segment Display

 


Top module

 

## Utilization/Implementation:

Resource	Utilization	Available	Utilization %
LUT	28	63400	0.04
FF	56	126800	0.04
IO	36	210	17.14

 


## Power

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 0.127 W  
**Design Power Budget:** Not Specified  
**Process:** typical  
**Power Budget Margin:** N/A  
**Junction Temperature:** 25.6°C  
Thermal Margin: 59.4°C (12.9 W)  
Ambient Temperature: 25.0 °C  
Effective  $\theta_{JA}$ : 4.6°C/W  
Power supplied to off-chip devices: 0 W  
Confidence level: Low  
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

### On-Chip Power

 

## **Time Summary:**

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 6.974 ns	Worst Hold Slack (WHS): 0.324 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 48	Total Number of Endpoints: 48	Total Number of Endpoints: 49

**All user specified timing constraints are met.**

## **Contributions:**

Jared Mocling (50%) - board demo, compiled code, report.

Kevin Tang (50%)- compiled code, simulation code, Synthesis reports, report