

**ECE 3300L**

**Lab Report #6**

**Group E**

Paul Kim (ID: 015236949)

Winson Zhu (ID: 016416790)


July 28, 2025

## Design:


- a) clock\_divider.v - 100 MHz clock is divided based on SW[4:0]. 32-bit counter, output bit is selected by a  $32 \times 1$  MUX.
- b) bcd\_counter.v - Counts 0–9 based on direction input (SW7/SW8). Resets on BTN0
- c) alu.v - Accepts two 4-bit BCD values. Performs add or subtract based on SW[6:5]. Output is 8-bit result
- d) control\_decoder.v - Takes {SW8, SW7, SW6, SW5}. Outputs as 4-bit control nibble for display
- e) seg7\_scan.v - 3-digit multiplexed display: AN0: result[3:0], AN1: result[7:4], AN2: control nibble
- f) top\_lab6.v - Instantiates all other modules

## Simulation:


### clock\_divider\_tb:

 


mux32x1\_tb:

 


bcd\_counter\_tb:

 


alu\_tb:

 

control\_decoder\_tb:

 

 seg7\_scan\_tb: Verify multiplexing and segment decoding.



## Implementation:

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	37	0	0	63400	0.06
LUT as Logic	37	0	0	63400	0.06
LUT as Memory	0	0	0	19000	0.00
Slice Registers	58	0	0	126800	0.05
Register as Flip Flop	58	0	0	126800	0.05
Register as Latch	0	0	0	126800	0.00
F7 Muxes	4	0	0	31700	0.01
F8 Muxes	0	0	0	15850	0.00

**Contributions:**

Paul Kim - Source Codes, Testbench, Simulation - 50% contribution

Winson Zhu - Source Codes, Implementation, Hardware Demo - 50% contribution