

ECE 3300 – Lab 5 Report
BCD Up/Down Counter on 7-Segment Display
Team Name: Group V
Date: July 21, 2025

Group Members

Nathan Marlow, Khristian Chan

1. Objective

The objective of this lab was to design and implement a two-digit BCD up/down counter on the Nexys A7 FPGA using Verilog. The system features speed control via SW[4:0], direction control using BTN1, and reset with BTN0. A 32-bit counter and 32×1 Mux were used for clock division, and the output is displayed on a dual-digit 7-segment display with multiplexing, while also being mirrored on LED[7:0] for debugging.

2. Verilog Code

Top Module:

```
module top_lab5(
    input clk,           // 100MHz
    input rst_n,         // BTN0 (active low)
    input dir,           // BTN1 (1=up, 0=down)
    input [4:0] sw,       // Speed select
    output [7:0] an,      // 7-seg anodes
    output [6:0] seg,     // 7-seg segments
    output [7:0] led      // LED output
);
    wire [31:0] cnt;
    wire clk_div;
    wire [4:0] notsw = ~sw;

    // Clock Divider
    clock_divider u_div(.clk(clk), .rst_n(rst_n), .cnt(cnt));

    // MUX for speed select
    mux32x1 u_mux(.cnt(cnt), .sel(notsw), .clk_out(clk_div));

    // BCD Up/Down Counter
    wire [3:0] units, tens;
    bcd_up_down_counter u_bcd(.clk(clk_div), .rst_n(rst_n), .dir(dir),
                              .units(units), .tens(tens), .leds(led));

    // 7-segment scan
    seg7_scan u_seg(.clk(cnt[15]), .rst_n(rst_n), .units(units), .tens(tens),
                    .an(an), .seg(seg));
endmodule
```

Our top module takes all of the other modules and instantiates them to work all at the same time.

7Seg Driver:

```
module seg7_scan(  
    input clk,  
    input rst_n,  
    input [3:0] units,  
    input [3:0] tens,  
    output reg [7:0] an,  
    output reg [6:0] seg  
);  
    reg select;  
  
    always @(posedge clk or negedge rst_n) begin  
        if (!rst_n)  
            select <= 0;  
        else  
            select <= ~select; // Toggle between digits  
        end  
  
    always @(*) begin  
        case (select)  
            0: begin  
                an = 8'b11111110; // enable units digit (AN0 active low)  
                seg = bcd_to_7seg(units);  
            end  
            1: begin  
                an = 8'b11111101; // enable tens digit (AN1 active low)  
                seg = bcd_to_7seg(tens);  
            end  
            default: begin  
                an = 8'b11111111;  
                //seg = bcd_to_7seg(7'd1111111);  
            end  
        endcase  
    end  
  
    function [6:0] bcd_to_7seg(input [3:0] bcd);  
        case (bcd)  
            4'd0: bcd_to_7seg = 7'b1000000;  
            4'd1: bcd_to_7seg = 7'b1111001;  
            4'd2: bcd_to_7seg = 7'b0100100;  
            4'd3: bcd_to_7seg = 7'b0110000;  
            4'd4: bcd_to_7seg = 7'b0011001;  
            4'd5: bcd_to_7seg = 7'b0010010;  
            4'd6: bcd_to_7seg = 7'b0000010;  
            4'd7: bcd_to_7seg = 7'b1111000;  
            4'd8: bcd_to_7seg = 7'b0000000;  
            4'd9: bcd_to_7seg = 7'b0010000;  
            default: bcd_to_7seg = 7'b1111111; // blank  
        endcase  
    endfunction  
endmodule
```

Similar to our previous lab, we are driving a seven segment display. This time, we only drive two of the anodes, so this simplifies the process a lot, and makes poll rate quicker for the driver. In

our code, we have an 8 bit wide anode, instead of 2, so that we can set the other 6 anodes to high, turning them off.

Clock Divider:

```
module clock_divider(  
    input clk,  
    input rst_n,  
    output reg [31:0] cnt  
);  
    //count is 0 if reset, else increment every clock cycle  
    always @(posedge clk or negedge rst_n) begin  
        if (!rst_n)  
            cnt <= 0;  
        else  
            cnt <= cnt + 1;  
        end  
    endmodule
```

If reset is low, our counter is zero, if its high, it counts as normal

32x1 Mux:

```
module mux32x1(  
    input [31:0] cnt,  
    input [4:0] sel,  
    output clk_out  
);  
    //mux assign clk_out to "array" index sel  
    assign clk_out = cnt[sel];  
endmodule
```

This is a normal 32x1 multiplexer with a 5 bit select. As done before, we can use an assign statement.

BCD UP/Down Counter:

```
module bcd_up_down_counter(  
    input clk,  
    input rst_n,  
    input dir, // 1 = up, 0 = down  
    output reg [3:0] units,  
    output reg [3:0] tens,  
    output reg [7:0] leds  
);  
    reg [3:0] prev_units;  
  
    always @(posedge clk or negedge rst_n) begin  
        //if reset, set 7seg's to 0, if not reset, set register prev_units =units at clock cycle  
        if (!rst_n) begin  
            units <= 0;  
            tens <= 0;  
        end else begin  
            prev_units <= units;  
  
            if (dir) begin // Count up  
                //reset to 0 if 9 for both units and tens.  
                if (units == 9) begin  
                    units <= 0;  
                    if (tens == 9)  
                        tens <= 0;  
                else  
                    //count normally  
                    tens <= tens + 1;  
                end else begin  
                    units <= units + 1;  
                end  
            end else begin // Count down  
                if (units == 0) begin  
                    units <= 9;  
                    if (tens == 0)  
                        tens <= 9;  
                else  
                    tens <= tens - 1;  
                end else begin  
                    units <= units - 1;  
                end  
            end  
        end  
    end  
  
    always @(*) begin  
        //set led's to our bcd numbers  
        leds[3:0] = units;  
        leds[7:4] = tens;  
    end  
endmodule
```

Lastly, this module essentially is our counter. It naturally counts down due to our dir naturally being low. When high, it will count up, with rollover when either tens or units go to 9. When dir is low, it will roll over the other direction, from 0 back to 9.

3. Implementation Results

After synthesizing and simulating the design in Vivado, the following results were observed:

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs	28	0	0	63400	0.04
LUT as Logic	28	0	0	63400	0.04
LUT as Memory	0	0	0	19000	0.00
Slice Registers	41	0	0	126800	0.03
Register as Flip Flop	41	0	0	126800	0.03
Register as Latch	0	0	0	126800	0.00
F7 Muxes	4	0	0	31700	0.01
F8 Muxes	0	0	0	15850	0.00

* Warning! LUT value is adjusted to account for LUT combining.

Total On-Chip Power (W)	0.142
Design Power Budget (W)	Unspecified*
Power Budget Margin (W)	NA
Dynamic (W)	0.045
Device Static (W)	0.097
Effective TJA (C/W)	4.6
Max Ambient (C)	84.4
Junction Temperature (C)	25.6
Confidence Level	Low
Setting File	---
Simulation Activity File	---
Design Nets Matched	NA

* Specify Design Power Budget using, set_operating_conditions -design_power_budget <value in Watts>

1.1 On-Chip Components

On-Chip	Power (W)	Used	Available	Utilization (%)
Clocks	<0.001	3	---	---
Slice Logic	<0.001	93	---	---
LUT as Logic	<0.001	28	63400	0.04
Register	<0.001	41	126800	0.03
CARRY4	<0.001	8	15850	0.05
F7/F8 Muxes	<0.001	4	63400	<0.01
Others	0.000	5	---	---
Signals	<0.001	77	---	---
I/O	0.043	31	210	14.76
Static Power	0.097			
Total	0.142			

Simulation Results:


Since the simulation would take a very long time to go through all possible values, we decided to just simulate one switch input. The testbench is able to validate our fpga code.

mux32x1_tb.v




We see that our chosen input waveform (alternating 1's and 0's 11001100...) is reflected in our output waveform

clock_divider_tb.v

 


We see once our reset goes high, we start counting up, and once reset is pressed again our output goes low again.

seg7_scan_tb.v

 


We see that our AN value for our unwanted bits is always high signifying that they are off. We see that our 7segment displays go through all values 0-9 on both displays.

bcd_updown_tb.v

 

We count down from 99, and we see that once dir goes high we count up.

top_lab5_tb.v

 

We see that we can count both down and up in this testbench, along with our reset working as intended.

6. Demonstration Video

https://youtu.be/_39TesYDkGE

Contributions:

Khristian Chan- 50%: Testbench, Simulation, Debugging, Report, Demo

Nathan Marlow- 50%: Implementation, Code, XDC, Report