

ECE3300L Lab 2

4x16 Decoder

Group X

Czyrone Agbayani (BID: 014766336)

Caleb Jala-Guinto (BID: 015446587)

Objective:

We will design, simulate and implement a 4-to-16 decoder with an enable input (SW4). When enabled, exactly one of the 16 outputs goes HIGH based on the 4-bit input. On the other hand, if disabled, all outputs are LOW.

Gate-Level Implementation:


3-to-8 Decoder

```
23 module decoder3to8 (  
24     input [2:0] SW,  
25     input en,  
26     output [7:0] LED  
27 );  
28     assign LED[0] = en & ~SW[2] & ~SW[1] & ~SW[0]; //3x8 truth table  
29     assign LED[1] = en & ~SW[2] & ~SW[1] & SW[0];  
30     assign LED[2] = en & ~SW[2] & SW[1] & ~SW[0];  
31     assign LED[3] = en & ~SW[2] & SW[1] & SW[0];  
32     assign LED[4] = en & SW[2] & ~SW[1] & ~SW[0];  
33     assign LED[5] = en & SW[2] & ~SW[1] & SW[0];  
34     assign LED[6] = en & SW[2] & SW[1] & ~SW[0];  
35     assign LED[7] = en & SW[2] & SW[1] & SW[0];  
36  
37 endmodule
```

4-to-16 Decoder using two 3-to-8 Decoders

```
23 module decoder4to16(  
24     input [3:0] SW,  
25     input en,  
26     output [15:0] LED  
27 );  
28     wire [7:0] low_out;  
29     wire [7:0] high_out;  
30  
31     wire en_low = en & ~SW[3];  
32     wire en_high = en & SW[3];  
33  
34     decoder3to8 lower_decoder (  
35         .SW(SW[2:0]),  
36         .en(en_low),  
37         .LED(low_out)  
38     );  
39  
40     decoder3to8 upper_decoder (  
41         .SW(SW[2:0]),  
42         .en(en_high),  
43         .LED(high_out)  
44     );  
45  
46     assign LED[7:0] = low_out;  
47     assign LED[15:8] = high_out;  
48  
49 endmodule
```

Schematic:

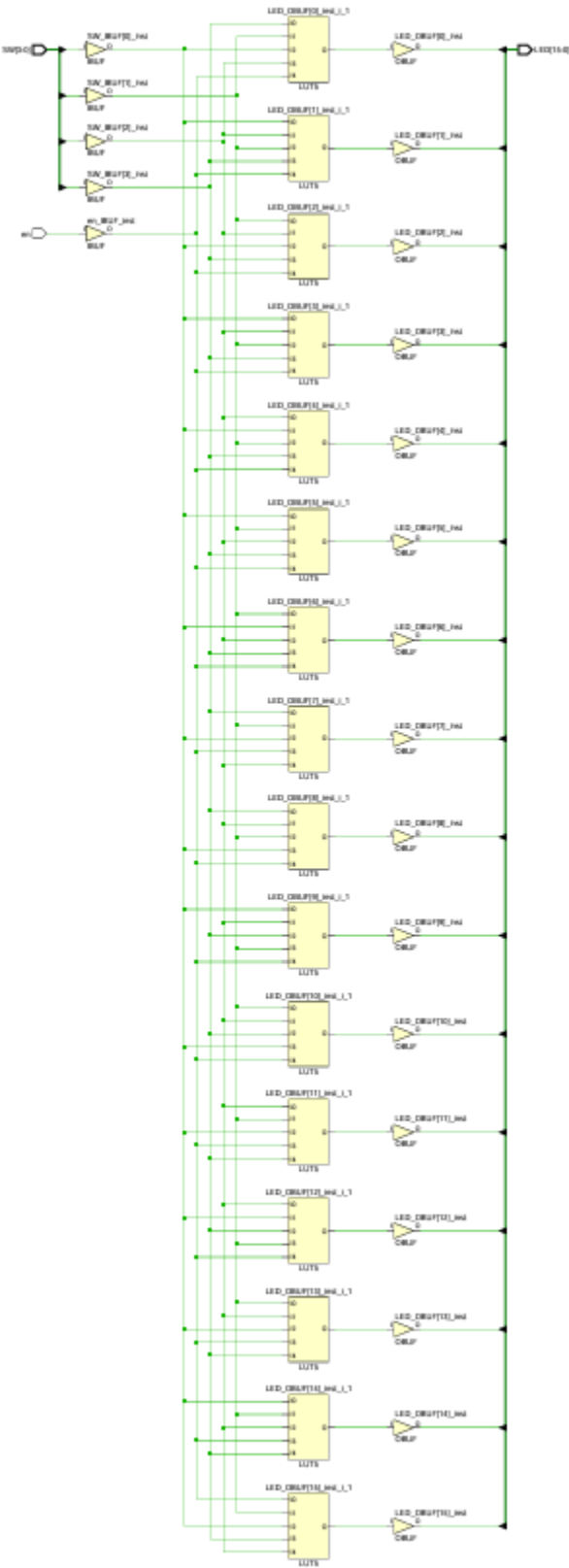

Behavioral Implementation:

4-to-16 Decoder Behave:

```
23 module decoder4to16_behave (
24     input [3:0] SW,
25     input en,
26     output reg [15:0] LED
27 );
28
29 always @(*) begin
30     LED = 16'b0;
31     if (en) begin
32         case (SW)
33             4'b0000: LED = 16'b0000_0000_0000_0001;
34             4'b0001: LED = 16'b0000_0000_0000_0010;
35             4'b0010: LED = 16'b0000_0000_0000_0100;
36             4'b0011: LED = 16'b0000_0000_0000_1000;
37             4'b0100: LED = 16'b0000_0000_0001_0000;
38             4'b0101: LED = 16'b0000_0000_0010_0000;
39             4'b0110: LED = 16'b0000_0000_0100_0000;
40             4'b0111: LED = 16'b0000_0000_1000_0000;
41             4'b1000: LED = 16'b0000_0001_0000_0000;
42             4'b1001: LED = 16'b0000_0010_0000_0000;
43             4'b1010: LED = 16'b0000_0100_0000_0000;
44             4'b1011: LED = 16'b0000_1000_0000_0000;
45             4'b1100: LED = 16'b0001_0000_0000_0000;
46             4'b1101: LED = 16'b0010_0000_0000_0000;
47             4'b1110: LED = 16'b0100_0000_0000_0000;
48             4'b1111: LED = 16'b1000_0000_0000_0000;
49         endcase
50     end
51 end
52
53 endmodule
```


Constraint file:

```
11 ##Switches
12
13 set_property -dict { PACKAGE_PIN J15 IOSTANDARD LVCMOS33 } [get_ports { SW[0] }]; #IO L24N T3 RS0_15 Sch=sw[0]
14 set_property -dict { PACKAGE_PIN L16 IOSTANDARD LVCMOS33 } [get_ports { SW[1] }]; #IO L3N T0 DQS_EMCCLK_14 Sch=sw[1]
15 set_property -dict { PACKAGE_PIN M13 IOSTANDARD LVCMOS33 } [get_ports { SW[2] }]; #IO L6N T0_D08_VREF_14 Sch=sw[2]
16 set_property -dict { PACKAGE_PIN R15 IOSTANDARD LVCMOS33 } [get_ports { SW[3] }]; #IO L13N T2_MRCC_14 Sch=sw[3]
17 set_property -dict { PACKAGE_PIN R17 IOSTANDARD LVCMOS33 } [get_ports { en }]; #IO L12N T1 MRCC_14 Sch=sw[4]
```

And we had all LEDs turned on

```
33 set_property -dict { PACKAGE_PIN H17 IOSTANDARD LVCMOS33 } [get_ports { LED[0] }]; #IO L18P T2_A24_15 Sch=led[0]
34 set_property -dict { PACKAGE_PIN K15 IOSTANDARD LVCMOS33 } [get_ports { LED[1] }]; #IO L24P T3_RS1_15 Sch=led[1]
35 set_property -dict { PACKAGE_PIN J13 IOSTANDARD LVCMOS33 } [get_ports { LED[2] }]; #IO L17N T2_A25_15 Sch=led[2]
36 set_property -dict { PACKAGE_PIN N14 IOSTANDARD LVCMOS33 } [get_ports { LED[3] }]; #IO L8P T1_D11_14 Sch=led[3]
37 set_property -dict { PACKAGE_PIN R18 IOSTANDARD LVCMOS33 } [get_ports { LED[4] }]; #IO L7P T1_D09_14 Sch=led[4]
38 set_property -dict { PACKAGE_PIN V17 IOSTANDARD LVCMOS33 } [get_ports { LED[5] }]; #IO L18N T2_A11_D27_14 Sch=led[5]
39 set_property -dict { PACKAGE_PIN U17 IOSTANDARD LVCMOS33 } [get_ports { LED[6] }]; #IO L17P T2_A14_D30_14 Sch=led[6]
40 set_property -dict { PACKAGE_PIN U16 IOSTANDARD LVCMOS33 } [get_ports { LED[7] }]; #IO L18P T2_A12_D28_14 Sch=led[7]
41 set_property -dict { PACKAGE_PIN V16 IOSTANDARD LVCMOS33 } [get_ports { LED[8] }]; #IO L16N T2_A15_D31_14 Sch=led[8]
42 set_property -dict { PACKAGE_PIN T15 IOSTANDARD LVCMOS33 } [get_ports { LED[9] }]; #IO L14N T2_SRCC_14 Sch=led[9]
43 set_property -dict { PACKAGE_PIN U14 IOSTANDARD LVCMOS33 } [get_ports { LED[10] }]; #IO L22P T3_A05_D21_14 Sch=led[10]
44 set_property -dict { PACKAGE_PIN T16 IOSTANDARD LVCMOS33 } [get_ports { LED[11] }]; #IO L15N T2_DQS_DOUT_CSO_B_14 Sch=led[11]
45 set_property -dict { PACKAGE_PIN V15 IOSTANDARD LVCMOS33 } [get_ports { LED[12] }]; #IO L16P T2_CSI_B_14 Sch=led[12]
46 set_property -dict { PACKAGE_PIN V14 IOSTANDARD LVCMOS33 } [get_ports { LED[13] }]; #IO L22N T3_A04_D20_14 Sch=led[13]
47 set_property -dict { PACKAGE_PIN V12 IOSTANDARD LVCMOS33 } [get_ports { LED[14] }]; #IO L20N T3_A07_D23_14 Sch=led[14]
48 set_property -dict { PACKAGE_PIN V11 IOSTANDARD LVCMOS33 } [get_ports { LED[15] }]; #IO L21N T3_DQS_A06_D22_14 Sch=led[15]
```

Test bench:

 

Video Link:

<https://youtu.be/DPPkRD5WqPA>

Contributions:

Czyrone (50%) - 3 to 8 decoder code, 4 to 16 behavior code, test bench.

Caleb (50%) - Board Demo, 4 to 16 decoder using upper and lower 3 to 8 decoders.

Both worked on the lab report together.

Reflections:

In this lab, a 4-to-16 decoder with an enable input was designed and implemented using the Nexys A7-100T FPGA board. The decoder was created using two different methods, which were a gate-level approach with basic logic gates and a behavioral approach using a case statement. Both versions were tested to make sure they worked correctly. To help build the decoder more efficiently, two 3-to-8 decoder modules were used. The most significant input bit (A3) was used to choose which 3-to-8 block to activate. This made the design easier to manage and understand. A self-checking testbench was created to automatically verify that only one output was high when the decoder was enabled, and that all outputs stayed low when disabled. After testing in simulation, the design was programmed onto the FPGA. Flipping the switches on the board correctly lit up one LED at a time, showing that the decoder worked as expected. This lab helped build a stronger understanding of Verilog coding, testbench creation, and how to bring a digital design from simulation to working hardware.