



Cal Poly
Pomona

College of Engineering

California Polytechnic State University, Pomona

ECE3300L

Experiment #6

GROUP K

Hoang, Dalton - 016062800

Siu, Andy - 016205137

July 28th, 2025

Introduction:

In Lab 6, we designed and implemented a digital system on the Nexys A7-100T FPGA that integrates two BCD counters, an arithmetic logic unit (ALU), and a 7-segment display controller. The primary objective was to design an interactive counting system that allowed each counter to count up or down based on switch inputs. The outputs of these counters were then processed by a simple ALU capable of performing addition or subtraction. The final result was displayed on a 3-digit 7-segment display. The first two digits showed the ALU's result, while the third digit reflected the switch-controlled operational settings. Additional features included clock speed control using switches SW[4] through SW[0], direction control for each counter using switches SW[8] and SW[7], ALU operation selection using switches SW[5] and SW[6], and system-wide reset using BTN0 as the reset. LEDs were also used to monitor the raw binary output of the counters as a form of debugging. Overall, this lab provided hands-on experience in Verilog design and the integration of instantiated modules.

Design:

alu.v: implements an arithmetic logic unit that takes two 4-bit BCD inputs and a 2-bit control signal to perform either addition or subtraction

```
23 module alu(  
24     input [3:0] A,  
25     input [3:0] B,  
26     input [1:0] ctrl,  
27  
28     output reg [7:0] result  
29 );  
30  
31 always @(*) begin  
32     case (ctrl)  
33         2'b00: result = A + B;    // Add  
34         2'b01: result = A - B;    // Subtract  
35         default: result = 8'b00000000; // Default  
36     endcase  
37 end  
38  
39 endmodule
```

bcd_counter.v: defines a BCD counter that increments or decrements a 4-bit value between 0 and 9 based on a direction control signal, and resets to 0 when the active-low reset is triggered.

```

22 module bcd_counter(
23     input wire bit_direct,          // up = 1 and 0 = down
24     input wire clk,
25     input wire rst_n,
26
27     output reg [3:0] value
28 );
29
30
31 always @(posedge clk or negedge rst_n) begin
32     if (!rst_n)
33         value <= 0;
34     else if (bit_direct)
35         value <= (value == 9) ? 0 : value + 1;
36     else
37         value <= (value == 0) ? 9 : value - 1;
38     end
39 endmodule

```

clk_divider.v: implements a clock divider that uses a 32-bit counter to generate a slower clock signal by selecting the MSB of the counter based on a 5-bit input select, with an active-low reset to zero the counter.

```

25 module clk_divider(
26     input wire clk,
27     input wire [4:0] sel,
28     input wire reset_n,
29
30     output wire clk_div,
31     output reg [31:0] counter
32 );
33
34 // Count up on every clock edge, reset on active-low reset
35 always @(posedge clk or negedge reset_n) begin
36     if (!reset_n)
37         counter <= 32'b0;
38     else
39         counter <= counter + 1;
40     end
41
42 assign clk_div = counter[sel];
43
44 endmodule

```

control_decoder.v: passes a 4-bit ctrl_in input directly to a 4-bit ctrl_out output, allowing switch settings to be displayed on a 7-segment display.

```

22 module control_decoder(
23     input wire [3:0] ctrl_input,    // SW8, SW7, SW6, SW5
24
25     output wire [3:0] ctrl_output    // Goes to 7-segment display
26 );
27
28     // Pass input directly to output
29     assign ctrl_output = ctrl_input;
30
31 endmodule
32

```

seg7_scan.v: implements a 3-digit 7-segment display scan that cycles through and displays the lower digit, upper digit, and control nibble.

```

22 module seg7_scan(
23     input wire [3:0] lower_digit,
24     input wire [3:0] upper_digit,
25     input wire clk,
26     input wire rst_n,
27     input wire [3:0] ctrl_nibble,
28
29     output reg [2:0] AN,
30     output reg [6:0] SEG
31 );
32     wire [3:0] curr_digit;
33     reg [1:0] scan = 0;
34     reg [15:0] counter_ref = 0;
35
36     // Refresh counter increments on every clock tick
37     always @(posedge clk) begin
38         counter_ref <= counter_ref + 1;
39     end
40
41     // Move scan position on slower tick
42     always @(posedge counter_ref[15]) begin
43         scan <= scan + 1;
44     end
45
46     // Select which digit to display based on scan
47     assign curr_digit = (scan == 2'd0) ? lower_digit :
48                         (scan == 2'd1) ? upper_digit :
49                         ctrl_nibble;
50
51     // Segment control logic
52     always @(*) begin
53         case (scan)
54             2'd0: AN = 3'b110;
55             2'd1: AN = 3'b101;
56             2'd2: AN = 3'b011;
57             default: AN = 3'b111;
58         endcase
59
60         case (curr_digit)
61             4'h0: SEG = 7'b1000000;
62             4'h1: SEG = 7'b1111001;
63             4'h2: SEG = 7'b0100100;
64             4'h3: SEG = 7'b0110000;

```

65	4'h4: SEG = 7'b0011001;
66	4'h5: SEG = 7'b0010010;
67	4'h6: SEG = 7'b0000010;
68	4'h7: SEG = 7'b1111000;
69	4'h8: SEG = 7'b0000000;
70	4'h9: SEG = 7'b0010000;
71	4'hA: SEG = 7'b0001000;
72	4'hb: SEG = 7'b0000011;
73	4'hC: SEG = 7'b1000110;
74	4'hd: SEG = 7'b0100001;
75	4'hE: SEG = 7'b0000110;
76	4'hF: SEG = 7'b0001110;
77	default: SEG = 7'b1111111;
78	endcase
79	end
80	
81	endmodule

top_lab6.v: connects all submodules to implement a hardware system that counts up/down in BCD, performs addition or subtraction based on switch settings, and displays the result and control state using a 3-digit 7-segment display and LEDs.


36	module top_lab6(74	
37	input wire clk,	75	control_decoder u_ctrl_dec(
38	input wire [8:0] SW,	76	.ctrl_input(SW[8:5]),
39	input wire BTN0,	77	.ctrl_output(ctrl_nibble)
40		78);
41	output wire [7:0] LED,	79	
42	output wire [7:0] AN,	80	alu u_alu(
43	output wire [6:0] SEG	81	.A(ones_dig),
44);	82	.B(tens_dig),
45		83	.ctrl(SW[6:5]),
46	wire [3:0] ones_dig;	84	.result(result)
47	wire [3:0] tens_dig;	85);
48	wire [3:0] ctrl_nibble;	86	
49	wire [31:0] count;	87	seg7_scan u_display(
50	wire clk_div;	88	.clk(clk),
51	wire [7:0] result;	89	.rst_n(BTN0),
52		90	.lower_digit(result[3:0])
53	clk_divider u_clk_div(91	.upper_digit(result[7:4])
54	.clk(clk),	92	.ctrl_nibble(ctrl_nibble)
55	.reset_n(BTN0),	93	.SEG(SEG),
56	.sel(SW[4:0]),	94	.AN(AN)
57	.counter(count),	95);
58	.clk_div(clk_div)	96	
59);	97	assign LED = result;
60		98	assign AN[7:3] = 5'b11111;
61	bcd_counter u_ones(99	
62	.clk(clk_div),	100	endmodule
63	.bit_direct(SW[7]),		
64	.rst_n(BTN0),		
65	.value(ones_dig)		
66);		
67			
68	bcd_counter u_tens(
69	.clk(clk_div),		
70	.bit_direct(SW[8]),		
71	.rst_n(BTN0),		
72	.value(tens_dig)		
73);		

Simulation:



alu_tb.v: Adds and subtracts digits 0 - 9



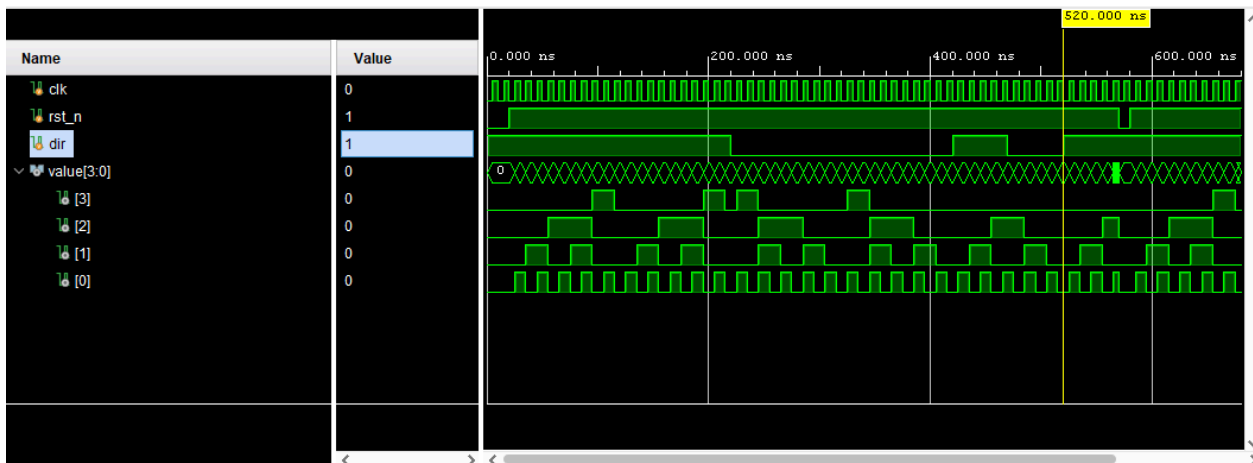
`bcd_counter_tb.v`: counts up from 0 - 9 and back down 9 - 0



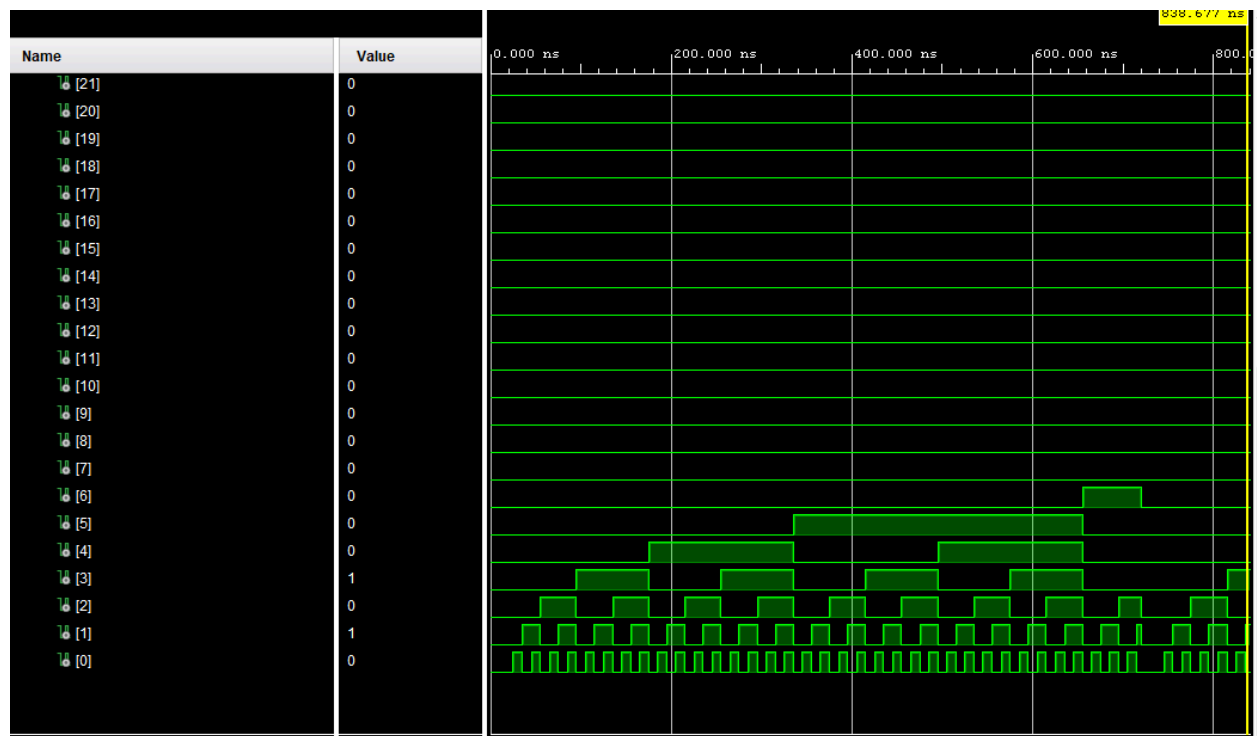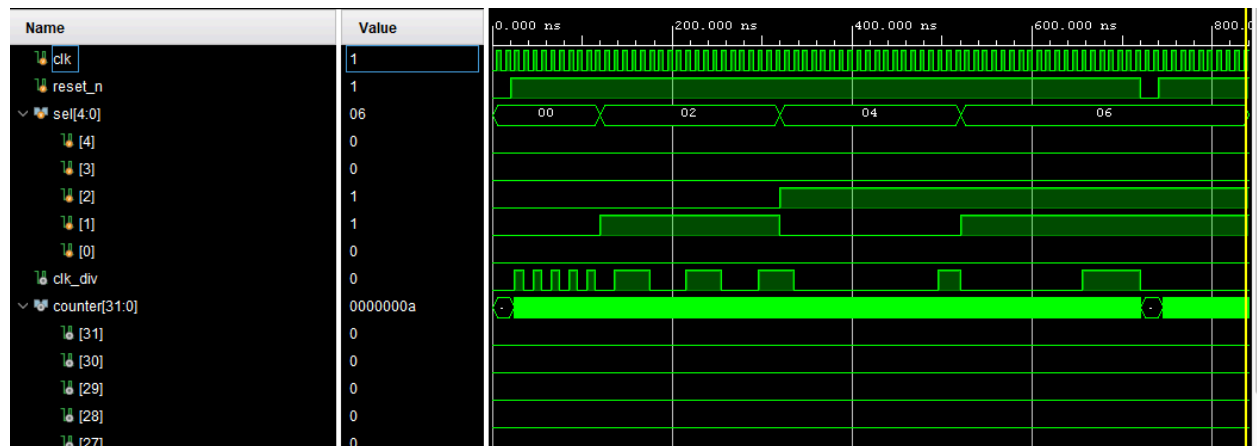
clk_divider_tb.v: Verify increment and toggle on rising edge



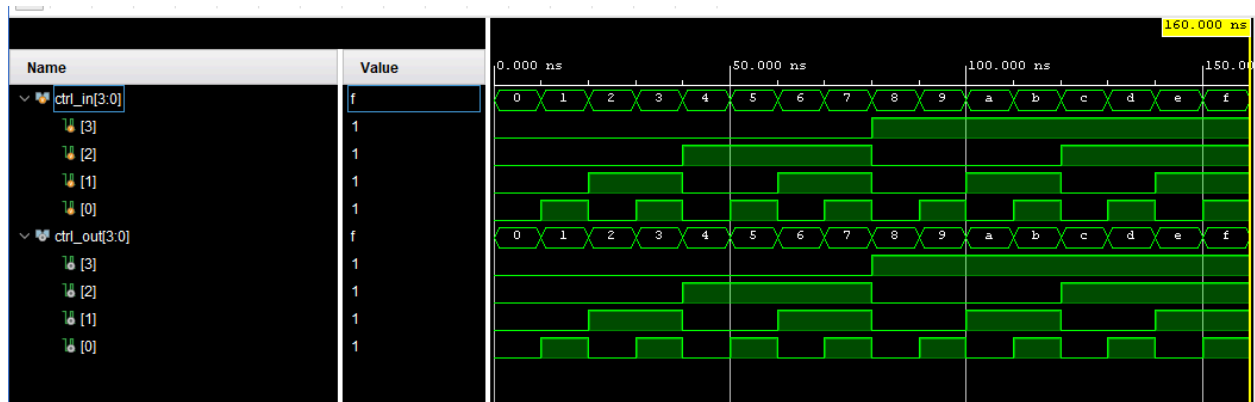control_decoder_tb.v: Verify inputs = outputs



 
`seg7_scan_tb.v`: Correctly cycles through and displays the lower, upper, and control digits on a 3-digit 7-segment display



Implementation:


Resource	Utilization	Available	Utilization %
LUT	26	63400	0.04
FF	60	126800	0.05
IO	33	210	15.71

 

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.131 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 25.6°C
Thermal Margin: 59.4°C (12.9 W)
Ambient Temperature: 25.0 °C
Effective θ_{JA} : 4.6°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

On-Chip Power

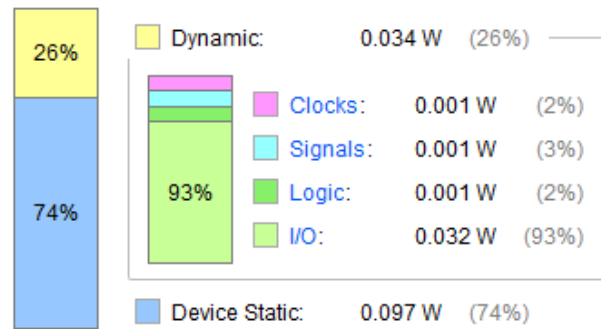

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 7.237 ns	Worst Hold Slack (WHS): 0.265 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 48	Total Number of Endpoints: 48	Total Number of Endpoints: 49

All user specified timing constraints are met.

Video Link: <https://youtu.be/4higxxSDsZA>

Contributions:

Andy Siu: (50%) Testbench, top, simulation, report, demo

Dalton Hoang: (50%) source files, top, report, implementation