## **ECE 3300L**

# Lab Report #2

## Group E

Paul Kim (ID: 015236949)

Winson Zhu (ID: 016416790)

June 25, 2025

#### **Design:**

The gate-level implementation manually defines each output using Boolean expressions with AND and NOT logic. Every output bit corresponds to one unique combination of the 4-bit input A, gated by the enable E.


```
decoder4x16_gate
input wire [3:0] sw,
input e,
output wire [15:0] led
assign led[0] = e\&\sim sw[3]\&\sim sw[2]\&\sim sw[1]\&\sim sw[0];
assign led[1] = e&\sim sw[3]&\sim sw[2]&\sim sw[1]&sw[0];
assign led[2] = e\&\sim sw[3]\&\sim sw[2]\&sw[1]\&\sim sw[0];
assign led[3] = e\&\sim sw[3]\&\sim sw[2]\&sw[1]\&sw[0];
assign led[4] = e&\sim sw[3]&sw[2]&\sim sw[1]&\sim sw[0];
assign led[5] = e&\sim sw[3]&sw[2]&\sim sw[1]&sw[0];
assign led[6] = e\&\sim sw[3]\&sw[2]\&sw[1]\&\sim sw[0];
assign led[7] = e&\sim sw[3]&sw[2]&sw[1]&sw[0];
assign led[8] = e\&sw[3]\&\sim sw[2]\&\sim sw[1]\&\sim sw[0];
assign led[9] = e&sw[3]&\sim sw[2]&\sim sw[1]&sw[0];
assign led[10] = e&sw[3]&\sim sw[2]&sw[1]&\sim sw[0];
assign led[11] = e&sw[3]&\sim sw[2]&sw[1]&sw[0];
assign led[12] = e&sw[3]&sw[2]&\sim sw[1]&\sim sw[0];
assign led[13] = e&sw[3]&sw[2]&\sim sw[1]&sw[0];
assign led[14] = e&sw[3]&sw[2]&sw[1]&~sw[0];
assign led[15] = e&sw[3]&sw[2]&sw[1]&sw[0];
```

The behavioral implementation uses an always block and case statement to set the output Y. It begins by resetting all outputs to zero, then selectively enables the correct bit based on the 4-bit input A, only when E is active.

```
decoder4x16 behav(
    output reg [15:0] led
  led = 16'b0; // reset all outputs to 0
       if (e) begin // only decode when enabled
       case (sw)
        4'b0000:led=16'b0000_0000_0000_0001; // > output 0
       4'b0001:led=16'b0000 0000 0000 0010; // > output 1
4'b0010:led=16'b0000 0000 0000 0100; // > output 2
4'b0011:led=16'b0000 0000 0000 1000; // > output 3
       4'b0100:led=16'b0000_0000_0001_0000; // > output
       4'b0101:led=16'b0000_0000_010_0000; // > output 5
4'b0110:led=16'b0000_0000_0100_0000; // > output 6
       4'b0111:led=16'b0000_0000_1000_0000; // > output 7
       4'b1000:led=16'b0000_0001_0000_0000; // > output 8
        4'b1001:led=16'b0000_0010_0000_0000; // > output 9
       4'b1010:led=16'b0000_0100_0000_0000; // > output 10
       4'b1011:led=16'b0000 1000 0000 0000; // > output 11
       4'b1101:led=16'b0010_0000_00000; // > output 13
4'b1110:led=16'b0100_0000_00000; // > output 14
       endcase
       end
ndmodule
```

### **Simulation:**



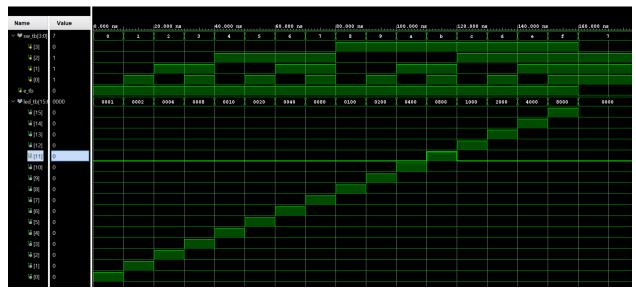

#### **Implementation:**

| Resource     | Used | Available | Utilization |  |
|--------------|------|-----------|-------------|--|
| Slice LUTs   | 8    | 63,400    | 0.013%      |  |
| Slices       | 4    | 15,850    | 0.025%      |  |
| LUT as Logic | 8    | 63,400    | 0.013%      |  |
| Bonded IOBs  | 21   | 210       | 10.0%       |  |

#### **Design Timing Summary**

| Setup                        |          | Hold                         |          | Pulse Width                              |    |
|------------------------------|----------|------------------------------|----------|--|----|
| Worst Negative Slack (WNS):  | inf      | Worst Hold Slack (WHS):      | inf      | Worst Pulse Width Slack (WPWS):          | NA |
| Total Negative Slack (TNS):  | 0.000 ns | Total Hold Slack (THS):      | 0.000 ns | Total Pulse Width Negative Slack (TPWS): | NA |
| Number of Failing Endpoints: | 0        | Number of Failing Endpoints: | 0        | Number of Failing Endpoints:             | NA |
| Total Number of Endpoints:   | 16       | Total Number of Endpoints:   | 16       | Total Number of Endpoints:               | NA |

There are no user specified timing constraints.

### **Contributions:**

Paul Kim - Testbench, Behavioral Code, Simulation - 50% contribution

Winson Zhu - Gate-Level Design, Hardware Demo - 50% contribution

### **Group Video Link:**

https://youtu.be/VDF3Er3c-Ik