

Lab 5 Report

by

Jonathan Huynh #016137719

Adam Godfrey #015981472

Instructor: Dr. Mohamed Aly

Class: ECE 3300L .E02-OU - Verilog Design

July 21st, 2025

Code with Explanation:

BCD Up/Down Counter on 7-Segment Display Top Module Code

```
`timescale 1ns / 1ps
module top_lab5 (
    input wire CLK,
    input wire BTN0,
    input wire BTN1,
    input wire [4:0] SW,
    output wire [6:0] SEG,
    output wire [7:0] AN,
    output wire [4:0] SWLED,
    output wire [7:0] BCDLED
);

wire [31:0] tick_counter;
wire divided_clk;
wire [3:0] unit_bcd, ten_bcd;
wire carry_from_unit;
wire rst_n = BTN0;
wire dir = BTN1;

clock_divider clk_div_inst (
    .sys_clk(CLK),
    .reset_n(rst_n),
    .tick_count(tick_counter)
);

mux32x1 mux_inst (
    .tick_bits(tick_counter),
    .speed_select(SW),
    .clk_out(divided_clk)
);

bcd_up_down_counter unit_counter (
    .clk_pulse(divided_clk),
    .rst_n(rst_n),
    .dir_up(dir),
    .enable_count(1'b1),
    .bcd_value(unit_bcd),
    .carry_pulse(carry_from_unit)
);

bcd_up_down_counter ten_counter (
    .clk_pulse(divided_clk),
    .rst_n(rst_n),
    .dir_up(dir),
    .enable_count(carry_from_unit),
    .bcd_value(ten_bcd),
```

This Verilog module, *top_lab5*, is the top-level design for a two-digit BCD up/down counter system. It takes inputs from a system clock (**CLK**), two push buttons (**BTN0** for *reset* and **BTN1** for *direction*), and a 5-bit switch array (**SW**). The outputs include signals to drive a 7-segment display (**SEG** and **AN**), display switch states (**SWLED**), and show the current BCD values on LEDs (**BCDLED**). Internally, a *clock_divider* and *mux32x1* module work together to generate a divided clock signal based on the selected speed from the switches.

The system uses two chained *bcd_up_down_counter* modules to represent units and tens digits. The unit counter always counts when the divided clock pulses, while the tens counter only increments or decrements when the unit counter produces a carry. This allows the system to count from 00 to 99 or in reverse, depending on the state of **BTN1**. The *reset* signal (**BTN0**) clears both counters when active. The BCD outputs from both counters are wired to LEDs for debugging and also routed to the 7-segment display driver.

The *seg7_scan* module handles fast multiplexed scanning of the 7-segment display to show the units and tens values. The anode control disables the upper six digits (**AN[7:2] = 6'b111111**) so only the two least significant digits are used. Additional assignments connect the switch inputs directly to LEDs (**SWLED**) and display the current BCD values on **BCDLED**. This design provides a way to demonstrate BCD counting with adjustable speed and direction.

<pre> .carry_pulse()); seg7_scan scan_driver (.clk_fast(CLK), .rst_n(rst_n), .units_val(unit_bcd), .tens_val(ten_bcd), .seg_pins(SEG), .dp(), .anodes(AN)); assign AN[7:2] = 6'b111111; assign SWLED[4:0] = SW; assign BCDLED[3:0] = unit_bcd; assign BCDLED[7:4] = ten_bcd; endmodule </pre>	
---	--

<u>Clock Divider Code</u>	
<pre> `timescale 1ns / 1ps module clock_divider (input wire sys_clk, input wire reset_n, output reg [31:0] tick_count); always @(posedge sys_clk or negedge reset_n) begin if (!reset_n) tick_count <= 0; else tick_count <= tick_count + 1; end endmodule </pre>	<p>The <i>clock_divider</i> module generates a 32-bit counter (tick_count) by incrementing it on every rising edge of the system clock (sys_clk). This effectively divides the clock frequency by creating slower pulses at each bit of the counter. The counter resets to zero asynchronously when reset_n is low. Each bit in tick_count can be used to derive a clock signal at a specific divided frequency, making this module useful for generating slower timing signals from a fast system clock.</p>

<u>MUX 32x1 Code</u>	
<pre> `timescale 1ns / 1ps module mux32x1 (input wire [31:0] tick_bits, input wire [4:0] speed_select, output wire clk_out); </pre>	<p>The <i>mux32x1</i> module selects one of the 32 bits from the tick_bits input based on the 5-bit speed_select value and outputs it as clk_out. Since each bit in tick_bits represents a progressively slower clock (from the <i>clock_divider</i> module), this acts as a</p>

<pre> assign clk_out = tick_bits[speed_select]; endmodule </pre>	32-to-1 multiplexer that allows the user to choose the desired clock frequency by adjusting speed_select . This makes it easy to dynamically control the speed of a system, such as a counter, using external inputs like switches.
---	--

<u>BCD Up/Down Counter Code</u>	
<pre> module bcd_up_down_counter (input wire clk_pulse, input wire rst_n, input wire dir_up, input wire enable_count, output reg [3:0] bcd_value, output reg carry_pulse); always @(posedge clk_pulse or negedge rst_n) begin if (!rst_n) begin bcd_value <= 0; carry_pulse <= 0; end else if (enable_count) begin carry_pulse <= 0; if (dir_up) begin if (bcd_value == 1) begin bcd_value <= 0; carry_pulse <= 1; end else if (bcd_value == 0) begin bcd_value <= 9; end else begin bcd_value <= bcd_value - 1; end end else begin if (bcd_value == 8) begin bcd_value <= 9; carry_pulse <= 1; end else if (bcd_value == 9) begin bcd_value <= 0; end else begin bcd_value <= bcd_value + 1; end end end end end </pre>	<p>In the <i>bcd_up_down_counter</i> module we designed, we created a 4-bit counter that can count either up or down depending on the dir_up input. It updates on the rising edge of the clock pulse and can be asynchronously reset with rst_n. When counting is enabled, the counter either increments or decrements the BCD value stored in bcd_value, and we use carry_pulse to signal when the count rolls over like from 9 back to 0 or 0 down to 9.</p>

endmodule	
-----------	--

7 Segment Code

```
`timescale 1ns / 1ps
module seg7_scan (
    input wire clk_fast,
    input wire rst_n,
    input wire [3:0] units_val,
    input wire [3:0] tens_val,
    output reg [6:0] seg_pins,
    output wire dp,
    output reg [1:0] anodes
);

reg [15:0] refresh_timer;
wire current_digit = refresh_timer[13];

assign dp = 1'b1;

always @(posedge clk_fast or negedge
rst_n) begin
    if (!rst_n)
        refresh_timer <= 0;
    else
        refresh_timer <= refresh_timer + 1;
end

always @(*) begin
    case (current_digit)
        1'b0: begin
            anodes = 2'b10;
            case (units_val)
                4'd0: seg_pins = 7'b1000000;
                4'd1: seg_pins = 7'b1001111;
                4'd2: seg_pins = 7'b0100100;
                4'd3: seg_pins = 7'b0110000;
                4'd4: seg_pins = 7'b0011001;
                4'd5: seg_pins = 7'b0010010;
                4'd6: seg_pins = 7'b0000010;
                4'd7: seg_pins = 7'b1111000;
                4'd8: seg_pins = 7'b0000000;
                4'd9: seg_pins = 7'b0010000;
                default: seg_pins = 7'b1111111;
            endcase
        end
        1'b1: begin
            anodes = 2'b01;
            case (tens_val)
```

This Verilog module, *seg7_scan*, is responsible for driving a two-digit 7-segment display using time-multiplexing. It receives a high-frequency clock (**clk_fast**) and a reset signal (**rst_n**), along with 4-bit BCD inputs representing the units (**units_val**) and tens (**tens_val**) digits. It outputs 7 segment control lines (**seg_pins**), a decimal point (**dp**, which is disabled), and anode control lines (**anodes**) to select which digit is currently active.


The module uses a 16-bit **refresh_timer** to alternate between displaying the units and tens digits at a rate determined by bit 13 of the timer. This bit acts as a simple frequency divider to toggle the active digit approximately every few milliseconds, creating the illusion that both digits are lit continuously to the human eye. When **current_digit** is 0, the module displays the units digit and activates the corresponding anode (2'b10) when 1, it shows the tens digit and activates its anode (2'b01).

Each digit is converted from its 4-bit BCD value to a corresponding 7-segment encoding using a case statement. If the value is outside 0–9, the display shows blank (7'b1111111). This design allows efficient scanning of two 7-segment digits using minimal pins and ensures flicker-free operation using the fast input clock and timer-based digit switching.

<pre> 4'd0: seg_pins = 7'b1000000; 4'd1: seg_pins = 7'b1001111; 4'd2: seg_pins = 7'b0100100; 4'd3: seg_pins = 7'b0110000; 4'd4: seg_pins = 7'b0011001; 4'd5: seg_pins = 7'b0010010; 4'd6: seg_pins = 7'b0000010; 4'd7: seg_pins = 7'b1111000; 4'd8: seg_pins = 7'b0000000; 4'd9: seg_pins = 7'b0010000; default: seg_pins = 7'b1111111; endcase end endcase end endmodule </pre>	
--	--

Screenshot Proofs:

Resource Utilization Table:

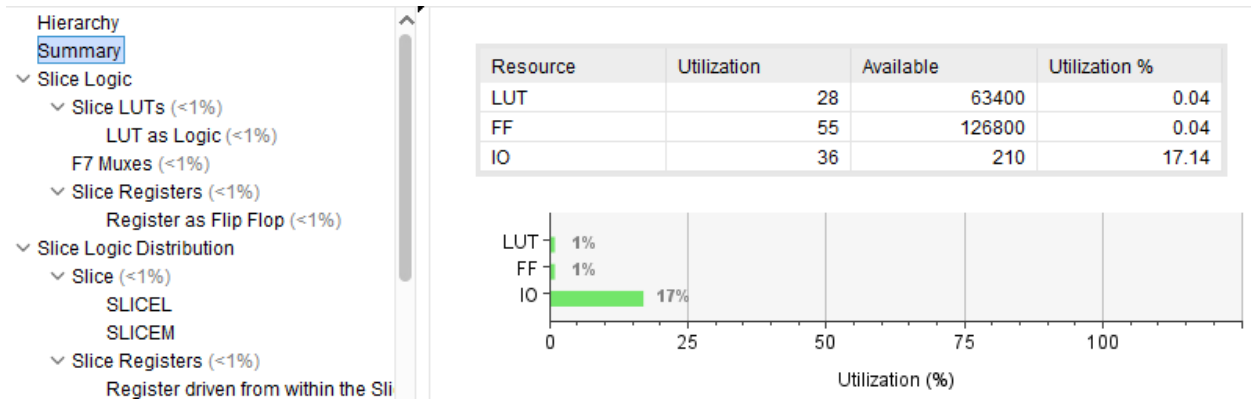

Power Utilization:

Settings

Summary (0.127 W, Margin: N/A)

Power Supply

Utilization Details

Hierarchical (0.03 W)

Clocks (0.001 W)

Signals (<0.001 W)

Data (<0.001 W)

Clock Enable (<0.001 W)

Set/Reset (0 W)

Logic (<0.001 W)

IO (0.029 W)

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:

0.127 W

Design Power Budget:

Not Specified

Process:

typical

Power Budget Margin:

N/A

Junction Temperature:

25.6°C

Thermal Margin:

59.4°C (12.9 W)

Ambient Temperature:

25.0 °C

Effective θJA:

4.6°C/W

Power supplied to off-chip devices:

0 W

Confidence level:

Low

Launch Power Constraint Advisor

to find and fix invalid switching activity

On-Chip Power

24%

76%

Dynamic: 0.030 W (24%)

Clocks: 0.001 W (2%)

Signals: <0.001 W (2%)

Logic: <0.001 W (1%)

IO: 0.029 W (95%)

95%

Device Static: 0.097 W (76%)

Timing Summary:

Q

⌵

⌶

↺

📄

●

General Information

Timer Settings

Design Timing Summary

Clock Summary (1)

Methodology Summary (25)

Check Timing (374)

Intra-Clock Paths

Inter-Clock Paths

Other Path Groups

User Ignored Paths

Unconstrained Paths


Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 7.349 ns	Worst Hold Slack (WHS): 0.254 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 46	Total Number of Endpoints: 46	Total Number of Endpoints: 47


All user specified timing constraints are met.

Simulation Waveform:

 
BCD Up/Down Counter on 7-Segment Display Full Waveform:




BCD Up/Down Counter Module Waveform:

 


Clock Divider Module Waveform:

 

MUX 32x1 Module Waveform:

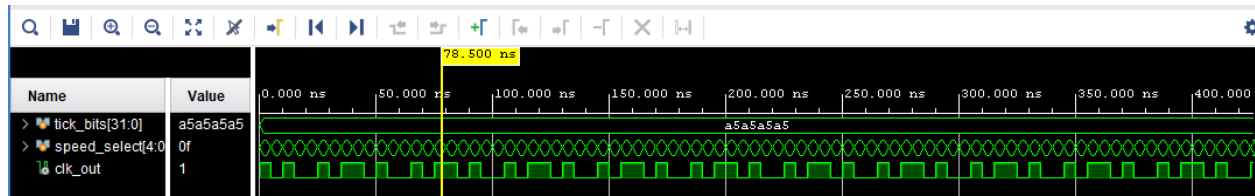

7 Segment Module Waveform:

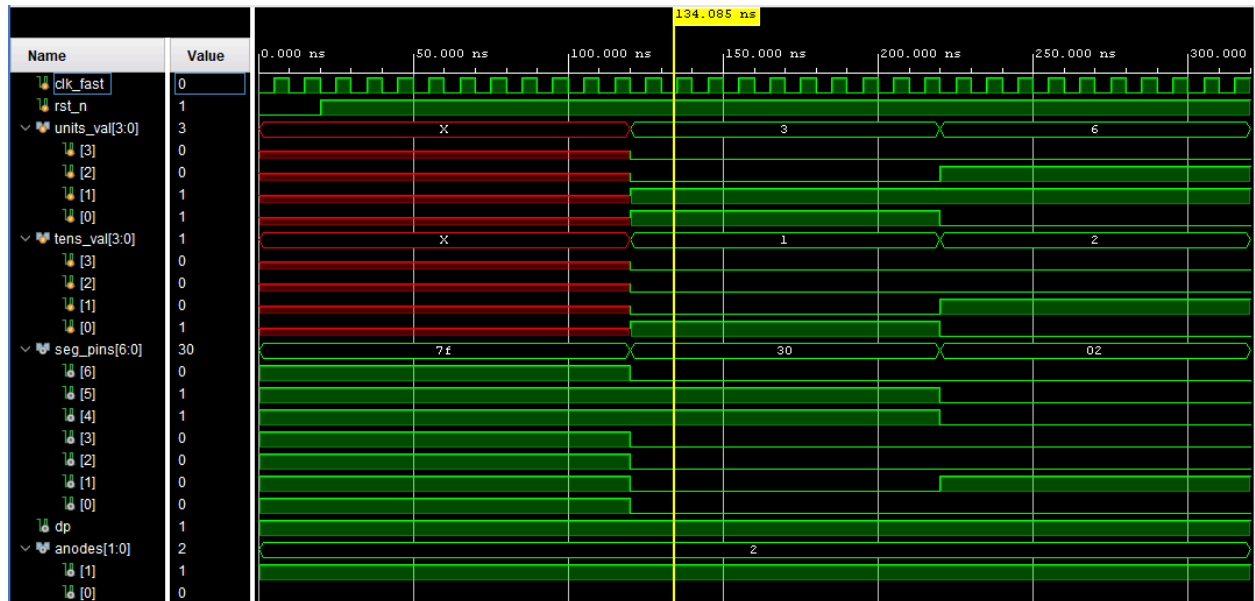

Partner Contributions:

Team Member	Contribution	% Effort
Jonathan Huynh	Code: [Clock Divide, BCD Up/Down Counter, 32x1 MUX] Testbench: [Top Module and 32x1 MUX] Additional: Synthesis/Implementation and Demo	50%
Adam Godfrey	Code: [7 Segment and Top Module] Testbench: [7 Segment, BCD Up/Down, Clock Divider] Additional: Simulation and Lab Report	50%