

California Polytechnic State University, Pomona
Department of Electrical and Computer Engineering

Digital Circuit Design Using Verilog Laboratory
ECE 3300L

Lab 7



16-bit Barrel Shifter / Rotator & 4-Digit 7-Segment Display

By

**Jetts Crittenden (ID# 015468128) and
Evan Tram(#ID 016404570)**

8/7/2025

Design:

This design uses the basic principles from previous labs and reuses them in tandem with new methods. This project uses the generation of different trees of shifts with basic logic design to provide a system that allows the user to shift, change shift type (Logical / Rotate), and the direction of the shift. It controls these inputs through debounced and controlled inputs from the push buttons on the Nexys board. The original word value is also input through the switches on the board. It then displays the shifted 4-digit hex value on the 7-segment board just like in previous labs.

Code:

top_lab7.v

```
`timescale 1ns / 1ps

module top_lab7(
    input wire clk,                // 100 MHz system clock
    /
    input wire [15:0] SW,          // Slide switches for input
word
    input wire [4:0] BTN,          // BTN[4] = BTNC, BTN[3:0] =
BTNU, BTND, BTNL, BTNR
    output wire [7:0] LED,         // Optional debug LEDs
    output wire [6:0] SEG,         // 7-segment segments
    output wire DP,
    output wire [7:0] AN           // Digit enables
);

    wire rst_n;
    wire clk_rst;
    assign DP = 1;
    wire clk_1kHz, clk_2Hz;
    clock_divider_fixed clkdiv (
        .clk(clk),
        .rst_n(clk_rst),
        .clk_out(clk_1kHz)
    );

    // Debounced Button Toggles
```

```

    wire dir, rot;
    wire [1:0] shamtl;
    wire [1:0] shamtm;
    wire btnc_toggle;

    debounce_toggle db_dir (.clk(clk_1kHz),
    .btn_raw(BTN[0]), .btn_toggle(dir)); // BTNL
    debounce_toggle db_rot (.clk(clk_1kHz),
    .btn_raw(BTN[1]), .btn_toggle(rot)); // BTNR
    debounce_toggle db_shamt0 (.clk(clk_1kHz),
    .btn_raw(BTN[2]), .btn_toggle(shamtl[0])); // BTND
    debounce_toggle db_shamt1 (.clk(clk_1kHz),
    .btn_raw(BTN[3]), .btn_toggle(shamtl[1])); // BTNU

    //SHAMT Counter (MSBs)
    wire btnc_raw = BTN[4];
    assign rst_n = ~btnc_raw;
    assign clk_rst = 1; // reset disable for now
    shamt_counter shamt_ctrl (
        .clk(clk_1kHz), // 1 kHz clock
        .btn_raw(btnc_raw), // Raw BTNC input
        .shamt(shamtm) // One-cycle pulse for SHAMT
increment
    );

    wire [3:0] shamtl = {shamtm, shamtl}; // Combine MSBs and
LSBs

    // Barrel Shifter
    wire [15:0] barrel_out;
    barrel_shifter16 shifter (
        .data_in(SW[15:0]),
        .shamt(shamtl),
        .dir(dir),
        .rotate(rot),
        .data_out(barrel_out)
    );

```

```

    );

// Segment Scanner
    wire [3:0] ones, tens, hundreds, thousands;
    assign ones = barrel_out[3:0];
    assign tens = barrel_out[7:4];
    assign hundreds = barrel_out[11:8];
    assign thousands = barrel_out[15:12];
    seg7_scan8 scanner (
        .clk(clk),
        .rst_n(rst_n),
        .onesPlace(ones),
        .tensPlace(tens),
        .hundredsPlace(hundreds),
        .thousandsPlace(thousands),
        .SEG(SEG),
        .AN(AN)
    );

// 💡 Optional Debug LEDs
    assign LED[7] = dir;
    assign LED[6] = rot;
    assign LED[5:2] = shamt;
    assign LED[1:0] = 2'b00; // Unused or reserved
endmodule

```

barrel_shifter16.v

`timescale 1ns / 1ps

```

module barrel_shifter16(
    input wire [15:0] data_in,
    input wire [3:0] shamt,
    input wire dir,           // 0 = left, 1 = right
    input wire rotate,       // 0 = logical, 1 = rotate
    output wire [15:0] data_out

```

```

);

wire [15:0] stage [0:4]; // 5 stages: input + 4 shift stages
assign stage[0] = data_in;

genvar i;
generate
    for (i = 0; i < 4; i = i + 1) begin : shift_stage
        wire [15:0] shifted;
        wire [15:0] fill;

        // Shift amount for this stage: 2^i
        localparam integer SHIFT = 1 << i;

        // Fill bits depend on rotate vs logical
        assign fill = (rotate) ?
            (dir ? stage[i] << (16 - SHIFT) : stage[i] >>
(16 - SHIFT)) :
            16'b0;

        assign shifted = (dir) ?
            (stage[i] >> SHIFT) | fill :
            (stage[i] << SHIFT) | fill;

        assign stage[i+1] = (shamt[i]) ? shifted : stage[i];
    end
endgenerate

assign data_out = stage[4];

endmodule

```

clock_divider_fixed.v

```

`timescale 1ns / 1ps

```

```

module clock_divider_fixed(
    input wire clk,           // 100 MHz input clock
    input wire rst_n,        // Active-low reset
    output reg clk_out        // Slower output clock
);

    parameter DIV_VALUE = 26'd50_000; // Half-period count
    reg [25:0] cnt;

    always @(posedge clk or negedge rst_n) begin
        if (!rst_n) begin
            cnt <= 0;
            clk_out <= 0;
        end else begin
            if (cnt == DIV_VALUE - 1) begin
                cnt <= 0;
                clk_out <= ~clk_out; // Toggle output clock
            end else begin
                cnt <= cnt + 1;
            end
        end
    end
end

endmodule

```

debounce_toggle.v

```

module debounce_toggle (
    input wire clk,
    input wire btn_raw,    // Raw button input
    output reg btn_toggle  // Toggled output state
);

    wire btn_clean;
    reg btn_prev;

    // Debounce module (assumed to be defined elsewhere)
    debounce db (

```

```

        .clk(clk),
        .btn_in(btn_raw),
        .btn_clean(btn_clean)
    );

    always @(posedge clk ) begin

        if (btn_clean && !btn_prev)
            btn_toggle <= ~btn_toggle; // Toggle on rising edge
            btn_prev <= btn_clean;
        end

    endmodule

```

shamt_counter.v

```

`timescale 1ns / 1ps

module shamt_counter (
    input wire clk,           // 1 kHz clock
    input wire btn_raw,      // Raw BTNC input
    output reg [1:0] shamt    // One-cycle pulse for SHAMT increment
);
    reg shamt_pulse;
    wire btn_clean;
    reg btn_prev;

    // Debounce the raw button
    debounce db (
        .clk(clk),
        .btn_in(btn_raw),
        .btn_clean(btn_clean)
    );

    // One-cycle pulse on rising edge of debounced button
    always @(posedge clk) begin
        btn_prev <= btn_clean;
        shamt_pulse <= btn_clean & ~btn_prev;
    end
endmodule

```

```

        if (shamt_pulse) begin
            shamt <= shamt + 1;
        end
    end

endmodule

```

hex_to_7seg.v

```

`timescale 1ns / 1ps

module hex_to_7seg(
    input wire [3:0] digitVal,
    output reg [6:0] SEG
);
    always@(*)
        begin
            case(digitVal)
                4'd0: SEG = 7'b1000000; // 0
                4'd1: SEG = 7'b1111001; // 1
                4'd2: SEG = 7'b0100100; // 2
                4'd3: SEG = 7'b0110000; // 3
                4'd4: SEG = 7'b0011001; // 4
                4'd5: SEG = 7'b0010010; // 5
                4'd6: SEG = 7'b0000010; // 6
                4'd7: SEG = 7'b1111000; // 7
                4'd8: SEG = 7'b0000000; // 8
                4'd9: SEG = 7'b0010000; // 9
                4'd10: SEG = 7'b0001000; // A
                4'd11: SEG = 7'b0000011; // b
                4'd12: SEG = 7'b1000110; // C
                4'd13: SEG = 7'b0100001; // d
                4'd14: SEG = 7'b0000110; // E
                4'd15: SEG = 7'b0001110; // F
                default: SEG = 7'b1111111; // Blank
            endcase
        end
endmodule

```



```
endmodule
```

seg7_scan8.v

```
`timescale 1ns / 1ps

module seg7_scan8(
    input wire clk,
    input wire rst_n,
    input wire [3:0] onesPlace,
    input wire [3:0] tensPlace,
    input wire [3:0] hundredsPlace,
    input wire [3:0] thousandsPlace,
    output wire [6:0] SEG,
    output reg [7:0] AN
);

    reg [19:0] refresh_counter = 0;
    wire [1:0] sel;
    reg [3:0] digit_val;
    wire [6:0] seg_val;
    assign SEG = seg_val;
    assign sel = refresh_counter[19:18];

    always @(posedge clk or negedge rst_n)
        begin
            if (!rst_n)
                refresh_counter <= 0;
            else
                refresh_counter <= refresh_counter + 1;
        end

    always @(*)
        begin
            case(sel)
                2'd0:
                    begin
                        AN = 8'b11111110;

```

```


        digit_val = onesPlace;
    end
    2'd1:
    begin
        AN = 8'b11111101;
        digit_val = tensPlace;
    end
    2'd2:
    begin
        AN = 8'b11111011;
        digit_val = hundredsPlace;
    end
    2'd3:
    begin
        AN = 8'b11110111;
        digit_val = thousandsPlace;
    end
    default: AN = 8'b11111111;
endcase
end

hex_to_7seg decoder (
    .digitVal(digit_val),
    .SEG(seg_val)
);

endmodule

```

Hardware Schematic:

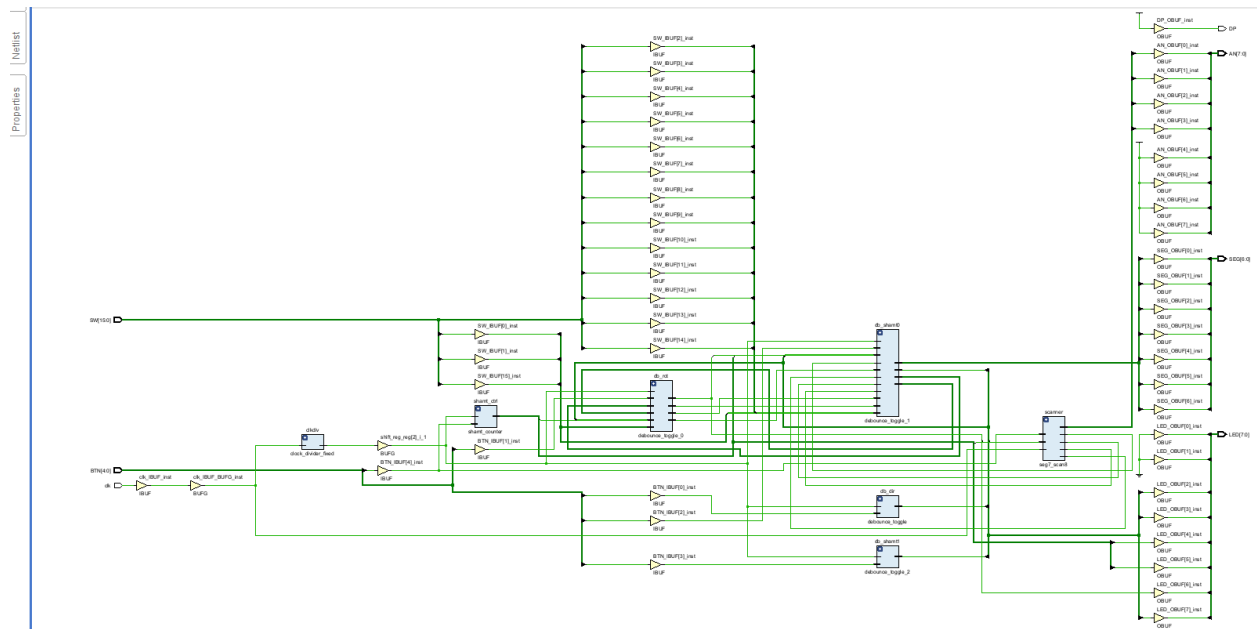

XDC Snippet:

```
## Clock signal
set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 }
[get_ports { clk }]; #IO_L12P_T1_MRCC_35 Sch=clk100mhz
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5}
[get_ports {clk}];
```

##Switches

```
set_property -dict { PACKAGE_PIN J15      IOSTANDARD LVCMOS33 }
[get_ports { SW[0] }]; #IO_L24N_T3_RS0_15 Sch=sw[0]
set_property -dict { PACKAGE_PIN L16      IOSTANDARD LVCMOS33 }
[get_ports { SW[1] }]; #IO_L3N_T0_DQS_EMCCLK_14 Sch=sw[1]
set_property -dict { PACKAGE_PIN M13      IOSTANDARD LVCMOS33 }
[get_ports { SW[2] }]; #IO_L6N_T0_D08_VREF_14 Sch=sw[2]
set_property -dict { PACKAGE_PIN R15      IOSTANDARD LVCMOS33 }
[get_ports { SW[3] }]; #IO_L13N_T2_MRCC_14 Sch=sw[3]
set_property -dict { PACKAGE_PIN R17      IOSTANDARD LVCMOS33 }
[get_ports { SW[4] }]; #IO_L12N_T1_MRCC_14 Sch=sw[4]
set_property -dict { PACKAGE_PIN T18      IOSTANDARD LVCMOS33 }
[get_ports { SW[5] }]; #IO_L7N_T1_D10_14 Sch=sw[5]
set_property -dict { PACKAGE_PIN U18      IOSTANDARD LVCMOS33 }
[get_ports { SW[6] }]; #IO_L17N_T2_A13_D29_14 Sch=sw[6]
```

```
set_property -dict { PACKAGE_PIN R13    IOSTANDARD LVCMOS33 }
[get_ports { SW[7] }]; #IO_L5N_T0_D07_14 Sch=sw[7]
set_property -dict { PACKAGE_PIN T8     IOSTANDARD LVCMOS18 }
[get_ports { SW[8] }]; #IO_L24N_T3_34 Sch=sw[8]
set_property -dict { PACKAGE_PIN U8     IOSTANDARD LVCMOS18 }
[get_ports { SW[9] }]; #IO_25_34 Sch=sw[9]
set_property -dict { PACKAGE_PIN R16    IOSTANDARD LVCMOS33 }
[get_ports { SW[10] }]; #IO_L15P_T2_DQS_RDWR_B_14 Sch=sw[10]
set_property -dict { PACKAGE_PIN T13    IOSTANDARD LVCMOS33 }
[get_ports { SW[11] }]; #IO_L23P_T3_A03_D19_14 Sch=sw[11]
set_property -dict { PACKAGE_PIN H6     IOSTANDARD LVCMOS33 }
[get_ports { SW[12] }]; #IO_L24P_T3_35 Sch=sw[12]
set_property -dict { PACKAGE_PIN U12    IOSTANDARD LVCMOS33 }
[get_ports { SW[13] }]; #IO_L20P_T3_A08_D24_14 Sch=sw[13]
set_property -dict { PACKAGE_PIN U11    IOSTANDARD LVCMOS33 }
[get_ports { SW[14] }]; #IO_L19N_T3_A09_D25_VREF_14 Sch=sw[14]
set_property -dict { PACKAGE_PIN V10    IOSTANDARD LVCMOS33 }
[get_ports { SW[15] }]; #IO_L21P_T3_DQS_14 Sch=sw[15]
```

LEDs

```
set_property -dict { PACKAGE_PIN H17    IOSTANDARD LVCMOS33 }
[get_ports { LED[0] }]; #IO_L18P_T2_A24_15 Sch=led[0]
set_property -dict { PACKAGE_PIN K15    IOSTANDARD LVCMOS33 }
[get_ports { LED[1] }]; #IO_L24P_T3_RS1_15 Sch=led[1]
set_property -dict { PACKAGE_PIN J13    IOSTANDARD LVCMOS33 }
[get_ports { LED[2] }]; #IO_L17N_T2_A25_15 Sch=led[2]
set_property -dict { PACKAGE_PIN N14    IOSTANDARD LVCMOS33 }
[get_ports { LED[3] }]; #IO_L8P_T1_D11_14 Sch=led[3]
set_property -dict { PACKAGE_PIN R18    IOSTANDARD LVCMOS33 }
[get_ports { LED[4] }]; #IO_L7P_T1_D09_14 Sch=led[4]
set_property -dict { PACKAGE_PIN V17    IOSTANDARD LVCMOS33 }
[get_ports { LED[5] }]; #IO_L18N_T2_A11_D27_14 Sch=led[5]
set_property -dict { PACKAGE_PIN U17    IOSTANDARD LVCMOS33 }
[get_ports { LED[6] }]; #IO_L17P_T2_A14_D30_14 Sch=led[6]
set_property -dict { PACKAGE_PIN U16    IOSTANDARD LVCMOS33 }
[get_ports { LED[7] }]; #IO_L18P_T2_A12_D28_14 Sch=led[7]
```

##7 segment display

```
set_property -dict { PACKAGE_PIN T10    IOSTANDARD LVCMOS33 }
[get_ports { SEG[0] }]; #IO_L24N_T3_A00_D16_14 Sch=ca
```

```

set_property -dict { PACKAGE_PIN R10    IOSTANDARD LVCMOS33 }
[get_ports { SEG[1] }]; #IO_25_14 Sch=cb
set_property -dict { PACKAGE_PIN K16    IOSTANDARD LVCMOS33 }
[get_ports { SEG[2] }]; #IO_25_15 Sch=cc
set_property -dict { PACKAGE_PIN K13    IOSTANDARD LVCMOS33 }
[get_ports { SEG[3] }]; #IO_L17P_T2_A26_15 Sch=cd
set_property -dict { PACKAGE_PIN P15    IOSTANDARD LVCMOS33 }
[get_ports { SEG[4] }]; #IO_L13P_T2_MRCC_14 Sch=ce
set_property -dict { PACKAGE_PIN T11    IOSTANDARD LVCMOS33 }
[get_ports { SEG[5] }]; #IO_L19P_T3_A10_D26_14 Sch=cf
set_property -dict { PACKAGE_PIN L18    IOSTANDARD LVCMOS33 }
[get_ports { SEG[6] }]; #IO_L4P_T0_D04_14 Sch=cg
set_property -dict { PACKAGE_PIN H15    IOSTANDARD LVCMOS33 }
[get_ports { DP }]; #IO_L19N_T3_A21_VREF_15 Sch=dp
set_property -dict { PACKAGE_PIN J17    IOSTANDARD LVCMOS33 }
[get_ports { AN[0] }]; #IO_L23P_T3_F0E_B_15 Sch=an[0]
set_property -dict { PACKAGE_PIN J18    IOSTANDARD LVCMOS33 }
[get_ports { AN[1] }]; #IO_L23N_T3_FWE_B_15 Sch=an[1]
set_property -dict { PACKAGE_PIN T9     IOSTANDARD LVCMOS33 }
[get_ports { AN[2] }]; #IO_L24P_T3_A01_D17_14 Sch=an[2]
set_property -dict { PACKAGE_PIN J14    IOSTANDARD LVCMOS33 }
[get_ports { AN[3] }]; #IO_L19P_T3_A22_15 Sch=an[3]
set_property -dict { PACKAGE_PIN P14    IOSTANDARD LVCMOS33 }
[get_ports { AN[4] }]; #IO_L8N_T1_D12_14 Sch=an[4]
set_property -dict { PACKAGE_PIN T14    IOSTANDARD LVCMOS33 }
[get_ports { AN[5] }]; #IO_L14P_T2_SRCC_14 Sch=an[5]
set_property -dict { PACKAGE_PIN K2     IOSTANDARD LVCMOS33 }
[get_ports { AN[6] }]; #IO_L23P_T3_35 Sch=an[6]
set_property -dict { PACKAGE_PIN U13    IOSTANDARD LVCMOS33 }
[get_ports { AN[7] }]; #IO_L23N_T3_A02_D18_14 Sch=an[7]

##CPU Reset Button
#set_property -dict { PACKAGE_PIN C12    IOSTANDARD LVCMOS33 }
[get_ports { CPU_RESETN }]; #IO_L3P_T0_DQS_AD1P_15 Sch=cpu_resetrn

##Buttons
set_property -dict { PACKAGE_PIN N17    IOSTANDARD LVCMOS33 }
[get_ports { BTN[4] }]; #IO_L9P_T1_DQS_14 Sch=btnc
set_property -dict { PACKAGE_PIN M18    IOSTANDARD LVCMOS33 }


```

```
[get_ports { BTN[3] }]; #IO_L4N_T0_D05_14 Sch=btneu
set_property -dict { PACKAGE_PIN P17 IOSTANDARD LVCMOS33 }
[get_ports { BTN[0] }]; #IO_L12P_T1_MRCC_14 Sch=btnl
set_property -dict { PACKAGE_PIN M17 IOSTANDARD LVCMOS33 }
[get_ports { BTN[1] }]; #IO_L10N_T1_D15_14 Sch=btnr
set_property -dict { PACKAGE_PIN P18 IOSTANDARD LVCMOS33 }
[get_ports { BTN[2] }]; #IO_L9N_T1_DQS_D13_14 Sch=btnd
```

Simulation:

The testbench code was withheld from the report to avoid distracting from the content. All testbench code is found in the GitHub repository.


barrel_shifter16_tb.v

 


clock_divider_fixed_tb.v




debounce_toggle_tb.v

 


shamt_counter_tb.v

 

hex_to_7seg_tb.v

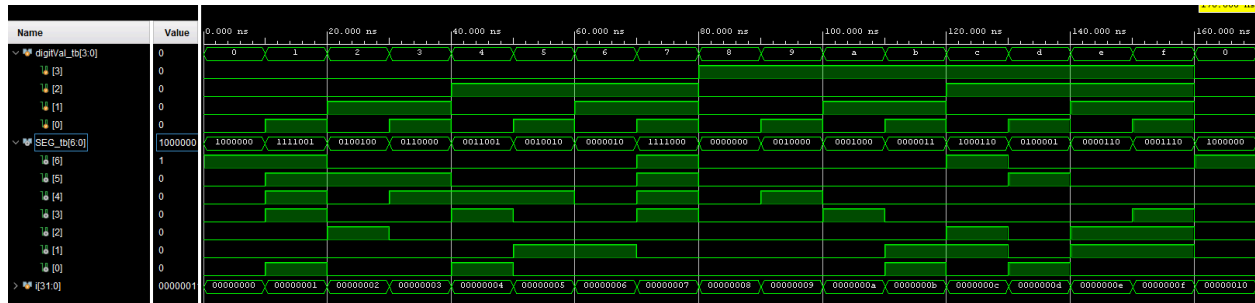

seg7_scan8_tb.v

 

Implementation: Resource utilization table(s):

Slice Logic Utilization:

LUTs Used: **80 used 0.13% Utilization**

Registers Used: 79 used 0.06% Utilization

Muxes:

F7: 0 used

F8: 0 used

Registers:

Registers used as Flip-flops

IO: 46 IO used , 21.9% Utilization

Timing:

Worst Negative Slack: 4.740 ns, 72 endpoints

Worst Hold Slack: 0.140 ns, 72 endpoints

Worst Pulse Width Slack: 4.500 ns, 48 endpoints

Timing constraints are met, providing adequate slack.

Group video link:

<https://youtu.be/5cZJpbCB5Aw?si=F6NKejCM2gSPB-SU>

Contributions:

The contributions of this report were equally split. Both Jetts Crittenden and Evan Tram worked on the modules and testbenches separately and collaborated during the discussion and the development of the `top_lab7.v` module to appropriately combine the modules. Many of the modules used in this lab were used in previous labs, such as the 7-segment scan module, which was also developed with equal effort on both parts of the team. The demo video was recorded by Jetts Crittenden, and synthesis reports were recorded by Evan Tram, with the paper being written by both team members.