

# Lab 2 Report

---

*by*

**Jonathan Huynh #016137719**

**Adam Godfrey #015981472**

*Instructor:* Dr. Mohamed Aly

*Class:* ECE 3300L.E02-OU - Verilog Design

June 25th, 2025

## Summary:

In lab 2, we are tasked with designing, simulating, and implementing a 4-to-16 decoder along with an enable input on our Digilent Nexys A7-100T board.

## Design:

<u>Behavior Level Snippet:</u>	<u>Gate Level Snippet:</u>
<pre>always @(*) begin   Y = 16'b0; // reset all outputs to 0   if (E) begin // only decode when enabled     case (A)       4'b0000: Y = 16'b0000_0000_0000_0001; //      output 0       4'b0001: Y = 16'b0000_0000_0000_0010;       4'b0010: Y = 16'b0000_0000_0000_0100;       4'b0011: Y = 16'b0000_0000_0000_1000;       4'b0100: Y = 16'b0000_0000_0001_0000;       4'b0101: Y = 16'b0000_0000_0010_0000;       4'b0110: Y = 16'b0000_0000_0100_0000;       4'b0111: Y = 16'b0000_0000_1000_0000;       4'b1000: Y = 16'b0000_0001_0000_0000;       4'b1001: Y = 16'b0000_0010_0000_0000;       4'b1010: Y = 16'b0000_0100_0000_0000;       4'b1011: Y = 16'b0000_1000_0000_0000;       4'b1100: Y = 16'b0001_0000_0000_0000;       4'b1101: Y = 16'b0010_0000_0000_0000;       4'b1110: Y = 16'b0100_0000_0000_0000;       4'b1111: Y = 16'b1000_0000_0000_0000;     endcase   end end</pre>	<pre>assign Y[0] = E &amp; ~A[3] &amp; ~A[2] &amp; ~A[1] &amp; ~A[0]; assign Y[1] = E &amp; ~A[3] &amp; ~A[2] &amp; ~A[1] &amp; A[0]; assign Y[2] = E &amp; ~A[3] &amp; ~A[2] &amp; A[1] &amp; ~A[0]; assign Y[3] = E &amp; ~A[3] &amp; ~A[2] &amp; A[1] &amp; A[0]; assign Y[4] = E &amp; ~A[3] &amp; A[2] &amp; ~A[1] &amp; ~A[0]; assign Y[5] = E &amp; ~A[3] &amp; A[2] &amp; ~A[1] &amp; A[0]; assign Y[6] = E &amp; ~A[3] &amp; A[2] &amp; A[1] &amp; ~A[0]; assign Y[7] = E &amp; ~A[3] &amp; A[2] &amp; A[1] &amp; A[0]; assign Y[8] = E &amp; A[3] &amp; ~A[2] &amp; ~A[1] &amp; ~A[0]; assign Y[9] = E &amp; A[3] &amp; ~A[2] &amp; ~A[1] &amp; A[0]; assign Y[10] = E &amp; A[3] &amp; ~A[2] &amp; A[1] &amp; ~A[0]; assign Y[11] = E &amp; A[3] &amp; ~A[2] &amp; A[1] &amp; A[0]; assign Y[12] = E &amp; A[3] &amp; A[2] &amp; ~A[1] &amp; ~A[0]; assign Y[13] = E &amp; A[3] &amp; A[2] &amp; ~A[1] &amp; A[0]; assign Y[14] = E &amp; A[3] &amp; A[2] &amp; A[1] &amp; ~A[0]; assign Y[15] = E &amp; A[3] &amp; A[2] &amp; A[1] &amp; A[0];</pre>

## Simulation:


### Testbench Description:

The testbench tb\_decoder4x16 is designed to verify the correct functionality of a 4-to-16 line decoder module (decoder4x16\_behav). The decoder takes a 4-bit input A, an enable signal E, and produces a 16-bit one-hot output Y.


- Enable = 1 (Active Phase):
  - When the enable signal E is asserted (E = 1), the testbench iterates through all 16 possible values of the 4-bit input A (from 0000 to 1111)
  - For each input value, it checks that the decoder output Y produces a one-hot encoding by comparing it to  $1 \ll A$

- If the output does not match, the simulation halts with a failure message; otherwise, a success message is displayed.
- Enable = 0 (Disabled Phase):
  - After verifying all valid inputs with the decoder enabled, the testbench disables the decoder by setting E = 0
  - It again iterates over all values of A to ensure that the output Y remains zero regardless of the input
  - Any non-zero output is treated as an error and flagged.

Sample Waveform:

 

Zoomed in to 3 periods:

 

## Implementation:

Resource Utilization Table

Resource	Used	Available	Utilization
LUTs	8	63,400	0.0126%
Registers (FFs)	0	126,800	0%
Bonded IOB	21	210	10%

Timing Summary:

Worst Negative Slack (WNS)	
Minimum Clock Period	
Max Frequency	

## Contributions:

Team Member	Contribution	% Effort
-------------	--------------	----------

Jonathan Huynh	Demo, Debugging, Synthesis, Simulation, Written Report	50%
Adam Godfrey	Verilog Code, Test Bench, Written Report	50%

## **Link To Video:**

<https://youtu.be/pE-wBqzjdYA>