

ECE 3300L.01 - Lab 7

Barrel Shifter & 7-Segment Display

Professor Mohamed Aly
Group Q: Kevin Tang(015429622) &
Jared Mocling(015215057)

August 6th, 2025

Design:

Barrel_shifter16.v

```
module barrel_shifter16(
    input wire [15:0] data_in,
    input wire [3:0] shamt,
    input wire dir,
    input wire rotate,
    output wire [15:0] data_out
);
    wire [15:0] s_stage1, s_stage2, s_stage3, s_stage4;

    // shift/rotate by 1
    assign s_stage1 = (shamt[0]) ?
        (rotate ? (dir ? {data_in[0], data_in[15:1]} : {data_in[14:0], data_in[15]}) :
            (dir ? {1'b0, data_in[15:1]} : {data_in[14:0], 1'b0})) :
        data_in;

    // shift/rotate by 2
    assign s_stage2 = (shamt[1]) ?
        (rotate ? (dir ? {s_stage1[1:0], s_stage1[15:2]} : {s_stage1[13:0], s_stage1[15:14]})
        :
            (dir ? {2'b00, s_stage1[15:2]} : {s_stage1[13:0], 2'b00})) :
        s_stage1;

    // shift/rotate by 4
    assign s_stage3 = (shamt[2]) ?
        (rotate ? (dir ? {s_stage2[3:0], s_stage2[15:4]} : {s_stage2[11:0], s_stage2[15:12]})
        :
            (dir ? {4'b0000, s_stage2[15:4]} : {s_stage2[11:0], 4'b0000})) :
        s_stage2;

    // shift/rotate by 8
    assign s_stage4 = (shamt[3]) ?
        (rotate ? (dir ? {s_stage3[7:0], s_stage3[15:8]} : {s_stage3[7:0], s_stage3[15:8]}) :
            (dir ? {8'b00000000, s_stage3[15:8]} : {s_stage3[7:0], 8'b00000000})) :
        s_stage3;

    assign data_out = s_stage4; // Final
    shifted/rotated result
endmodule
```

Clock_divider_fixed.v

```
module clock_divider_fixed(
    input clk,
    output reg clk_1khz,
    output reg clk_2khz
);
    parameter DIV_2HZ = 26'd25_000_000; // for 2Hz (toggle)
    parameter DIV_1KHZ = 17'd50_000; // for 1kHz

    reg [25:0] cnt_2hz = 0;
    reg [16:0] cnt_1khz = 0;

    always @(posedge clk) begin
        if (cnt_2hz == DIV_2HZ-1) begin
            cnt_2hz <= 0;
            clk_2khz <= ~clk_2khz;
        end else begin
            cnt_2hz <= cnt_2hz + 1;
        end
    end

    always @(posedge clk) begin
        if (cnt_1khz == DIV_1KHZ-1) begin
            cnt_1khz <= 0;
            clk_1khz <= ~clk_1khz;
        end else begin
            cnt_1khz <= cnt_1khz + 1;
        end
    end
endmodule
```

Debounce_toggle.v

```
module debounce_toggle(
    input wire clk_1khz,
    input wire btn_raw,
    output reg btn_toggle = 0
);

    reg [2:0] shift_reg = 3'b000;
    reg debounced = 0;
```

```

reg prev_debounced = 0;

always @(posedge clk_1khz) begin
    shift_reg <= {shift_reg[1:0], btn_raw};
    if (shift_reg == 3'b111)    // Debounced value = 1 if all 3 bits are high, 0 if all 3
bits are low
        debounced <= 1;
    else if (shift_reg == 3'b000)
        debounced <= 0;
    if (~prev_debounced && debounced)
        btn_toggle <= ~btn_toggle;

    prev_debounced <= debounced;    // Save previous debounced state
end
Endmodule

```

Hex_to_7seg.v

```

module hex_to_7seg(
    input wire [3:0] HEX,
    output reg [6:0] SEG
);
    always @(*) begin
        case (HEX)
            4'h0: SEG = 7'b1000000; // 0
            4'h1: SEG = 7'b1111001; // 1
            4'h2: SEG = 7'b0100100; // 2
            4'h3: SEG = 7'b0110000; // 3
            4'h4: SEG = 7'b0011001; // 4
            4'h5: SEG = 7'b0010010; // 5
            4'h6: SEG = 7'b0000010; // 6
            4'h7: SEG = 7'b1111000; // 7
            4'h8: SEG = 7'b0000000; // 8
            4'h9: SEG = 7'b0011000; // 9
            4'hA: SEG = 7'b0001000; // A
            4'hB: SEG = 7'b0000011; // b
            4'hC: SEG = 7'b1000110; // C
            4'hD: SEG = 7'b0100001; // d
            4'hE: SEG = 7'b0000110; // E
            4'hF: SEG = 7'b0001110; // F
            default: SEG = 7'b1111111; // Blank;
        endcase
    end
endmodule

```

```
        endcase
    end
endmodule
```

Shamt_count.v

```
`timescale 1ns / 1ps
```

```
module shamt_counter(
    input wire clk,
    input BTNC,
    output reg [1:0] shamt_hi
);

    reg btnc_last = 0;
    always @(posedge clk) begin
        btnc_last <= BTNC;
        if (BTNC & ~btnc_last)
            shamt_hi <= shamt_hi + 1;
    end
endmodule
```

Top_lab7.v

```
`timescale 1ns / 1ps
```

```
module top_lab7(
    input wire clk,
    input wire rst,
    input wire [15:0] SW,
    input wire BTNC, BTNU, BTND, BTNL, BTNR,
    output wire [7:0] AN,
    output wire [6:0] SEG,
    output wire [7:0] LED
);
    // Clock dividers
    wire clk_2khz, clk_1khz;
    clock_divider_fixed clkdiv(.clk(clk), .clk_2khz(clk_2khz), .clk_1khz(clk_1khz));

    // Debounce buttons to toggles
    wire dir, rot, sh0, sh1;
    debounce_toggle d0(.clk_1khz(clk_1khz), .btn_raw(BTNU), .btn_toggle(dir));
```

```

debounce_toggle d1(.clk_1khz(clk_1khz), .btn_raw(BTND), .btn_toggle(rot));
debounce_toggle d2(.clk_1khz(clk_1khz), .btn_raw(BTNL), .btn_toggle(sh1));
debounce_toggle d3(.clk_1khz(clk_1khz), .btn_raw(BTNR), .btn_toggle(sh0));

// Shift amount counter high bits
wire [1:0] shamt_hi;
shamt_counter sc(.clk(clk), .BTNC(BTNC), .shamt_hi(shamt_hi));

wire [3:0] shamt = {shamt_hi, sh1, sh0};

// Barrel shifter
wire [15:0] shifted;
barrel_shifter16 bs(.data_in(SW), .shamt(shamt), .dir(dir), .rotate(rot),
.data_out(shifted));

// 7-seg display
wire [6:0] seg0, seg1, seg2, seg3;
hex_to_7seg h0(.HEX(shifted[3:0]), .SEG(seg0));
hex_to_7seg h1(.HEX(shifted[7:4]), .SEG(seg1));
hex_to_7seg h2(.HEX(shifted[11:8]), .SEG(seg2));
hex_to_7seg h3(.HEX(shifted[15:12]), .SEG(seg3));

wire [6:0] blank = 7'b1111111;
seg7_scan8 scanner(
    .clk_1khz(clk_1khz),
    .seg0(seg0),
    .seg1(seg1),
    .seg2(seg2),
    .seg3(seg3),
    .seg4(blank),
    .seg5(blank),
    .seg6(blank),
    .seg7(blank),
    .AN(AN),
    .SEG(SEG)
);

assign LED[3:0] = shamt;
assign LED[4] = dir;
assign LED[5] = rot;

```

```
assign LED[7:6] = 2'b00;
```


```
endmodule
```

Testbench Waveform:


barrel_shifter16_tb



debounce_toggle_tb

 

seg7_scan8_tb

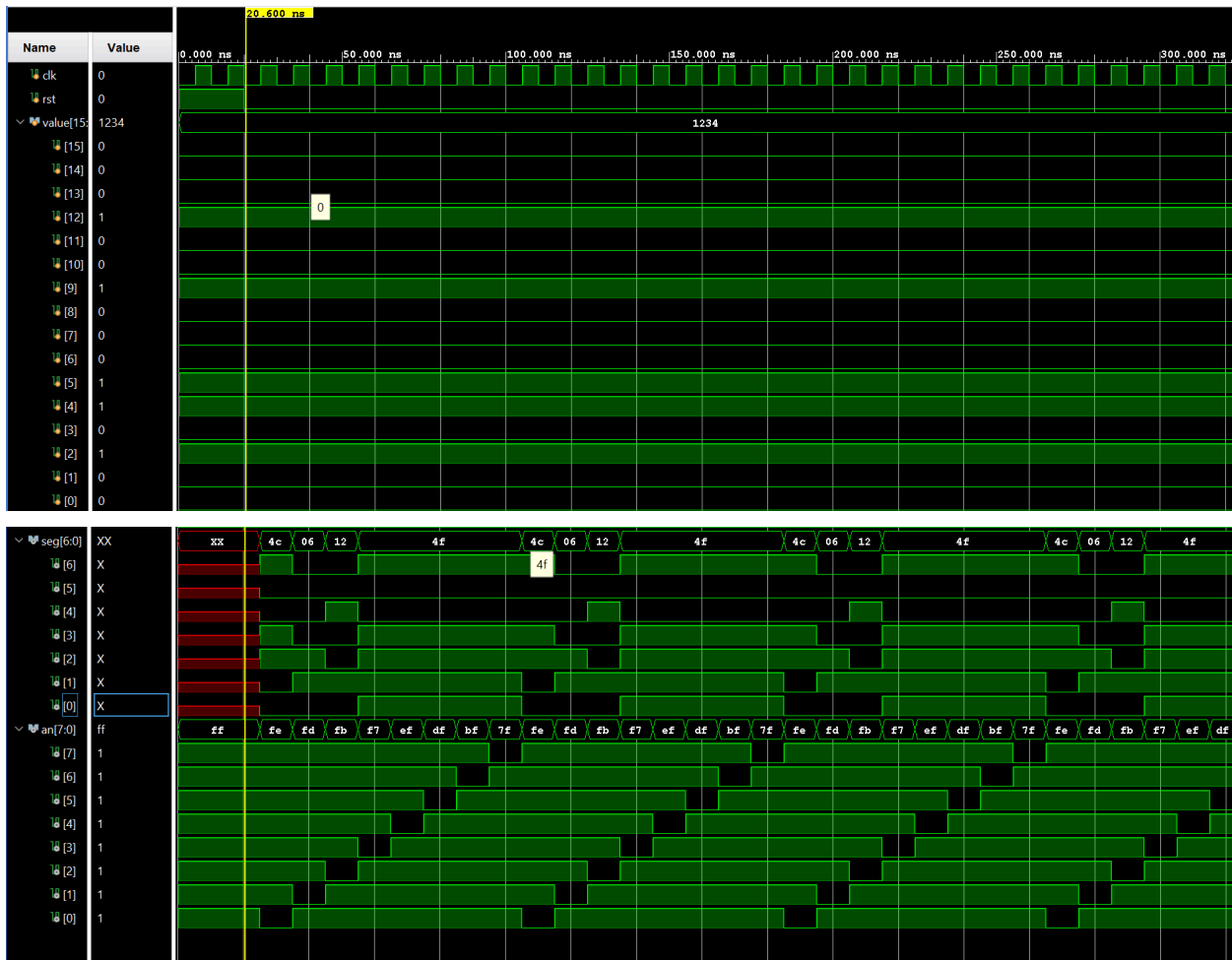

Utilization/Implementation:


Name	Slice LUTs (63400)	Slice Registers (126800)	F7 Muxes (31700)	Bonded IOB (210)	BUFGCTRL (32)
▼ N top_lab7	195	94	1	45	2
I sc (shamt_counter)	164	2	1	0	0

Power

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 0.1 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 25.5°C
 Thermal Margin: 59.5°C (12.9 W)
 Ambient Temperature: 25.0 °C
 Effective θ_{JA} : 4.6°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

Contributions:

Jared Mocling (50%) - testbench code, compiled code, Synthesis reports, report
 Kevin Tang (50%) - board demo, compiled code, report