

Lab 6 Report

by

Jonathan Huynh #016137719

Adam Godfrey #015981472

Instructor: Dr. Mohamed Aly

Class: ECE 3300L .E02-OU - Verilog Design

July 28th, 2025

Code with Explanation:

BCD Up/Down Counter on 7-Segment Display Top Module Code	
<pre>`timescale 1ns / 1ps module top_lab6 (input wire CLK, input wire BTN0, input wire [8:0] SW, output wire [6:0] SEG, output wire [7:0] AN, output wire [7:0] LED); wire [31:0] tick_bits; wire clk_div; wire [3:0] count_a; wire [3:0] count_b; wire [3:0] ctrl_nibble; wire [7:0] alu_output; clock_divider clk_div_inst (.base_clk(CLK), .reset_n(BTN0), .sel(SW[4:0]), .clk_div(clk_div), .tick_bits(tick_bits)); control_decoder ctrl_decoder_inst (.control_switches(SW[8:5]), .ctrl_nibble(ctrl_nibble)); bcd_counter counter_a (.clk_div(clk_div), .reset_n(BTN0), .count_up(SW[7]), .bcd_out(count_a)); bcd_counter counter_b (.clk_div(clk_div), .reset_n(BTN0), .count_up(SW[8]), .bcd_out(count_b)); alu alu_inst (.A_val(count_a), .B_val(count_b),</pre>	<p>We wrote this top-level Verilog module, <i>top_lab6</i>, to integrate several submodules into a cohesive digital system that runs on the Nexys A7 100T. The module accepts a clock input (CLK), a reset button (BTN0), and a set of switches (SW) to control the functionality. We coded this to demonstrate the interaction of clock division, control decoding, BCD counting, ALU operations, and 7-segment display scanning. Each submodule plays a specific role, and this top module wires them all together.</p> <p>We coded the <i>clock_divider</i> to scale down the input clock frequency based on user-selected settings via SW[4:0], producing a slower clock (clk_div) and a 32-bit tick pattern (tick_bits). This slower clock is used to drive two instances of <i>bcd_counter</i>, which we wrote to count up based on two different switch bits (SW[7] and SW[8]). Meanwhile, the <i>control_decoder</i> interprets bits SW[8:5] to generate a nibble (ctrl_nibble) for controlling the display and ALU behavior. We coded this to allow the user to dynamically adjust counting and display logic using switches.</p> <p>The alu module takes the outputs from the two BCD counters and performs a logic operation determined by SW[6:5], producing an 8-bit result that we send to the LEDs and the display. We wrote the <i>seg7_scan</i> module to show the high and low nibbles of this result on a two-digit 7-segment display, while</p>

<pre> .control_bits(SW[6:5]), .result_out(alu_output)); seg7_scan_display_inst (.clk_fast(CLK), .rst_n(BTN0), .lower_digit(alu_output[3:0]), .upper_digit(alu_output[7:4]), .ctrl_nibble(ctrl_nibble), .seg_pins(SEG), .dp(), .anodes(AN)); assign LED = alu_output; assign AN[7:3] = 5'b11111; endmodule </pre>	<p>keeping the other five digits disabled using AN[7:3] = 5'b11111. We coded this setup to give clear visual feedback on both the ALU computation and its control logic, making the system easy to test and demonstrate.</p>
--	---

<u>ALU</u>	
<pre> `timescale 1ns / 1ps module alu(input wire [3:0] A_val, input wire [3:0] B_val, input wire [1:0] control_bits, output reg [7:0] result_out); always @(*) begin case (control_bits) 2'b00: result_out = A_val + B_val; 2'b01: result_out = A_val - B_val; default: result_out = 8'd0; endcase end endmodule </pre>	<p>We coded this <i>alu</i> module to perform basic arithmetic between two 4-bit inputs, A_val and B_val, based on a 2-bit control signal. We wrote this because we needed a simple way to calculate either the sum or difference of two counters in our top-level design. The always @(*) block ensures the logic is purely combinational, updating the 8-bit result_out instantly based on the selected operation. Addition for 00, subtraction for 01, and zero for all other cases to keep the behavior predictable.</p>

BCD Up/Down Counter Code

```
`timescale 1ns / 1ps
module bcd_counter(
    input wire clk_div,
    input wire reset_n,
    input wire count_up,
    output reg [3:0] bcd_out
);
    always @(posedge clk_div or negedge
reset_n) begin
        if (!reset_n)
            bcd_out <= 0;
        else if (count_up)
            bcd_out <= (bcd_out == 9) ? 0 :
bcd_out + 1;
        else
            bcd_out <= (bcd_out == 0) ? 9 :
bcd_out - 1;
        end
    endmodule
```

We coded this *bcd_counter* module to produce a 4-bit decimal counter that counts up or down between 0 and 9 based on the **count_up** input. The counter updates on the rising edge of a divided clock and resets to zero when **reset_n** is low. We designed it to wrap from 9 to 0 when counting up, and from 0 to 9 when counting down, ensuring the output always stays within valid BCD range.

Clock Divider Code

```
`timescale 1ns / 1ps
module clock_divider(
    input wire base_clk,
    input wire reset_n,
    reset signal
    input wire [4:0] sel,
    output wire clk_div,
    output reg [31:0] tick_bits
);
    always @(posedge base_clk or negedge
reset_n) begin
        if (!reset_n)
            tick_bits <= 32'b0;
        else
            tick_bits <= tick_bits + 1;
        end
    assign clk_div = tick_bits[sel];
endmodule
```

We coded this *clock_divider* module to generate a slower, selectable clock signal (**clk_div**) by incrementing a 32-bit counter (**tick_bits**) on each pulse of the base clock. We wrote this because other modules in the system, like the counters and display, require a slower clock for proper operation and visibility. The **sel** input lets us choose which bit of the counter to output as the divided clock, allowing easy adjustment of speed. When **reset_n** is low, the counter resets to zero, ensuring consistent behavior on startup.

Control Decoder

```
`timescale 1ns / 1ps
module control_decoder(
    input wire [3:0] control_switches,
    output wire [3:0] ctrl_nibble
);
    assign ctrl_nibble = control_switches;
endmodule
```

We coded this *control_decoder* module to pass the 4-bit **control_switches** input directly to the **ctrl_nibble** output without modification. We wrote this because we needed a clean and modular way to route control signals, such as those for display formatting or operation selection, from external switches into other parts of the system.

7 Segment Code

```
`timescale 1ns / 1ps
module seg7_scan (
    input wire clk_fast,
    input wire rst_n,
    input wire [3:0] lower_digit,
    input wire [3:0] upper_digit,
    input wire [3:0] ctrl_nibble,
    output reg [6:0] seg_pins,
    output wire dp,
    output reg [2:0] anodes
);

    reg [15:0] refresh_counter = 0;
    reg [1:0] scan = 0;
    wire [3:0] current_digit;

    always @(posedge clk_fast) begin
        refresh_counter <= refresh_counter + 1;
    end

    always @(posedge refresh_counter[15])
begin
    scan <= scan + 1;
end

    assign current_digit = (scan == 2'd0) ?
lower_digit :
                        (scan == 2'd1) ? upper_digit
: ctrl_nibble;


    always @(*) begin
```

We coded this *seg7_scan* module to control a 3-digit 7-segment display by rapidly cycling through and displaying **lower_digit**, **upper_digit**, and **ctrl_nibble**. We wrote this because we needed a compact way to multiplex multiple digits on limited hardware, using time-division to refresh one digit at a time. A refresh counter and 2-bit scan register determine which digit to display and which anode to activate, while a case block maps each 4-bit value to its corresponding 7-segment LED pattern. This design lets us show three hexadecimal digits clearly with minimal wiring and efficient timing.


<pre> case (scan) 2'd0: anodes = 3'b110; 2'd1: anodes = 3'b101; 2'd2: anodes = 3'b011; default: anodes = 3'b111; endcase case (current_digit) 4'h0: seg_pins = 7'b1000000; 4'h1: seg_pins = 7'b1111001; 4'h2: seg_pins = 7'b0100100; 4'h3: seg_pins = 7'b0110000; 4'h4: seg_pins = 7'b0011001; 4'h5: seg_pins = 7'b0010010; 4'h6: seg_pins = 7'b0000010; 4'h7: seg_pins = 7'b1111000; 4'h8: seg_pins = 7'b0000000; 4'h9: seg_pins = 7'b0010000; 4'hA: seg_pins = 7'b0001000; 4'hb: seg_pins = 7'b0000011; 4'hC: seg_pins = 7'b1000110; 4'hd: seg_pins = 7'b0100001; 4'hE: seg_pins = 7'b0000110; 4'hF: seg_pins = 7'b0001110; default: seg_pins = 7'b1111111; endcase end endmodule </pre>	
---	--

Screenshot Proofs:

Resource Utilization Table:

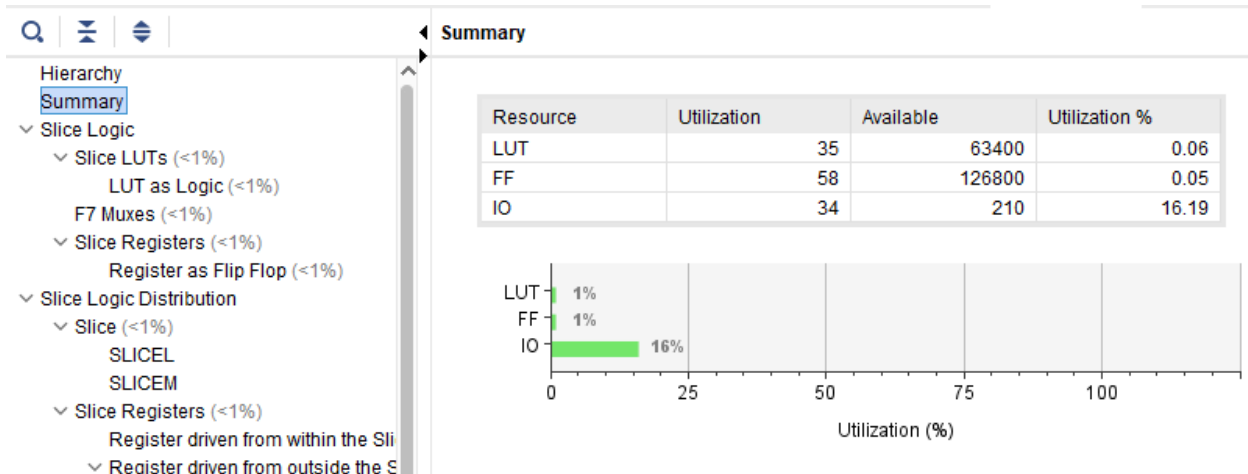

Power Utilization:

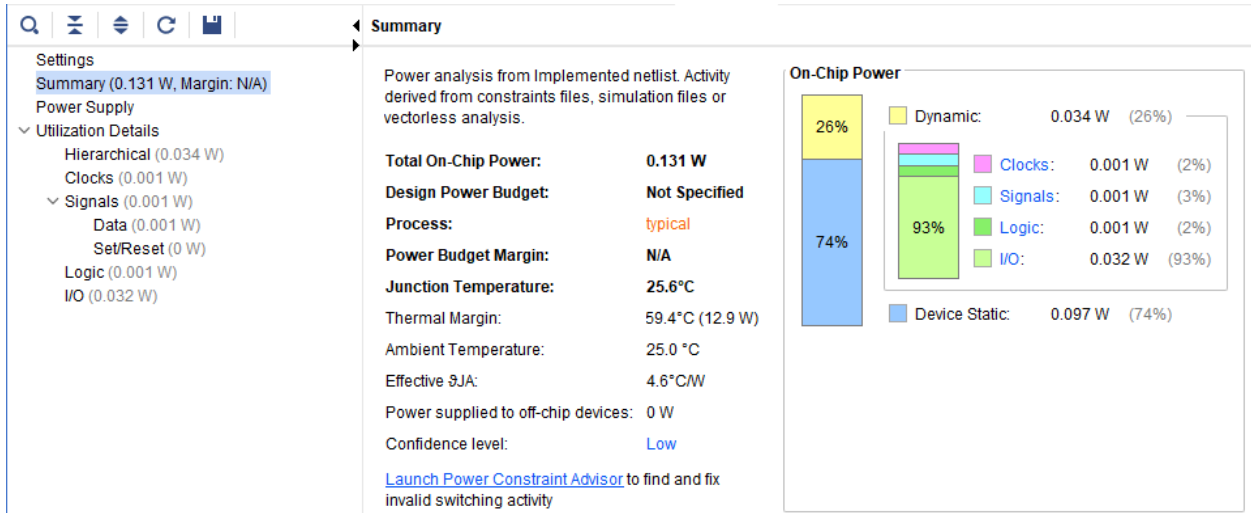

On-Chip Power

26%

74%

Dynamic: 0.034 W (26%)

93%

Device Static: 0.097 W (74%)


Clocks: 0.001 W (2%)

Signals: 0.001 W (3%)

Logic: 0.001 W (2%)

I/O: 0.032 W (93%)

Timing Summary:

 

Design Timing Summary

Setup

Hold

Pulse Width

Worst Negative Slack (WNS): 7.238 ns

Worst Hold Slack (WHS): 0.265 ns

Worst Pulse Width Slack (WPWS): 4.500 ns

Total Negative Slack (TNS): 0.000 ns

Total Hold Slack (THS): 0.000 ns

Total Pulse Width Negative Slack (TPWS): 0.000 ns

Number of Failing Endpoints: 0

Number of Failing Endpoints: 0

Number of Failing Endpoints: 0

Total Number of Endpoints: 48


Total Number of Endpoints: 48

Total Number of Endpoints: 49


All user specified timing constraints are met.

Simulation Waveforms:


Top Module

 


ALU

 


BCD Counter

 


Clock Divider

 

Control Decoder

 

7 Segment

 

Partner Contributions:

Team Member	Contribution	% Effort
Jonathan Huynh	Code: [Clock Divider, BCD Up/Down Counter, ALU] Testbench: [Top Module, ALU, Control Decoder] Additional: Synthesis/Implementation and Demo	50%
Adam Godfrey	Code: [7 Segment, Top Module, Control Decoder] Testbench: [7 Segment, BCD Up/Down, Clock Divider] Additional: Simulation and Lab Report	50%