



**CalPolyPomona**

---

College of  
Engineering

**California Polytechnic State University Pomona**

Department of Electrical & Computer Engineering

Digital Circuit Design Lab Verilog

ECE 3300L

Lab Report #6

Presented By: Kobe Aquino (StudentID: 015266433)

& Daniel Mondragon Xicotencatl (StudentID: 012803856)


Presented to Mohamed Aly

July 28, 2025

**Objective:** So this week we took last week's lab of a BCD counter of a 2 7-segment display and modified it so that we can see each 7-segment counting up/down independently using LED's. In addition, we made an ALU module that adds/subtracts these 2 values which was shown in the 7-segment displays in HEX (0-18). We also added a new control module that displayed what settings were active in a third 7-seg display. We mapped the constraints file to the specifications below.

Clock Divider: Use SW0–SW4 to slow down the 100 MHz clock for visible counting. Reset: BTN0 resets both counters to 0. Direction: SW7 & SW8 set up/down for each counter. ALU Operation: SW5 & SW6 select add or subtract. Display: Show result and control nibble on 7-seg; use LEDs for raw BCD debugging.

**Schematic:**

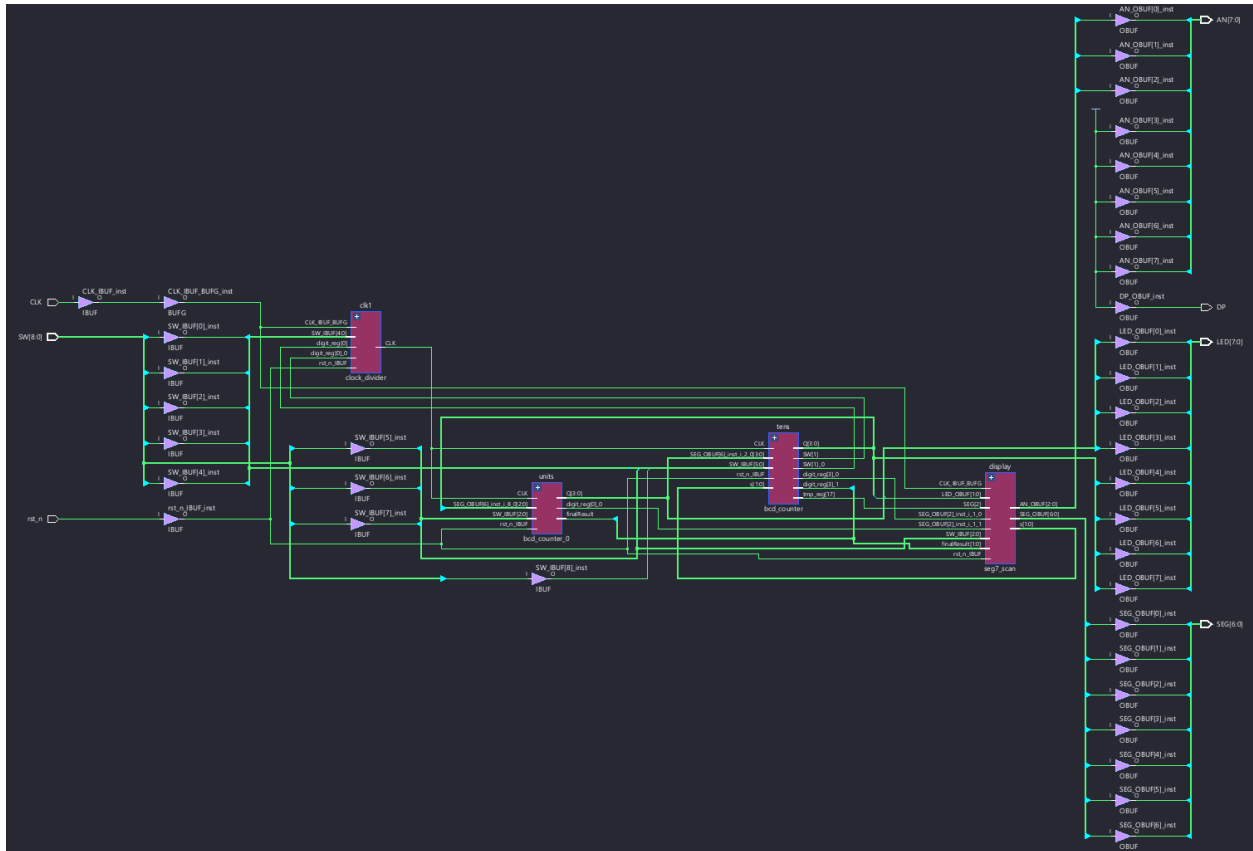


## Utilization:


Tcl Console	Messages	Log	Reports	Design Runs	Methodology	DRC	Power	Timing
Q								
<pre> +-----+-----+-----+-----+-----+   Site Type   Used   Fixed   Prohibited   Available   Util%   +-----+-----+-----+-----+-----+   Slice   22   0   0   15850   0.14     SLICEL   14   0              SLICEM   8   0              LUT as Logic   34   0   0   63400   0.05     using O5 output only   0                 using O6 output only   23                 using O5 and O6   11                 LUT as Memory   0   0   0   19000   0.00     LUT as Distributed RAM   0   0              using O5 output only   0                 using O6 output only   0                 using O5 and O6   0                 LUT as Shift Register   0   0              using O5 output only   0                 using O6 output only   0                 using O5 and O6   0                 Slice Registers   59   0   0   126800   0.05     Register driven from within the Slice   59                 Register driven from outside the Slice   0                 Unique Control Sets   2      0   15850   0.01   +-----+-----+-----+-----+-----+ * * Note: Available Control Sets calculated as Slice * 1, Review the Control Sets Report for more information regarding control sets. </pre>								

## Simulation:


clock\_divider\_tb

 


bcd\_counter\_tb

 


Control\_decoder\_tb

 

alu\_tb

 

## seg7\_scan\_tb

 

Team Contributions:

Daniel Mondragon Xicotencatl + 50%

Kobe Aquino + 50%

We both collaborated on the Verilog HDL by testing and modifying each other's modules, writing the test bench simulations together, and writing the report.