

**CALIFORNIA STATE POLYTECHNIC
UNIVERSITY, POMONA
COLLEGE OF ENGINEERING**

LAB 3

**16x1 Multiplexer Using Nested 2x1 MUXes
with Debounced Toggle Select Control**

ECE 3300L Summer 2025

Digital Circuit Design using Verilog

Professor Mohamed Aly

By: Clay Kim and Changwe Musonda

Objective

Our objective of this lab is to design and implement a 16-to-1 multiplexer (MUX16x1) using gate-level 2x1 multiplexers in Verilog. The multiplexer's select inputs will be controlled by pushbuttons on the Nexys A7 board, which will be converted into toggle switches through the implementation of a debouncing system and a toggle flip-flop for each select bit. The multiplexer's output will be displayed on LED0, with its 16 inputs driven by the 16 onboard switches (SW [15:0]).

MUX 2x1 Gate-Level Verilog

```
module mux2x1 (  
    input a, b,  
    input sel,  
    output y  
);  
    wire nsel, a1, b1;  
    not (nsel, sel);  
    and (a1, a, nsel);  
    and (b1, b, sel);  
    or (y, a1, b1);  
endmodule
```

Code given by instructor that creates a 2x1 multiplexer using not, and, or gates,

MUX 16x1 Using Generate Loops

```
module mux16x1 (  
    input [15:0] in,  
    input [3:0] sel,  
    output out  
);  
    wire [15:0] level1;  
    wire [7:0] level2;  
    wire [3:0] level3;  
    genvar i;  
    generate  
        for (i = 0; i < 8; i = i + 1)  
            mux2x1 m1 (.a(in[2*i]), .b(in[2*i+1]), .sel(sel[0]), .y(level1[i]));  
        for (i = 0; i < 4; i = i + 1)  
            mux2x1 m2 (.a(level1[2*i]), .b(level1[2*i+1]), .sel(sel[1]), .y(level2[i]));  
        for (i = 0; i < 2; i = i + 1)  
            mux2x1 m3 (.a(level2[2*i]), .b(level2[2*i+1]), .sel(sel[2]), .y(level3[i]));  
            mux2x1 m4 (.a(level3[0]), .b(level3[1]), .sel(sel[3]), .y(out));  
    endgenerate  
endmodule
```

Code given by instructor that uses multiple 2x1 multiplexer code to create a 16x1 multiplexer using for loops.

Debounce Module

```
module debounce (  
    input clk,  
    input btn_in,  
    output reg btn_clean  
);  
    reg [2:0] shift_reg;  
    always @(posedge clk) begin  
        shift_reg <= {shift_reg[1:0], btn_in};  
        if (shift_reg == 3'b111) btn_clean <= 1;  
        else if (shift_reg == 3'b000) btn_clean <= 0;  
    end  
endmodule
```

A module created in order to remove any bounces (basically filters out any inconsistent mechanical switch pulses)

Toggle Flip-Flop

```
module toggle_switch (  
    input clk,  
    input rst,  
    input btn_raw,  
    output reg state  
);  
    wire btn_clean;  
    reg btn_prev;  
    debounce db (.clk(clk), .btn_in(btn_raw), .btn_clean(btn_clean));  
    always @(posedge clk) begin  
        if (rst) begin  
            state <= 0;  
            btn_prev <= 0;  
        end else begin  
            if (btn_clean && !btn_prev)  
                state <= ~state;  
            btn_prev <= btn_clean;  
        end  
    end  
endmodule
```

This code takes the debounced signal and converts it into a toggling output. It “cleans” the raw button input and then uses a register to detect a rising edge and flips the value.

Top-Level Module

```
module top_mux_lab3 (  
    input clk,  
    input rst,  
    input [15:0] SW,  
    input btnU, btnD, btnL, btnR,  
    output LED0  
);  
    wire [3:0] sel;  
    toggle_switch t0 (.clk(clk), .rst(rst), .btn_raw(btnD), .state(sel[0]));  
    toggle_switch t1 (.clk(clk), .rst(rst), .btn_raw(btnR), .state(sel[1]));  
    toggle_switch t2 (.clk(clk), .rst(rst), .btn_raw(btnL), .state(sel[2]));  
    toggle_switch t3 (.clk(clk), .rst(rst), .btn_raw(btnU), .state(sel[3]));  
    mux16x1 mux (.in(SW), .sel(sel), .out(LED0));  
endmodule
```


Integrates all the different coded modules to work together.

Testbench code


```
module mux16x1_tb;  
    reg [15:0] in;  
    reg [3:0] sel;  
    wire out;  
    mux16x1 uut (.in(in), .sel(sel), .out(out));  
    initial begin  
        in = 16'b1010_0101_1100_0011;  
        for (sel = 0; sel < 16; sel = sel + 1) begin  
            #10;  
            $display("sel=%d, out=%b", sel, out);  
        end  
    $finish;  
end  
endmodule
```

Testbench code to initialize 16 data inputs and cycles through the values from 0 to 15 in the 16x1 MUX and prints the selected value and resulting the output of the MUX to the console.

Simulation Screenshot

 

Vivado Utilization

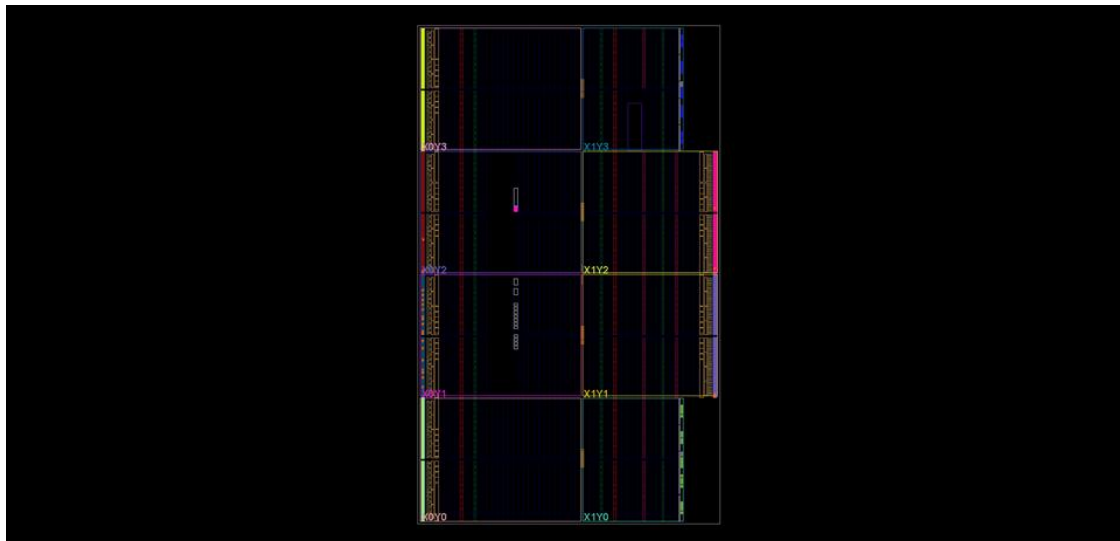

Utilization x

Q Hierarchy

Name	^1	Slice LUTs (63400)	Slice Registers (126800)	F7 Muxes (31700)	F8 Muxes (15850)	Bonded IOB (210)	BUFGCTRL (32)
top_mux_lab3		12	24	2	1	23	1
t0 (toggle_switch)		2	6	0	0	0	0
db (debounce_5)		2	4	0	0	0	0
t1 (toggle_switch_0)		6	6	2	1	0	0
db (debounce_4)		2	4	0	0	0	0
t2 (toggle_switch_1)		2	6	0	0	0	0
db (debounce_3)		2	4	0	0	0	0
t3 (toggle_switch_2)		2	6	0	0	0	0
db (debounce)		2	4	0	0	0	0

Power x Methodology DRC Timing Utilization

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.1 W

Design Power Budget: Not Specified

Process: typical

Power Budget Margin: N/A

Junction Temperature: 25.5°C

Thermal Margin: 59.5°C (12.9 W)

Ambient Temperature: 25.0 °C

Effective θ_{JA} : 4.6°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic: 0.003 W (3%)

- Clocks: 0.001 W (17%)
- Signals: <0.001 W (6%)
- Logic: <0.001 W (2%)
- I/O: 0.002 W (75%)

Device Static: 0.097 W (97%)

Partner Contribution

Clay Kim: Testbench and Simulation

Changwe Musonda: Demonstration video and implementation