

# ECE3300L Lab 3

## 16x1 Multiplexer Using Nested 2x1 MUXes with Debounced Toggle Select Control

Group X

Czyrone Agbayani (BID: 014766336)

Caleb Jala-Guinto (BID: 015446587)

## Objective:

The objective of this lab is to design and implement a 16-to-1 multiplexer (MUX16x1) on the Nexys A7 FPGA board using gate-level 2-to-1 multiplexers in Verilog. The multiplexer selects one of 16 switch inputs (SW[15:0]) to be displayed on a single LED (LED0), based on a 4-bit select signal. Instead of using simple switches for the select lines, the lab introduces the use of pushbuttons with toggle behavior. To make this possible, students must implement a debouncing system to filter out signal noise and a toggle flip-flop to store each select bit. This lab provides hands-on experience with building hierarchical digital circuits, managing mechanical input issues, and applying real-time logic on FPGA hardware.

## MUX2x1 Gate-Level Verilog:

```
1 module mux2x1 (  
2     input a, b,  
3     input sel,  
4     output y  
5 );  
6     wire nsel, al, bl;  
7     not (nsel, sel);  
8     and (al, a, nsel);  
9     and (bl, b, sel);  
10    or (y, al, bl);  
11 endmodule
```

This is a simple MUX2x1 module. If sel is high, the output is the state of b, but if sel is low, the output is the state of a. This will help later with making the MUX16x1

## MUX16x1 Using Generate Loops:

```
23 module mux16x1(  
24     input [15:0] in,  
25     input [3:0] sel,  
26     output out  
27 );  
28     wire [15:0] level1;  
29     wire [7:0] level2;  
30     wire [3:0] level3;  
31  
32     genvar i;  
33     generate  
34         for (i = 0; i < 8; i = i + 1)  
35             mux2x1 m1 (.a(in[2*i]), .b(in[2*i+1]), .sel(sel[0]), .y(level1[i]));  
36  
37         for (i = 0; i < 4; i = i + 1)  
38             mux2x1 m2 (.a(level1[2*i]), .b(level1[2*i+1]), .sel(sel[1]), .y(level2[i]));  
39  
40         for (i = 0; i < 2; i = i + 1)  
41             mux2x1 m3 (.a(level2[2*i]), .b(level2[2*i+1]), .sel(sel[2]), .y(level3[i]));  
42  
43         mux2x1 m4 (.a(level3[0]), .b(level3[1]), .sel(sel[3]), .y(out));  
44     endgenerate  
45 endmodule
```

This module uses eight 2x1 MUXes to make a 16x1 MUX. It uses the 2x1 MUXes to select the different levels of bits. It starts by using eight MUXes to connect to four MUXes, then those four MUXes connect to two MUXes, and finally those two MUXes connect to one MUX, which determines the output of the 16x1 MUX. This process is seen through the generate block and the for loops.

### Debounce Module:

```
23 module debounce (  
24     input clk,  
25     input btn_in,  
26     output reg btn_clean  
27 );  
28     reg [2:0] shift_reg;  
29  
30 always @(posedge clk) begin  
31     shift_reg <= {shift_reg[1:0], btn_in};  
32     if (shift_reg == 3'b111) btn_clean <= 1;  
33     else if (shift_reg == 3'b000) btn_clean <= 0;  
34 end  
35 endmodule
```

This module helps prevent the buttons from jumping from high to low too many times. This module works by making sure the button is high for at least three clock cycles before outputting the signal on the next clock cycle. This goes the same when the button is low.

### Toggle Flip-Flop:

```
--  
23 module toggle_switch (  
24     input clk,  
25     input rst,  
26     input btn_raw,  
27     output reg state  
28 );  
29     wire btn_clean;  
30     reg btn_prev;  
31  
32     debounce db (.clk(clk), .btn_in(btn_raw), .btn_clean(btn_clean));  
33  
34 always @(posedge clk) begin  
35     if (rst) begin  
36         state <= 0;  
37         btn_prev <= 0;  
38     end else begin  
39         if (btn_clean && !btn_prev)  
40             state <= ~state;  
41         btn_prev <= btn_clean;  
42     end  
43 end  
44 endmodule
```

This module uses the debounce module to make sure that there are no unintentional triggers. This works by having the state of the toggle switch when it gets a clean signal from the button. There are also parameters in the code to make sure it isn't constantly switching states whenever the button is held down.

### Top-Level Module:

```
23 module top_mux_lab3 (  
24     input clk,  
25     input rst,  
26     input [15:0] SW,  
27     input btnU, btnD, btnL, btnR,  
28     output LED0  
29 );  
30     wire [3:0] sel;  
31  
32     toggle_switch t0 (.clk(clk), .rst(rst), .btn_raw(btnD), .state(sel[0]));  
33     toggle_switch t1 (.clk(clk), .rst(rst), .btn_raw(btnR), .state(sel[1]));  
34     toggle_switch t2 (.clk(clk), .rst(rst), .btn_raw(btnL), .state(sel[2]));  
35     toggle_switch t3 (.clk(clk), .rst(rst), .btn_raw(btnU), .state(sel[3]));  
36  
37     mux16x1 mux (.in(SW), .sel(sel), .out(LED0));  
38 endmodule
```

This module implements a toggle\_switch method on each button used. The buttons are used to communicate each bit in our select. Their outputs are connected to the MUX16x1, which are connected to the sixteen data inputs to the switches. This then outputs onto LED0.

## XDC file:


```

6  # Clock signal
7  set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 } [get_ports { clk }]; #IO_L12P_T1_MRCC_35 Sch=clk100mhz
8  create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {clk}];

11 ##Switches
12
13 set_property -dict { PACKAGE_PIN J15      IOSTANDARD LVCMOS33 } [get_ports { SW[0] }]; #IO_L24N_T3_R50_15 Sch=sw[0]
14 set_property -dict { PACKAGE_PIN L16      IOSTANDARD LVCMOS33 } [get_ports { SW[1] }]; #IO_L3N_T0_DQS_EMCCLK_14 Sch=sw[1]
15 set_property -dict { PACKAGE_PIN M13      IOSTANDARD LVCMOS33 } [get_ports { SW[2] }]; #IO_L6N_T0_D08_VREF_14 Sch=sw[2]
16 set_property -dict { PACKAGE_PIN R15      IOSTANDARD LVCMOS33 } [get_ports { SW[3] }]; #IO_L13N_T2_MRCC_14 Sch=sw[3]
17 set_property -dict { PACKAGE_PIN R17      IOSTANDARD LVCMOS33 } [get_ports { SW[4] }]; #IO_L12N_T1_MRCC_14 Sch=sw[4]
18 set_property -dict { PACKAGE_PIN T18      IOSTANDARD LVCMOS33 } [get_ports { SW[5] }]; #IO_L7N_T1_D10_14 Sch=sw[5]
19 set_property -dict { PACKAGE_PIN U18      IOSTANDARD LVCMOS33 } [get_ports { SW[6] }]; #IO_L17N_T2_A13_D29_14 Sch=sw[6]
20 set_property -dict { PACKAGE_PIN R13      IOSTANDARD LVCMOS33 } [get_ports { SW[7] }]; #IO_L5N_T0_D07_14 Sch=sw[7]
21 set_property -dict { PACKAGE_PIN T8       IOSTANDARD LVCMOS18 } [get_ports { SW[8] }]; #IO_L24N_T3_34 Sch=sw[8]
22 set_property -dict { PACKAGE_PIN U8       IOSTANDARD LVCMOS18 } [get_ports { SW[9] }]; #IO_25_34 Sch=sw[9]
23 set_property -dict { PACKAGE_PIN R16      IOSTANDARD LVCMOS33 } [get_ports { SW[10] }]; #IO_L15P_T2_DQS_RDWR_B_14 Sch=sw[10]
24 set_property -dict { PACKAGE_PIN T13      IOSTANDARD LVCMOS33 } [get_ports { SW[11] }]; #IO_L23P_T3_A03_D19_14 Sch=sw[11]
25 set_property -dict { PACKAGE_PIN H6       IOSTANDARD LVCMOS33 } [get_ports { SW[12] }]; #IO_L24P_T3_35 Sch=sw[12]
26 set_property -dict { PACKAGE_PIN U12      IOSTANDARD LVCMOS33 } [get_ports { SW[13] }]; #IO_L20P_T3_A08_D24_14 Sch=sw[13]
27 set_property -dict { PACKAGE_PIN U11      IOSTANDARD LVCMOS33 } [get_ports { SW[14] }]; #IO_L19N_T3_A09_D25_VREF_14 Sch=sw[14]
28 set_property -dict { PACKAGE_PIN V10      IOSTANDARD LVCMOS33 } [get_ports { SW[15] }]; #IO_L21P_T3_DQS_14 Sch=sw[15]
29
30
31 ## LEDs
32
33 set_property -dict { PACKAGE_PIN H17      IOSTANDARD LVCMOS33 } [get_ports { LED0 }]; #IO_L18P_T2_A24_15 Sch=led[0]
34
35 ##Buttons
36
37 #set_property -dict { PACKAGE_PIN C12      IOSTANDARD LVCMOS33 } [get_ports { CPU_RESETN }]; #IO_L3P_T0_DQS_AD1P_15 Sch=cpu_resetrn
38
39 set_property -dict { PACKAGE_PIN N17      IOSTANDARD LVCMOS33 } [get_ports { rst }]; #IO_L9P_T1_DQS_14 Sch=btnc
40 set_property -dict { PACKAGE_PIN M18      IOSTANDARD LVCMOS33 } [get_ports { btnU }]; #IO_L4N_T0_D05_14 Sch=btneu
41 set_property -dict { PACKAGE_PIN P17      IOSTANDARD LVCMOS33 } [get_ports { btnL }]; #IO_L12P_T1_MRCC_14 Sch=btlnl
42 set_property -dict { PACKAGE_PIN M17      IOSTANDARD LVCMOS33 } [get_ports { btnR }]; #IO_L10N_T1_D15_14 Sch=btlnr
43 set_property -dict { PACKAGE_PIN P18      IOSTANDARD LVCMOS33 } [get_ports { btnD }]; #IO_L9N_T1_DQS_D13_14 Sch=btnd

```

## Test Bench:

 

**Video Link:**

<https://youtube.com/shorts/7H1bLrLX0Xw>

**Contributions:**

Czyrone (50%) - Physical Demo, Debugging Code

Caleb (50%) - Debugging Code and Explaining Coding Process

Both worked on the lab report together and troubleshooted code

**Reflections:**

In this lab, a 16-to-1 multiplexer was built using gate-level 2-to-1 multiplexers in Verilog and controlled by the push buttons on the Nexys A7 FPGA board. To make the push buttons behave like toggle switches, a debouncing system and a toggle flip-flop were implemented for each select bit. This allowed each button press to reliably change the value of one of the four select bits, which controlled which of the 16 switches was routed to the output. The selected input value was displayed in real time on LED0. By combining digital design with input filtering and state-based control, this lab demonstrated how to manage noisy mechanical signals and implement clean, user-driven selection logic using hardware description language and FPGA tools.