

LAB 3
Switches to turn on LEDs on FPGA board
By Nicholas Williams and Faris Khan
ECE3300
7/2//2025

Introduction

In this lab we were tasked to create a 16 x 1 multiplexer using gate-level 2x1 multiplexer in verilog. The method we used to give our inputs came from our buttons which functioned as toggle switches. 4 buttons made a 4 digit binary number which could get 0 to 15 values. This allowed us to give the input to the 16 x 1 multiplexer. We also had to use the debouncing function due to when a button is pressed it is counted more than once for a few milliseconds which isn't what we want for this lab.

Mux2x1 Module:

```
module mux2x1 (  
    input a, b,  
    input sel,  
    output y  
);  
    wire nsel, al, bl;  
    not (nsel, sel);  
    and (al, a, nsel);  
    and (bl, b, sel);  
    or (y, al, bl);  
endmodule
```

Code provided by the professor which defines the logic of our nested 2x1 muxes.

Debounce Module:

```
module debounce (  
    input clk,  
    input btn_in,  
    output reg btn_clean  
);  
    reg [2:0] shift_reg;  
    always @(posedge clk) begin  
        shift_reg <= {shift_reg[1:0], btn_in};  
        if (shift_reg == 3'b111) btn_clean <= 1;  
        else if (shift_reg == 3'b000) btn_clean <= 0;  
    end  
endmodule
```

In order to filter the signals to get rid of any unnecessary triggers we implement a debounce module for this. Code provided by the professor.

16x1 Mux Module:

```
module mux16x1 (
    input [15:0] in,
    input [3:0] sel,
    output out
);
    wire [15:0] level1;
    wire [7:0] level2;
    wire [3:0] level3;
    genvar i;
    generate
        for (i = 0; i < 8; i = i + 1)
            mux2x1 m1 (.a(in[2*i]), .b(in[2*i+1]), .sel(sel[0]), .y(level1[i]));
        for (i = 0; i < 4; i = i + 1)
            mux2x1 m2 (.a(level1[2*i]), .b(level1[2*i+1]), .sel(sel[1]), .y(level2[i]));
        for (i = 0; i < 2; i = i + 1)
            mux2x1 m3 (.a(level2[2*i]), .b(level2[2*i+1]), .sel(sel[2]), .y(level3[i]));
            mux2x1 m4 (.a(level3[0]), .b(level3[1]), .sel(sel[3]), .y(out));
    endgenerate
endmodule
```

Code for the 16x1 mux provided by the professor. Defines a multiplexer with 16 inputs and 4 select bits with the nested 2x1 muxes.

Toggle_switch Module:

```
module toggle_switch (
    input clk,
    input rst,
    input btn_raw,
    output reg state
);
    wire btn_clean;
    reg btn_prev;
    debounce db (.clk(clk), .btn_in(btn_raw), .btn_clean(btn_clean));
    always @(posedge clk) begin
        if (rst) begin
            state <= 0;
            btn_prev <= 0;
        end else begin
            if (btn_clean && !btn_prev)
                state <= ~state;
            btn_prev <= btn_clean;
        end
    end
endmodule
```



The `toggle_switch` module implements flipping the output state each time a button is pressed. It uses a `debounce` module to filter out noise from the raw button input (`btn_raw`). The logic detects a rising edge on the clean signal (`btn_clean`) to trigger the toggle. On reset, the state is initialized to 0, and the button press history is cleared.

Top-level Mux Module:


```
module top_mux_lab3 (  
    input clk,  
    input rst,  
    input [15:0] sw,  
    input btnU, btnD, btnL, btnR,  
    output LED0  
);  
    wire [3:0] sel;  
  
    toggle_switch t0 (.clk(clk), .rst(rst), .btn_raw(btnD), .state(sel[0]));  
    toggle_switch t1 (.clk(clk), .rst(rst), .btn_raw(btnR), .state(sel[1]));  
    toggle_switch t2 (.clk(clk), .rst(rst), .btn_raw(btnL), .state(sel[2]));  
    toggle_switch t3 (.clk(clk), .rst(rst), .btn_raw(btnU), .state(sel[3]));  
  
    mux16x1 mux (.in(sw), .sel(sel), .out(LED0));  
endmodule
```

The `top_mux_lab3` module integrates four `toggle_switch` instances to control the 4-bit select input `sel` of a `mux16x1`. Each push-button is wired to a toggle switch, which toggles one of the bits of `sel[3:0]`. The 16-bit input `sw` is passed into the multiplexer, and the selected bit (based on `sel`) is output to `LED0`. This design lets you manually select one of the 16 inputs using debounced toggle buttons to choose the selector bits.

Data

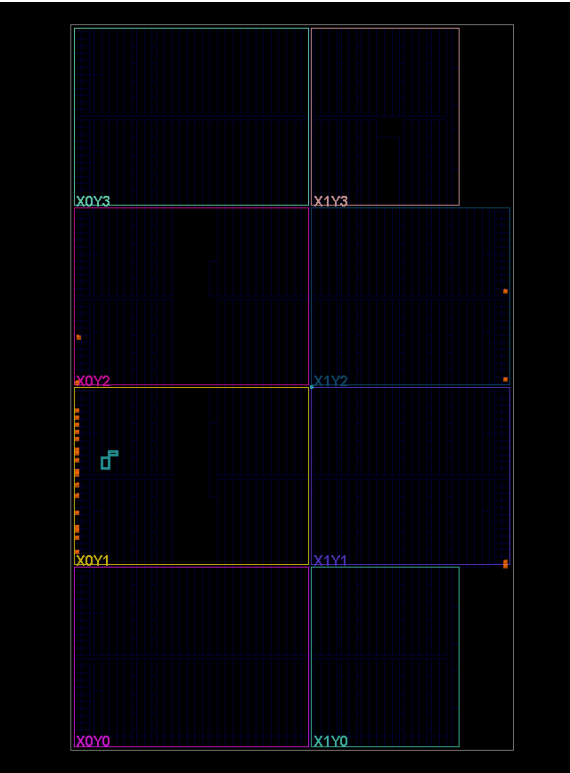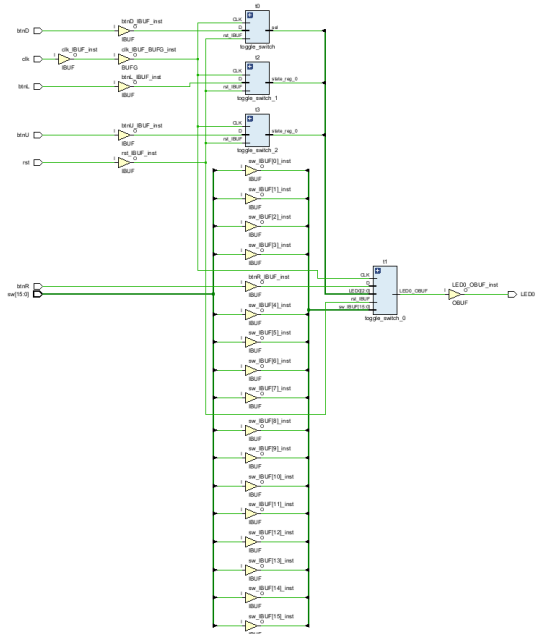

| Name | Slice LUTs (63400) | Slice Registers (126800) | F7 Muxes (31700) | F8 Muxes (15850) | Slice (15850) | LUT as Logic (63400) | Bonded IOB (210) | BUFGCTRL (32) |
|--------------|-----------------------|-----------------------------|---------------------|---------------------|------------------|-------------------------|---------------------|------------------|
| top_mux_lab3 | 12 | 24 | 2 | 1 | 6 | 12 | 23 | 1 |

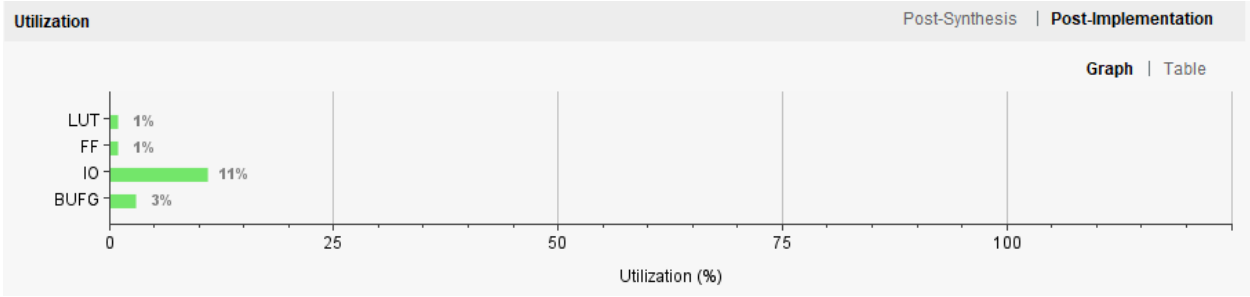

Data Analysis

Testbench

```
1  `timescale 1ns / 1ps
2
3  module tb_mux16x1;
4
5      // Inputs
6      reg [15:0] in;
7      reg [3:0] sel;
8
9      // Output
10     wire out;
11
12     // Instantiate the Unit Under Test (UUT)
13     mux16x1 uut (
14         .in(in),
15         .sel(sel),
16         .out(out)
17     );
18
19     integer i;
20
21     initial begin
22         // Set a fixed test pattern
23         in = 16'b1010110000110101;
24         $display("Input: %b", in);
25         $display("sel\t in[sel]\t out");
26
27         // Test all selection values
28         for (i = 0; i < 16; i = i + 1) begin
29             sel = i;
30             #10;
31             if (out == 1'b1) begin
32                 $display("%2d\t %b\t\t %b <-- PASS", sel, in[sel], out);
33             end
34         end
35
36         $display("Test complete.");
37     end
38
39 endmodule
```

In this an input is defined and we are comparing each bit of the value. Based on the position of the 1s, it will output: the select bit, the value at the select indice, and the output of the led which will be 1 if it passes.

```

Input: 1010110000110101
sel  in[sel]    out
  0      1      1 <-- PASS
  2      1      1 <-- PASS
  4      1      1 <-- PASS
  5      1      1 <-- PASS
 10      1      1 <-- PASS
 11      1      1 <-- PASS
 13      1      1 <-- PASS
 15      1      1 <-- PASS
Test complete.

```

Here is the screenshot of the output.



Here is the waveform screenshot.

Conclusion

In this lab we made a working 16x1 multiplexer using 2x1 multiplexers in verilog which combined to make one big 16x1 multiplexer. The switches ran whether the input was hi or low and the led was the output which showed the hi or low status. We used the debouncing function to be able to use the switches to drive the 4 bit selector for the 16x1 mux. In this lab

Contributions

Nicholas Williams- 50% uploaded youtube video, helped make the Testbench file, showed demo, introduction on lab report and conclusion, help with data screenshots.

Faris Khan- 50% Worked mainly on the testbench file with the simulations, included the screenshots of the code and added explanations for each of them.