

# 4x16 Decoder Design on Nexys A7-100T FPGA

3300L

Dia Agrawal and Robert Lainez Torres

## Objective

The objective of this lab is to implement a 4-16 decoder with an enable input. We will put to practice gate-level coding, behavioral coding, self-checking testbench, understanding what resource utilization reports mean, and documentation.

## Hardware Connections

Hardware connections are controlled via the constraint file which is shown below.

```
## Decoder Inputs (A[3:0])
set_property -dict { PACKAGE_PIN J15 IOSTANDARD LVCMOS33 } [get_ports { A[0] }]; # SW[0]
set_property -dict { PACKAGE_PIN L16 IOSTANDARD LVCMOS33 } [get_ports { A[1] }]; # SW[1]
set_property -dict { PACKAGE_PIN M13 IOSTANDARD LVCMOS33 } [get_ports { A[2] }]; # SW[2]
set_property -dict { PACKAGE_PIN R15 IOSTANDARD LVCMOS33 } [get_ports { A[3] }]; # SW[3]

## Decoder Enable (E)
set_property -dict { PACKAGE_PIN R17 IOSTANDARD LVCMOS33 } [get_ports { E }]; # SW[4]

## Decoder Outputs (Y[15:0])
set_property -dict { PACKAGE_PIN H17 IOSTANDARD LVCMOS33 } [get_ports { Y[0] }]; # LED[0]
set_property -dict { PACKAGE_PIN K15 IOSTANDARD LVCMOS33 } [get_ports { Y[1] }]; # LED[1]
set_property -dict { PACKAGE_PIN J13 IOSTANDARD LVCMOS33 } [get_ports { Y[2] }]; # LED[2]
set_property -dict { PACKAGE_PIN N14 IOSTANDARD LVCMOS33 } [get_ports { Y[3] }]; # LED[3]
set_property -dict { PACKAGE_PIN R18 IOSTANDARD LVCMOS33 } [get_ports { Y[4] }]; # LED[4]
set_property -dict { PACKAGE_PIN V17 IOSTANDARD LVCMOS33 } [get_ports { Y[5] }]; # LED[5]
set_property -dict { PACKAGE_PIN U17 IOSTANDARD LVCMOS33 } [get_ports { Y[6] }]; # LED[6]
set_property -dict { PACKAGE_PIN U16 IOSTANDARD LVCMOS33 } [get_ports { Y[7] }]; # LED[7]
set_property -dict { PACKAGE_PIN V16 IOSTANDARD LVCMOS33 } [get_ports { Y[8] }]; # LED[8]
set_property -dict { PACKAGE_PIN T15 IOSTANDARD LVCMOS33 } [get_ports { Y[9] }]; # LED[9]
set_property -dict { PACKAGE_PIN U14 IOSTANDARD LVCMOS33 } [get_ports { Y[10] }]; # LED[10]
set_property -dict { PACKAGE_PIN T16 IOSTANDARD LVCMOS33 } [get_ports { Y[11] }]; # LED[11]
set_property -dict { PACKAGE_PIN V15 IOSTANDARD LVCMOS33 } [get_ports { Y[12] }]; # LED[12]
set_property -dict { PACKAGE_PIN V14 IOSTANDARD LVCMOS33 } [get_ports { Y[13] }]; # LED[13]
set_property -dict { PACKAGE_PIN V12 IOSTANDARD LVCMOS33 } [get_ports { Y[14] }]; # LED[14]
set_property -dict { PACKAGE_PIN V11 IOSTANDARD LVCMOS33 } [get_ports { Y[15] }]; # LED[15]
```

In the image above, we show the decoder inputs as SW[0], SW[1], SW[2] and, SW[3] and the output as LEDs 0 to 15 (16-bit output)

## Gate-Level and Behavioral implementation:

The gate level implementation shows the logic using gates to express the logic whereas the behavioral implementation shows this expressed directly in binary form.

## Test-Bench:

The testbench cycles through all 16 possible input values twice — once with enable off to verify zero output, and once with enable on to confirm one-hot decoding. I used a task to check the gate and behavioral outputs against expected values at every step.

## Gate-Level implementation

```
module decoder4x16_gate(  
    input [3:0] A,      // [BLUE]  
    input E,           // [BLUE]  
    output [15:0] Y     // [GREEN]  
);  
  
//assigning output values  
  
// Enable LOW  
assign Y[0] = E & ~A[3] & ~A[2] & ~A[1] & ~A[0]; // [GREEN]  
assign Y[1] = E & ~A[3] & ~A[2] & ~A[1] & A[0]; // [GREEN]  
assign Y[2] = E & ~A[3] & ~A[2] & A[1] & ~A[0]; // [GREEN]  
assign Y[3] = E & ~A[3] & ~A[2] & A[1] & A[0]; // [GREEN]  
assign Y[4] = E & ~A[3] & A[2] & ~A[1] & ~A[0]; // [GREEN]  
assign Y[5] = E & ~A[3] & A[2] & ~A[1] & A[0]; // [GREEN]  
assign Y[6] = E & ~A[3] & A[2] & A[1] & ~A[0]; // [GREEN]  
assign Y[7] = E & ~A[3] & A[2] & A[1] & A[0]; // [GREEN]  
  
// Enable HIGH  
assign Y[8] = E & A[3] & ~A[2] & ~A[1] & ~A[0]; // [GREEN]  
assign Y[9] = E & A[3] & ~A[2] & ~A[1] & A[0]; // [GREEN]  
assign Y[10] = E & A[3] & ~A[2] & A[1] & ~A[0]; // [GREEN]  
assign Y[11] = E & A[3] & ~A[2] & A[1] & A[0]; // [GREEN]  
assign Y[12] = E & A[3] & A[2] & ~A[1] & ~A[0]; // [GREEN]  
assign Y[13] = E & A[3] & A[2] & ~A[1] & A[0]; // [GREEN]  
assign Y[14] = E & A[3] & A[2] & A[1] & ~A[0]; // [GREEN]  
assign Y[15] = E & A[3] & A[2] & A[1] & A[0]; // [GREEN]  
endmodule
```

## Behavioral Implementation

```
module decoder4x16_behav(  
    input [3:0] A,      // [BLUE] Input Address  
    input E,           // [BLUE] Enable Signal  
    output reg [15:0] Y // [GREEN] Output  
);  
  
always @(*) begin // [ORANGE]  
    Y = 16'b0; // [ORANGE]  
    if (E) begin // [ORANGE]  
        case (A)  
            4'b0000: Y = 16'b0000000000000001; //  
            4'b0001: Y = 16'b0000000000000010;  
            4'b0010: Y = 16'b0000000000000100;  
            4'b0011: Y = 16'b00000000000001000;  
            4'b0100: Y = 16'b0000000000010000;  
            4'b0101: Y = 16'b0000000000100000;  
            4'b0110: Y = 16'b0000000001000000;  
            4'b0111: Y = 16'b0000000010000000;  
            4'b1000: Y = 16'b0000000100000000;  
            4'b1001: Y = 16'b0000001000000000;  
            4'b1010: Y = 16'b0000010000000000;  
            4'b1011: Y = 16'b0000100000000000;  
            4'b1100: Y = 16'b0001000000000000;  
            4'b1101: Y = 16'b0010000000000000;  
            4'b1110: Y = 16'b0100000000000000;  
            4'b1111: Y = 16'b1000000000000000;  
        endcase // [ORANGE]  
    end  
end  
endmodule
```

$\pi$  J

```
# run 1000ns
starting 4-to-16 decoder testbench..
PASS GATE: E=0 A=0000 Y=000000000000000000
PASS BEHAV: E=0 A=0000 Y=000000000000000000
PASS GATE: E=0 A=0001 Y=000000000000000000
PASS BEHAV: E=0 A=0001 Y=000000000000000000
PASS GATE: E=0 A=0010 Y=000000000000000000
PASS BEHAV: E=0 A=0010 Y=000000000000000000
PASS GATE: E=0 A=0011 Y=000000000000000000
PASS BEHAV: E=0 A=0011 Y=000000000000000000
PASS GATE: E=0 A=0100 Y=000000000000000000
PASS BEHAV: E=0 A=0100 Y=000000000000000000
PASS GATE: E=0 A=0101 Y=000000000000000000
PASS BEHAV: E=0 A=0101 Y=000000000000000000
PASS GATE: E=0 A=0110 Y=000000000000000000
PASS BEHAV: E=0 A=0110 Y=000000000000000000
PASS GATE: E=0 A=0111 Y=000000000000000000
PASS BEHAV: E=0 A=0111 Y=000000000000000000
PASS GATE: E=0 A=1000 Y=000000000000000000
PASS BEHAV: E=0 A=1000 Y=000000000000000000
PASS GATE: E=0 A=1001 Y=000000000000000000
PASS BEHAV: E=0 A=1001 Y=000000000000000000
PASS GATE: E=0 A=1010 Y=000000000000000000
PASS BEHAV: E=0 A=1010 Y=000000000000000000
PASS GATE: E=0 A=1011 Y=000000000000000000
PASS BEHAV: E=0 A=1011 Y=000000000000000000
PASS GATE: E=0 A=1100 Y=000000000000000000
PASS BEHAV: E=0 A=1100 Y=000000000000000000
PASS GATE: E=0 A=1101 Y=000000000000000000
PASS BEHAV: E=0 A=1101 Y=000000000000000000
PASS GATE: E=0 A=1110 Y=000000000000000000
PASS BEHAV: E=0 A=1110 Y=000000000000000000
PASS GATE: E=0 A=1111 Y=000000000000000000
PASS BEHAV: E=0 A=1111 Y=000000000000000000
PASS GATE: E=1 A=0000 Y=000000000000000001
PASS BEHAV: E=1 A=0000 Y=000000000000000001
PASS GATE: E=1 A=0001 Y=000000000000000010
PASS BEHAV: E=1 A=0001 Y=000000000000000010
PASS GATE: E=1 A=0010 Y=000000000000000100
PASS BEHAV: E=1 A=0010 Y=000000000000000100
PASS GATE: E=1 A=0011 Y=000000000000010000
PASS BEHAV: E=1 A=0011 Y=000000000000010000
PASS GATE: E=1 A=0100 Y=000000000000010000
PASS BEHAV: E=1 A=0100 Y=000000000000010000
PASS GATE: E=1 A=0101 Y=000000000001000000
PASS BEHAV: E=1 A=0101 Y=000000000001000000
PASS GATE: E=1 A=0110 Y=000000000001000000
PASS BEHAV: E=1 A=0110 Y=000000000001000000
PASS GATE: E=1 A=0111 Y=000000000100000000
PASS BEHAV: E=1 A=0111 Y=000000000100000000
PASS GATE: E=1 A=1000 Y=000000001000000000
PASS BEHAV: E=1 A=1000 Y=000000001000000000
PASS GATE: E=1 A=1001 Y=000000010000000000
PASS BEHAV: E=1 A=1001 Y=000000010000000000
PASS GATE: E=1 A=1010 Y=000000100000000000
PASS BEHAV: E=1 A=1010 Y=000000100000000000
PASS GATE: E=1 A=1011 Y=000001000000000000
PASS BEHAV: E=1 A=1011 Y=000001000000000000
PASS GATE: E=1 A=1100 Y=000010000000000000
PASS BEHAV: E=1 A=1100 Y=000010000000000000
PASS GATE: E=1 A=1101 Y=000100000000000000
PASS BEHAV: E=1 A=1101 Y=000100000000000000
PASS GATE: E=1 A=1110 Y=010000000000000000
PASS BEHAV: E=1 A=1110 Y=010000000000000000
PASS GATE: E=1 A=1111 Y=100000000000000000
PASS BEHAV: E=1 A=1111 Y=100000000000000000
Testbench completed.
```


## Utilization Report

Name	Slice LUTs (63400)	Bonded IOB (210)
N decoder4x16_gate	8	21

Resource usage was minimal, the design only used 8 LUTs out of 63,400 and 21 I/O pins out of 210. That makes sense since the logic is fully combinational with no registers or memory, and only one enable plus 4 input lines are needed to drive 16 outputs.

# Simulation Report

<pre> &gt; A[3:0] 0 E &gt; Y_gate[15:0] 0000 &gt; Y_behav[15:0] 0000 &gt; expected_out[15:0] 0000 &gt; i[31:0] 00000000 </pre>	<pre> 0 0 0000 0000 0000 00000000 </pre>	<pre> &gt; A[3:0] 0 E &gt; Y_gate[15:0] 0001 &gt; Y_behav[15:0] 0001 &gt; expected_out[15:0] 0001 &gt; i[31:0] 00000000 </pre>	<pre> 0 1 0001 0001 0001 00000000 </pre>	<pre> &gt; A[3:0] 0 E &gt; Y_gate[15:0] 8000 &gt; Y_behav[15:0] 8000 &gt; expected_out[15:0] 8000 &gt; i[31:0] 00000010 </pre>	<pre> f 1 8000 8000 8000 00000010 </pre>
--	--	--	--	--	--

 

The waveform and log output both confirm that the decoder behaves exactly as expected. Every output matches the intended value, and there were no failed assertions across the full range of inputs.

### Video Presentation

<https://www.youtube.com/watch?v=AU0JICCPny4>

### Conclusion

Overall, we have been able to put into practice concepts like decoder. We have a better understanding of utilization reports, testbenching, and simulation. We have been able to apply new coding concepts like color coded comments and display messages during testbench.