

Julio Flores (ID# : 016326856)
Victor Perez (ID# : 016196050)

Group I

Session E02

Lab 3

16x1 Multiplexer Using Nested 2x1 MUXes with Debounced Toggle Select Control

WEDNESDAY

JULY 2, 2025

ECE 3300L

Summer 2025

Objective:

The objective of this lab is to design and implement a 16-to-1 multiplexer using gate-level coding in Verilog by building it from 2-to-1 multiplexers. This lab incorporates toggle logic by using the Nexys A7-100T FPGA board's pushbuttons to control the select lines to behave like switches. The 16 input lines are connected to the board's switches through the (SW[15:0]), and the selected output is displayed on LED0. The design will be verified using testbenches and simulation in Vivado.

Design

Gate level code for 2x1 Mux:

-Addressing the inputs/outputs for the 2x1 mux.

```
module mux2x1(  
    input a, b,  
    input sel,  
    output y  
);  
    wire nsel, a1, b1;  
    not (nsel, sel);  
    and (a1, a, nsel);  
    and (b1, b, sel);  
    or (y, a1, b1);  
endmodule
```

16x1 Mux using loops:

-By using the module done before from the 2x1 mux, we are able to run a for-loop for each level of the mux.

```
module mux16x1(  
    input [15:0] in,  
    input [3:0] sel,  
    output out  
);  
    wire [15:0] level1;  
    wire [7:0] level2;  
    wire [3:0] level3;  
    genvar i;  
    generate  
        for (i = 0; i < 8; i = i + 1)  
            mux2x1 m1 (.a(in[2*i]), .b(in[2*i+1]), .sel(sel[0]), .y(level1[i]));  
        for (i = 0; i < 4; i = i + 1)  
            mux2x1 m2 (.a(level1[2*i]), .b(level1[2*i+1]), .sel(sel[1]), .y(level2[i]));  
        for (i = 0; i < 2; i = i + 1)  
            mux2x1 m3 (.a(level2[2*i]), .b(level2[2*i+1]), .sel(sel[2]), .y(level3[i]));  
  
        mux2x1 m4 (.a(level3[0]), .b(level3[1]), .sel(sel[3]), .y(out));  
    endgenerate  
endmodule
```

Debounce Module:

- This code help in debounce the signal of the button so it can get a clear number be getting the btn_clean to be 1 when the input signal is all 1111.

```
module debounce(  
    input clk,  
    input btn_in,  
    output reg btn_clean  
);  
    reg [2:0] shift_reg;  
  
    always @(posedge clk) begin  
        shift_reg <= {shift_reg[1:0], btn_in};  
        if (shift_reg == 3'b111) btn_clean <= 1;  
        else if (shift_reg == 3'b000) btn_clean <= 0;  
    end  
endmodule
```

Toggle Flip-Flop:

This section of the code implements the switches from the board to work correctly with the debounce button module. It uses if-else statements to toggle on or off the switches.


```
) module toggle_switch(  
    input clk,  
    input rst,  
    input btn_raw,  
    output reg state  
);  
    wire btn_clean;  
    reg btn_prev;  
  
    debounce db (.clk(clk), .btn_in(btn_raw), .btn_clean(btn_clean));  
  
    always @(posedge clk) begin  
        if (rst) begin  
            state <= 0;  
            btn_prev <= 0;  
        end else begin  
            if (btn_clean && !btn_prev)  
                state <= ~state;  
            btn_prev <= btn_clean;  
        end  
    end  
endmodule
```

Top-Level

- Combines all of the modules with the by using the toggle switch to verify if the button select is the same as the input lines.

```
module top_mux_lab3(  
    input clk,  
    input rst,  
    input [15:0] SW,  
    input btnU, btnD, btnL, btnR,  
    output LED0  
);  
    wire [3:0] sel;  
  
    toggle_switch t0 (.clk(clk), .rst(rst), .btn_raw(btnD), .state(sel[0]));  
    toggle_switch t1 (.clk(clk), .rst(rst), .btn_raw(btnR), .state(sel[1]));  
    toggle_switch t2 (.clk(clk), .rst(rst), .btn_raw(btnL), .state(sel[2]));  
    toggle_switch t3 (.clk(clk), .rst(rst), .btn_raw(btnU), .state(sel[3]));  
  
    mux16x1 mux (.in(SW), .sel(sel), .out(LED0));  
endmodule
```

Teshbench and Waveform

 

```

module tb_mux16x1;

    reg [15:0] in_tb;
    reg [3:0] sel_tb;
    wire out_tb;

    mux16x1 DUT (
        .in(in_tb),
        .sel(sel_tb),
        .out(out_tb)
    );

    integer i;

    initial begin
        in_tb = 16'b1001_0011_1010_0110;
        sel_tb = 4'b0000;

        #5;

        for (i = 0; i < 16; i = i + 1) begin
            sel_tb = i;
            #10;

            if (out_tb !== in_tb[i])
                $fatal(1, "FAIL: sel=%0d | Expected=%b | Got=%b", i, in_tb[i], out_tb);
            else
                $display("PASS: sel=%0d | out=%b", i, out_tb);
        end

        $display("All tests completed successfully.");
        $finish;
    end

endmodule

```

Implementation

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	12	0	0	63400	0.02
LUT as Logic	12	0	0	63400	0.02
LUT as Memory	0	0	0	19000	0.00
Slice Registers	24	0	0	126800	0.02
Register as Flip Flop	24	0	0	126800	0.02
Register as Latch	0	0	0	126800	0.00
F7 Muxes	2	0	0	31700	<0.01
F8 Muxes	1	0	0	15850	<0.01

Contributions:

Julio Flores: 50% - Verilog Code (Constraints Code) and Test demo and report

Victor Perez : 50% - Verilog Code (Testbench Code) and Waveform and report

Reflection:

This lab provided a comprehensive experience in verilog and FPGA implementation by designing a 16 to 1 MUX with a debouncing push button implementation. Seeing the final output accurately reflected on LED0 based on switch inputs confirmed that all components were working together correctly.