

ECE 3300L.01 - Lab 6

Dual BCD Up/Down Counters, ALU, and Control Display on 7-Segment

Professor Mohamed Aly
Group Q: Kevin Tang(015429622) &
Jared Mocling(015215057)

July 28th, 2025

Design:

clock_divider.v

```
module clock_divider(  
    input clockIn,  
    input [4:0] sel, // speed selector this uses SW[4:0]  
    input rst_n, // active-low reset  
    output clk_div  
  
);  
  
    reg [31:0] counter;  
  
    always @(posedge clockIn or negedge rst_n) begin  
        if (!rst_n)  
            counter <= 32'b0; // Reset the counter  
        else  
            counter <= counter + 1; // Increment on each rising clock edge  
        end  
  
    assign clk_div = counter[31 - sel]; // without 31 - : this will invert the physical switches
```

endmodule

bcd_counter.v

```
module bcd_counter(  
    input clk_div,  
    input rst_n, // Active-low reset (BTN0)  
    input dir_bit, // 1 = count up, 0 = count down (SW [8:7])  
    output reg [3:0] digit // Ones digit in BCD  
  
);  
  
    always@(posedge clk_div or negedge rst_n) begin  
  
        if (!rst_n) begin  
            digit <= 4'b0 ;  
            end  
        else begin
```

```

    if (!dir_bit) begin
        if (digit == 4'd9) begin
            digit <= 4'd0;

            end
        else
            digit <= digit + 1;
        end
    else begin
        if (digit == 4'd0) begin
            digit <= 4'd9;

            end
        else
            digit <= digit - 1;
        end

    end
end

```

endmodule

alu.v

`timescale 1ns / 1ps

module alu(

```

    input [3:0] A, //ones
    input [3:0] B, // tens
    input [1:0] ctrl, // SW[6:5]
    output reg [7:0] result
);
    reg [4:0] computation;

```

```

always @(*) begin
    if (ctrl == 2'b00)
        computation = A + B; // addition
    else if (ctrl == 2'b01)
        computation = A - B; // subtraction
    else
        computation = 8'd0;

    result[7:5] = 0;

```

```

        result[4] = computation / 4'd10;
        result[3:0] = computation % 4'd10;
end

```

```

endmodule

```

control_decoder.v

```

module control_decoder(
    input [3:0] controlSW, // {SW [8-5]}
    output reg [3:0] ctrl_nibble
);

```

```

    always@(*)begin
        ctrl_nibble = controlSW;
    end

```

```

endmodule

```

seg7_scan.v

```

module seg7_scan(
    input CLK,           // clock (used to multiplex)
    input rst_n,         // Active-low reset
    input [11:0] bits,
    output reg [6:0] SEG, // Segment outputs (active low)
    output [7:0] AN,     // 1 bit for each display, Digit select lines (active low)
    output DP
);
    assign DP = 1'b1; // turns off decimal point

```

```

    reg [3:0] digit;
    // Based on digit, the 7 segment will create an output between 0 - F
    always@(digit)
    case(digit)
        4'd0: SEG = 7'b0000001;
        4'd1: SEG = 7'b1001111;
        4'd2: SEG = 7'b0010010;
        4'd3: SEG = 7'b0000110;
        4'd4: SEG = 7'b1001100;
        4'd5: SEG = 7'b0100100;
        4'd6: SEG = 7'b0100000;

```

```
4'd7: SEG =7'b0001111;  
4'd8: SEG =7'b0000000;  
4'd9: SEG =7'b0001100;  
4'd10: SEG =7'b0001000; //A  
4'd11: SEG =7'b1100000; //b  
4'd12: SEG =7'b0110001; //c  
4'd13: SEG =7'b1000010; //d  
4'd14: SEG =7'b0110000; //E  
4'd15: SEG =7'b0111000; //F  
default: SEG = 7'b1111111;  
endcase
```

```
reg [20:0] tmp;  
always@(posedge CLK or negedge rst_n)  
if(!rst_n) tmp<=0;  
else tmp<=tmp+1;
```

```
wire [1:0] s = tmp[18:17];
```

```
always@(s, bits)  
case (s)  
2'd0:digit=bits[3:0]; 2'd1:digit=bits[7:4];  
2'd2:digit=bits[11:8];  
default:digit=4'b0000;  
endcase
```

```
reg [7:0] AN_tmp;  
always@(s)  
case(s)  
2'd0:AN_tmp=8'b11111110; 2'd1:AN_tmp=8'b11111101;  
2'd2:AN_tmp=8'b11111011;  
default:AN_tmp=8'b11111111;  
endcase
```

```
assign AN=AN_tmp;
```

```
endmodule
```

```
top_lab6.v
```

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer:
```

```
//
```

```
// Create Date: 07/28/2025 09:34:25 PM
```

```
// Design Name:
```

```
// Module Name:
```

```
// Project Name:
```

```
// Target Devices:
```

```
// Tool Versions:
```

```
// Description:
```

```
//
```

```
// Dependencies:
```

```
//
```

```
// Revision:
```

```
// Revision 0.01 - File Created
```

```
// Additional Comments:
```

```
//
```

```
////////////////////////////////////////////////////////////////
```

```
module top_lab6(
```

```
    input CLK,
```

```
    input rst_n, //BTN0 in the XDC file, the !rst_n input will make the button ACTIVE-LOW  
reset
```

```
    // SW[4:0] controls the speed
```

```
    // SW[6:5] controls the ALU bits
```

```
    //SW[8:7] controls the counter direction
```

```
    input [8:0] SW,
```

```
    // LED[7:4] debug for the tens BCD counter
```

```
    // LED[3:0] debug for the units BCD counter
```

```
    output [7:0] LED,
```

```
    output [6:0] SEG, // for the segments
```

```
    output DP, // decimal point
```

```
    output [7:0] AN //only have 3 displays showing so AN [2:0], 1 bit for each display
```

```

);
wire clk_out;
wire [3:0] digit0;
wire [3:0] digit1;
wire [7:0] finalResult;
wire [3:0] ctrl_nibble;
wire [11:0] bits;
assign bits[11:0] = { ctrl_nibble[3:0], finalResult[7:0] };
assign LED = {digit1[3:0], digit0[3:0]};

clock_divider clk1 ( .clockIn(CLK), .sel(SW[4:0]), .rst_n(!rst_n), .clk_div(clk_out) );

bcd_counter units ( .clk_div(clk_out), .rst_n(!rst_n), .dir_bit(SW[7]), .digit(digit0) );
bcd_counter tens ( .clk_div(clk_out), .rst_n(!rst_n), .dir_bit(SW[8]), .digit(digit1) );

alu addOrSubtract ( .A(digit0), .B(digit1), .ctrl(SW[6:5]), .result(finalResult) );

control_decoder control ( .controlSW(SW[8:5]), .ctrl_nibble(ctrl_nibble) );


seg7_scan display ( .CLK(CLK), .rst_n(!rst_n), .bits(bits), .SEG(SEG), .AN(AN),
.DP(DP) );

```


endmodule

Testbench Waveform:


Top_lab6_tb.v

 

Alu_tb.v

 


Bcd_counter_tb.v

 


Clock_divider_tb.v



Control_decoder_tb.v

 

Seg7_scan_tb.v

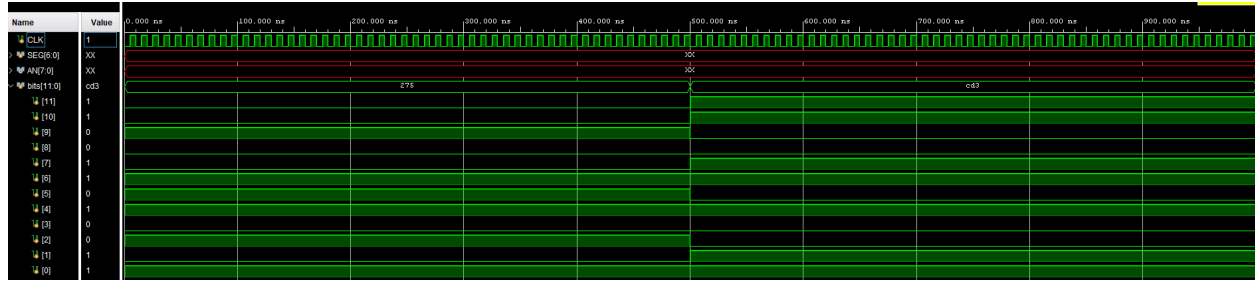

Utilization/Implementation:


Name	Slice LUTs (63400)	Slice Registers (126800)	F7 Muxes (31700)	Slice (15850)	LUT as Logic (63400)	Bonded IOB (210)	BUFGCTRL (32)
top_lab6	43	59	2	31	43	35	1

Power

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.132 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 25.6°C
Thermal Margin: 59.4°C (12.9 W)
Ambient Temperature: 25.0 °C
Effective θJA: 4.6°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

Time Summary:

Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 7.080 ns	Worst Hold Slack (WHS): 0.252 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 51	Total Number of Endpoints: 51	Total Number of Endpoints: 52

All user specified timing constraints are met

Contributions:

Jared Mocling (50%) - board demo, compiled code, report.

Kevin Tang (50%)- compiled code, testbench code, Synthesis reports, report