

ECE 3300L

Lab Report #4

Group A

Edwin Estrada (#015897050)

Michelle Lau (#016027427)

July 11, 2025

## Design

### 10 to 32 Decoder

```
module Decoder10to32(  
    input [9:0] SW_in,  
    output reg [31:0] out  
);  
  
    initial out = 32'd0;  
  
    always @(*) begin  
        case (SW_in[9:8])  
            2'b00: out[7:0] = SW_in;  
            2'b01: out[15:8] = SW_in;  
            2'b10: out[23:16] = SW_in;  
            2'b11: out[31:24] = SW_in;  
        endcase  
    end  
endmodule
```

Controlling the 8-digit 7-seg display involves using a 32-bit input bus. To control the 32-input bus, we use 10 of the 16 switches provided.

The MSB being the reset.

The next 2 of them are used to determine which 8-bit part of the 32-bit bus (in other words, which set of two digits on the display) to select.

The other 8 switches set the value of that 8-bit part of the 32-bit bus.

## 7-Segment Display Driver

```
module seg7_driver(  
    input clk,  
    input rst_n,  
    input [31:0] SW,  
    output reg [6:0] Cnode,  
    output dp,  
    output [7:0] AN  
);  
    reg [19:0] tmp;  
    reg [3:0] digit;  
    assign dp = 1'b1;  
    always@(digit)  
        case(digit)  
            4'd0: Cnode=7'b0000001; 4'd1: Cnode=7'b1001111; 4'd2: Cnode=7'b0010010;  
            4'd3: Cnode=7'b0000110; 4'd4: Cnode=7'b1001100; 4'd5: Cnode=7'b0100100;  
            4'd6: Cnode=7'b0100000; 4'd7: Cnode=7'b0001111; 4'd8: Cnode=7'b0000000;  
            4'd9: Cnode=7'b0001100; 4'd10: Cnode=7'b0001000; 4'd11: Cnode=7'b1100000;  
            4'd12: Cnode=7'b0110001; 4'd13: Cnode=7'b1000010; 4'd14: Cnode=7'b0110000;  
            4'd15: Cnode=7'b0111000; default: Cnode=7'b1111111;  
        endcase  
    always@(posedge clk or negedge rst_n)  
        if(!rst_n) tmp<=0;  
        else tmp<=tmp+1;  
    wire [2:0] s = tmp[19:17];  
  
    always@(s, SW)  
        case (s)  
            3'd0: digit=SW[3:0]; 3'd1: digit=SW[7:4];  
            3'd2: digit=SW[11:8]; 3'd3: digit=SW[15:12];  
            3'd4: digit=SW[19:16]; 3'd5: digit=SW[23:20];  
            3'd6: digit=SW[27:24]; 3'd7: digit=SW[31:28];  
            default: digit=4'b0000;  
        endcase  
    reg [7:0] AN_tmp;  
    always@(s)  
        case(s)  
            3'd0: AN_tmp=8'b11111110; 3'd1: AN_tmp=8'b11111101;  
            3'd2: AN_tmp=8'b11111011; 3'd3: AN_tmp=8'b11110111;  
            3'd4: AN_tmp=8'b11101111; 3'd5: AN_tmp=8'b11011111;  
            3'd6: AN_tmp=8'b10111111; 3'd7: AN_tmp=8'b01111111;  
            default: AN_tmp=8'b11111111;  
        endcase  
    assign AN=AN_tmp;  
endmodule
```

Given a 100Mhz base clock on the board, the board counts to 1 million and resets the counter, changing each anode of the 7-seg display to 0 one at a time throughout the time the board is counting to 1 million. With the 100Mhz clock, that means the 7-seg display is blinking 100 times per second (100hz), giving the illusion to the user that the seven seg display is on. Then, what 4-bit part of the 32-bit input to select depends on the current count of the 1 million, depending on the 3 highest bits of the counter. This makes sure each digit on the 7-seg display represents a unique value. Additionally, anytime digit is changed from the counter reaching certain values, a digit on the 7-seg display will display its respective value given by the 4-bit part of the 32-bit input.

## High Level Implementation


```
module MainProgram(  
    input clk,  
    input [10:0] SW_in,      // [10] rst_n, [9:8] digit, [7:0] input  
    output [10:0] led,  
    output [6:0] Cnode,     // 7-seg [a-g]  
    output dp,  
    output [7:0] AN        // 7-seg enable lines  
);  
  
    wire [31:0] SW;  
  
    Decoder10to32 decoder(.SW_in(SW_in[9:0]), .out(SW));  
    seg7_driver driver(.clk(clk), .rst_n(SW_in[10]), .SW(SW), .Cnode(Cnode), .dp(dp), .AN(AN));  
  
    assign led = SW_in;  
  
endmodule
```

Connecting everything together, the switches go into the decoder, which is output into a declared wire. The output from the wire goes into the driver, with Cnode, dp, and AN going into the 7-seg display. We also map the switches to their respective LED to show on the board that a switch is on.
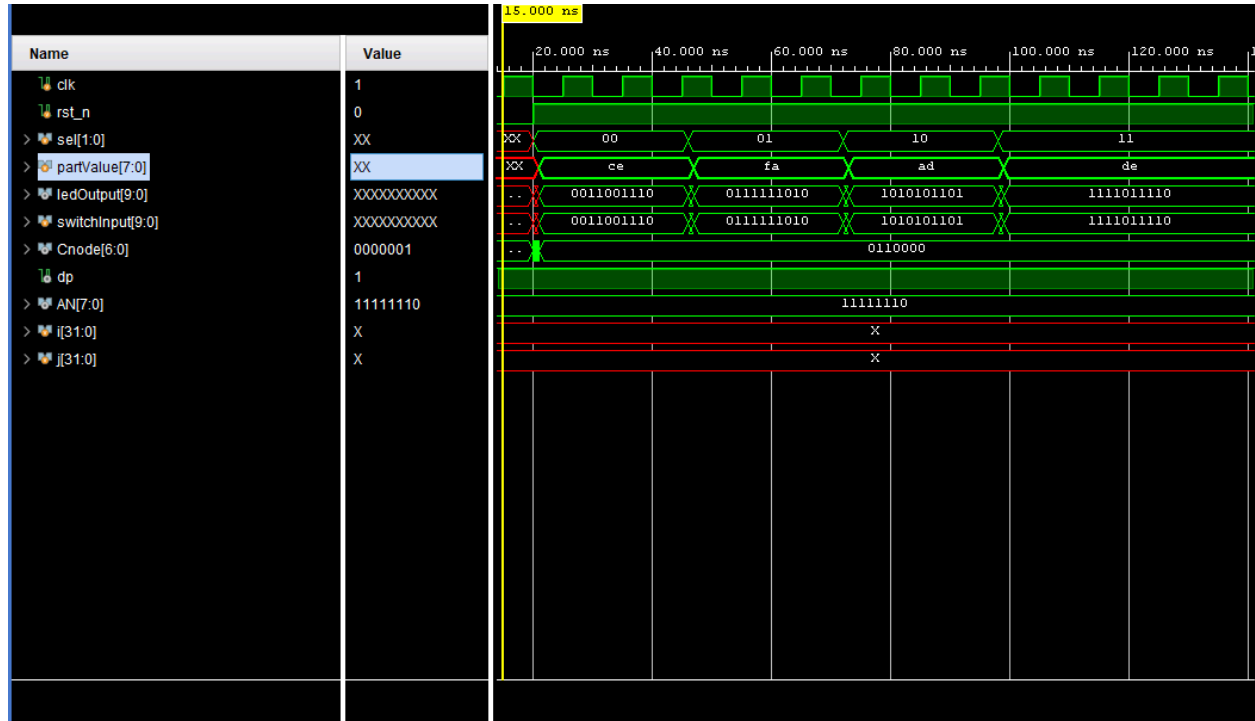
# Simulation Waveform

This simulation displays “DEADFACE” on the 8-digit 7-seg display.

We begin by toggling reset. We then use the 10 switches and the 10 to 32 decoder to give SW a value of 0xDEADFACE. AN selects the rightmost digit to turn on, with Cnode having a value of “0110000” (the letter E).




AN now selects the second rightmost bit, with Cnode having a value of “0110001” (the second rightmost digit on the display shows the letter C).




AN now selects the third rightmost bit, with Cnode having a value of “0001000” (the third rightmost digit on the display shows the letter A).



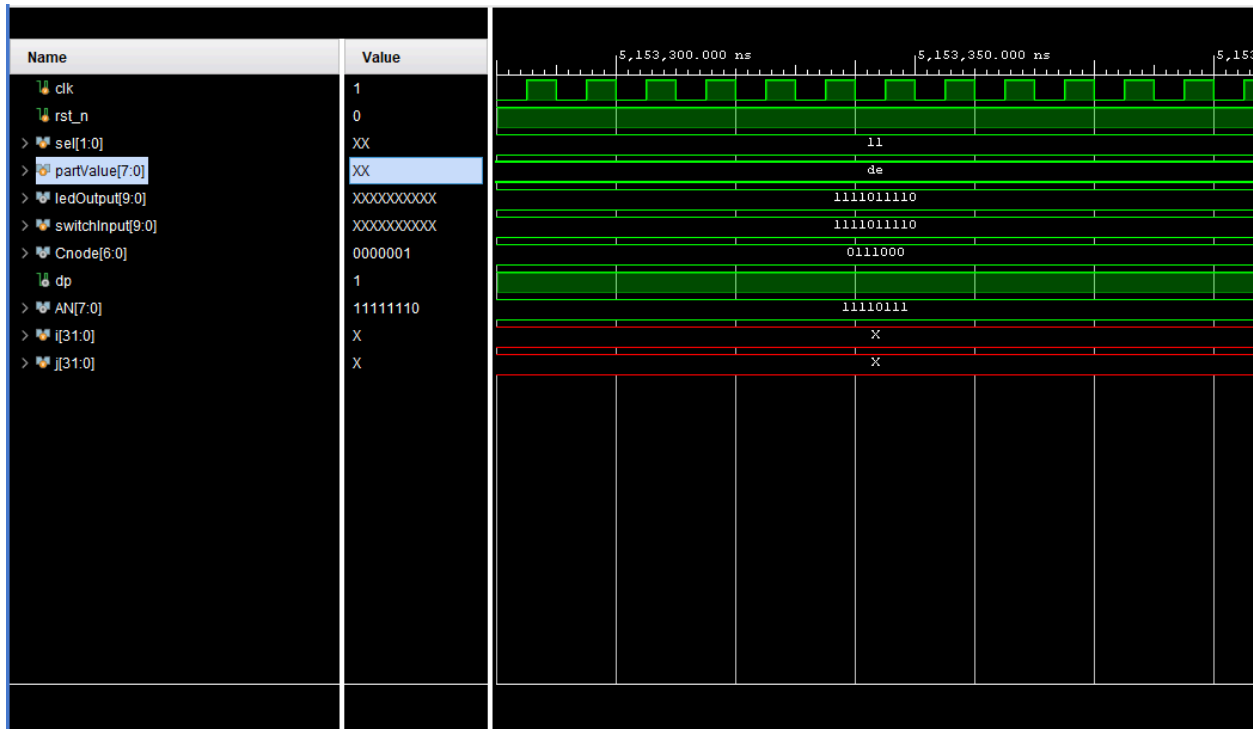AN now selects the fourth rightmost bit, with Cnode having a value of “0111000” (the fourth rightmost digit on the display shows the letter F).



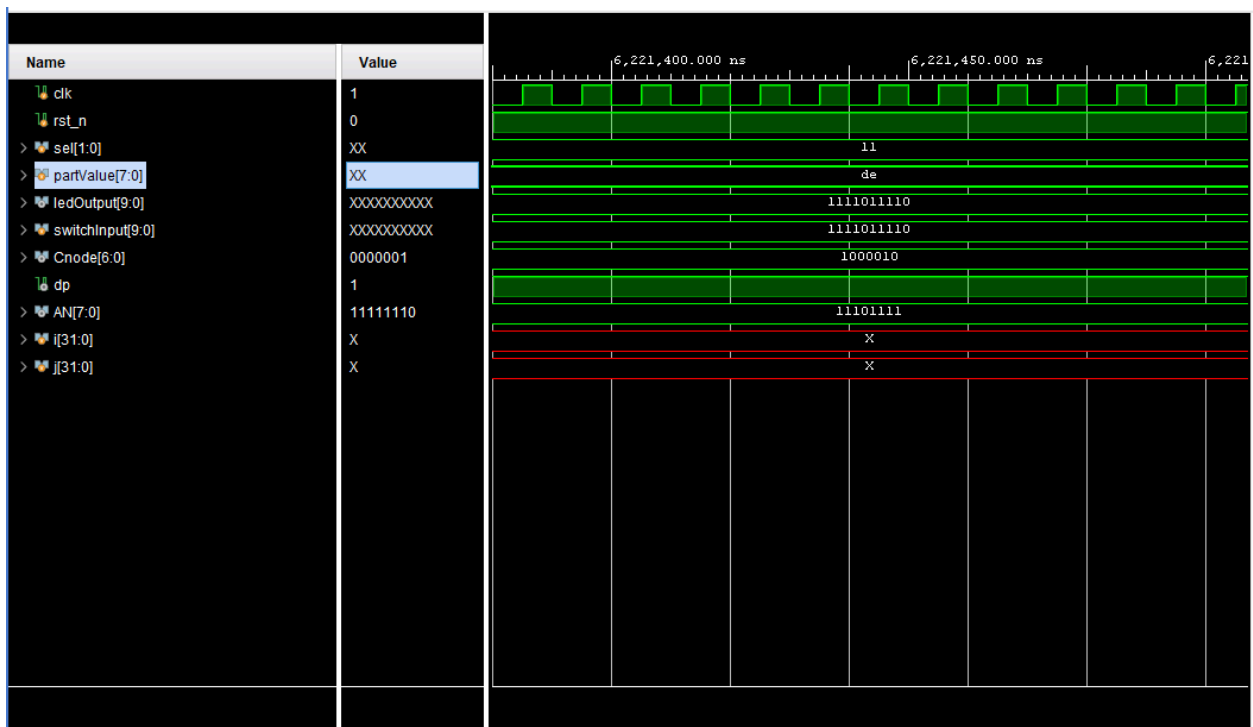AN now selects the fourth leftmost bit, with Cnode having a value of “1000010” (the fourth leftmost digit on the display shows the letter D).



AN now selects the third leftmost bit, with Cnode having a value of “0001000” (the third leftmost digit on the display shows the letter A).



AN now selects the second leftmost bit, with Cnode having a value of “0110000” (the second leftmost digit on the display shows the letter E).





AN now selects the leftmost bit, with Cnode having a value of “1000010” (the leftmost digit on the display shows the letter D).




# Implementation

## Utilization Table:

### Summary

Resource	Utilization	Available	Utilization %
LUT	20	63400	0.03
FF	52	126800	0.04
IO	39	210	18.57

 

## Timing Summary:

### Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 7.440 ns	Worst Hold Slack (WHS): 0.324 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 20	Total Number of Endpoints: 20	Total Number of Endpoints: 21


All user specified timing constraints are met.

# Contribution

Michelle Lau (50%) - Debugging, implementation and board demo

Edwin Estrada (50%) - Programming, debugging, and test benching

# Board Demo

<  Demo.MOV >