

ECE 3300L.01 - Lab 3

16x1 Multiplexer Using Nested 2x1 MUXes with Debounced Toggle Select Control

Professor Mohamed Aly
Group Q: Kevin Tang(015429622) &
Jared Mocling(015215057)

July 2nd, 2025

Objective: In this lab, you will design a 16-to-1 multiplexer (MUX16x1) using gate-level 2x1 multiplexers in Verilog. You will control the MUX using the push buttons on the Nexys A7 board, which must behave like switches using toggle logic. This requires implementing a debouncing system and a toggle flip-flop for each select bit. The output of the multiplexer will be shown on LED0, while the inputs will be fed from the 16 switches (SW[15:0])

Code

2x1 Mux Module:

```
1 module mux2x1 (  
2     input a, b,  
3     input sel,  
4     output y  
5 );  
6     wire nsel, a1, b1;  
7     not (nsel, sel);  
8     and (a1, a, nsel);  
9     and (b1, b, sel);  
10    or (y, a1, b1);  
11 endmodule
```

Here is our 2x1 module. This module addresses the inputs and outputs of the 2x1 module

16x1 Mux Module:

```
1 module mux16x1 (  
2     input [15:0] in, //switch inputs  
3     input [3:0] sel,  
4     output out //LED output  
5 );  
6  
7     wire [15:0] level1;  
8     wire [7:0] level2;  
9     wire [3:0] level3;  
10  
11     genvar i;  
12     generate  
13     for (i = 0; i < 8; i = i + 1)  
14     mux2x1 m1 (.a(in[2*i]), .b(in[2*i+1]), .sel(sel[0]), .y(level1[i]));  
15     for (i = 0; i < 4; i = i + 1)  
16     mux2x1 m2 (.a(level1[2*i]), .b(level1[2*i+1]), .sel(sel[1]), .y(level2[i]));  
17     for (i = 0; i < 2; i = i + 1)  
18     mux2x1 m3 (.a(level2[2*i]), .b(level2[2*i+1]), .sel(sel[2]), .y(level3[i]));  
19  
20     mux2x1 m4 (.a(level3[0]), .b(level3[1]), .sel(sel[3]), .y(out));  
21     endgenerate  
22 endmodule
```

Using our 2x1 mux module, we create our 16x1 mux by running for-loops for each level of the mux.

Debounce Module:

```

1 module debounce (
2     input clk,
3     input btn_in,
4     output reg btn_clean
5 );
6     reg [2:0] shift_reg;
7
8     always @(posedge clk) begin
9         shift_reg <= {shift_reg[1:0], btn_in};
10        if (shift_reg == 3'b111) btn_clean <= 1;
11        else if (shift_reg == 3'b000) btn_clean <= 0;
12    end
13 endmodule

```

Our debounce module is created so that the signal of the button can get a clear number and to get this clean signal btn_clean = 1 when the input signal is at 1111

Toggle Switch Module:

```

1 module toggle_switch (
2     input clk,
3     input rst,
4     input btn_raw,
5     output reg state
6 );
7     wire btn_clean;
8     reg btn_prev;
9
10    debounce db (.clk(clk), .btn_in(btn_raw), .btn_clean(btn_clean));
11
12    always @(posedge clk) begin
13        if (rst) begin
14            state <= 0;
15            btn_prev <= 0;
16        end else begin
17            if (btn_clean && !btn_prev)
18                state <= ~state;
19            btn_prev <= btn_clean;
20        end
21    end
22 endmodule

```

Here the toggle switch module uses the debounce module to make sure that one switch is the only trigger. This uses if-else statements to make sure that the toggle on or off is based on which switch is selected.


Top-Level Module:


```
module top_mux_lab3 (  
    input clk,  
    input rst,  
    input [15:0] SW,  
    input btnU, btnD, btnL, btnR,  
    output LED0  
);  
    wire [3:0] sel;  
  
    toggle_switch t0 (.clk(clk), .rst(rst), .btn_raw(btnD), .state(sel[0]));  
    toggle_switch t1 (.clk(clk), .rst(rst), .btn_raw(btnR), .state(sel[1]));  
    toggle_switch t2 (.clk(clk), .rst(rst), .btn_raw(btnL), .state(sel[2]));  
    toggle_switch t3 (.clk(clk), .rst(rst), .btn_raw(btnU), .state(sel[3]));  
  
    mux16x1 mux (.in(SW), .sel(sel), .out(LED0));  
endmodule
```

Here this combines all of our modules by using our toggle switch module to verify if the button that is selected is the same as the input lines.


Utilization Table:

Resource	Utilization	Available	Utilization %
LUT	12	63400	0.02
FF	24	126800	0.02
IO	23	210	10.95

 

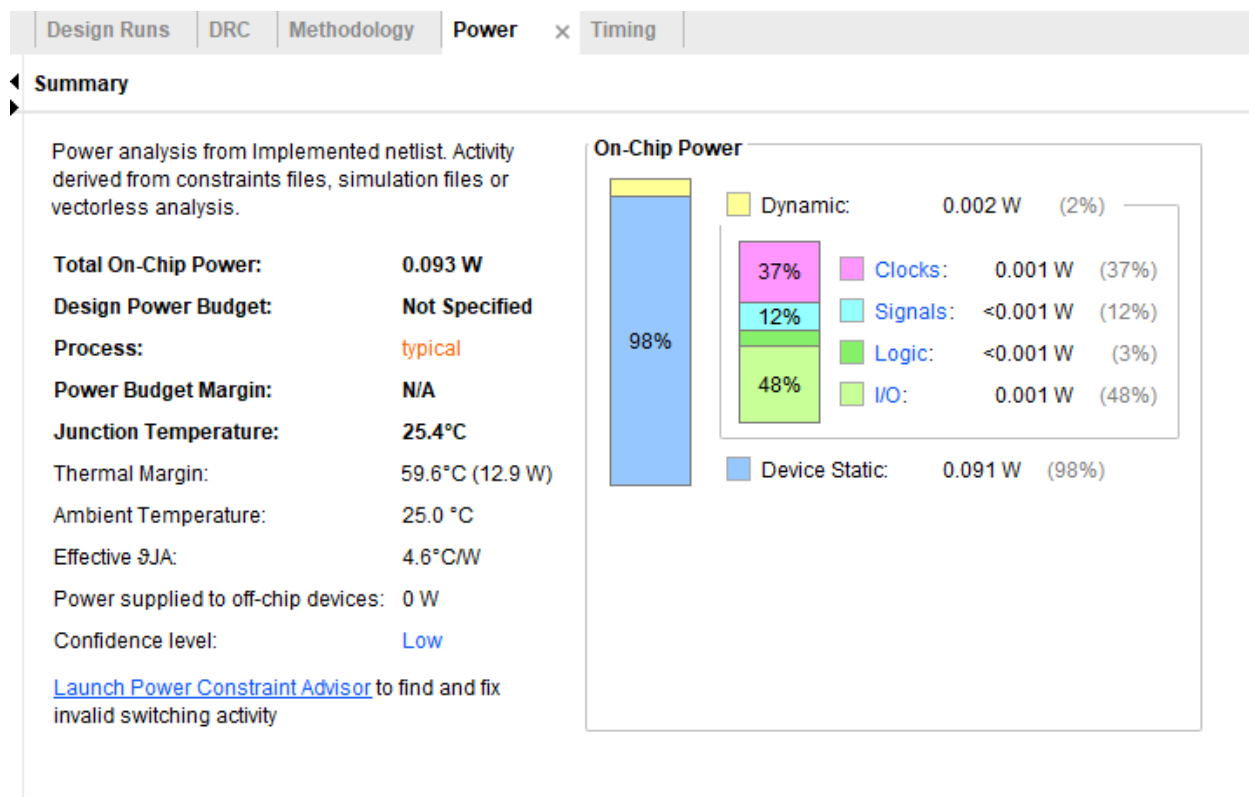

Simulation Table

 

```

module mux16x1_tb;
    reg [15:0] in;
    reg [3:0] sel;
    wire out;

    mux16x1 uut (
        .in(in),
        .sel(sel),
        .out(out)
    );

    initial begin
        in = 16'b1010_0101_1010_1100;
        for (sel = 0; sel < 16; sel = sel + 1) begin
            #10;
            $display("sel=%d, out=%b", sel, out);
        end
        $finish;
    end
endmodule

```

This testbench tests the 16x1 multiplexor module. We imputed a 16-bit value (1010 0101 1010 1100) and ran bits 0-15 for the sel values. The goal was to test the inputs.

Contributions:

Kevin Tang (50%) - board demo, compiled code

Jared Mocling (50%)- , test bench code, Synthesis reports

We both worked on the lab report together.