

ECE 3300L

Lab Report #5

Group E

Paul Kim (ID: 015236949)

Winson Zhu (ID: 016416790)


July 21, 2025

Design:


- **clock_divider.v** - Generates a 32-bit incrementing counter from the system clock.
- **mux32x1.v** - Selects one bit from the 32-bit counter using SW[4:0], outputting a divided clock.
- **bcd_up_down_counter.v** - A two-digit BCD counter. Handles up/down counting and cascading between digit0 and digit1.
- **seg7_scan.v** - Drives the 2-digit 7-segment display with time-multiplexed output.
- **top_lab5.v** - Integrates all submodules. Connects switches, buttons, LEDs, and 7-segment outputs.

Simulation:

 
clock_divider_tb: Verify counter increments.



 
mux32x1_tb: Ensure correct bit selection for various sel.



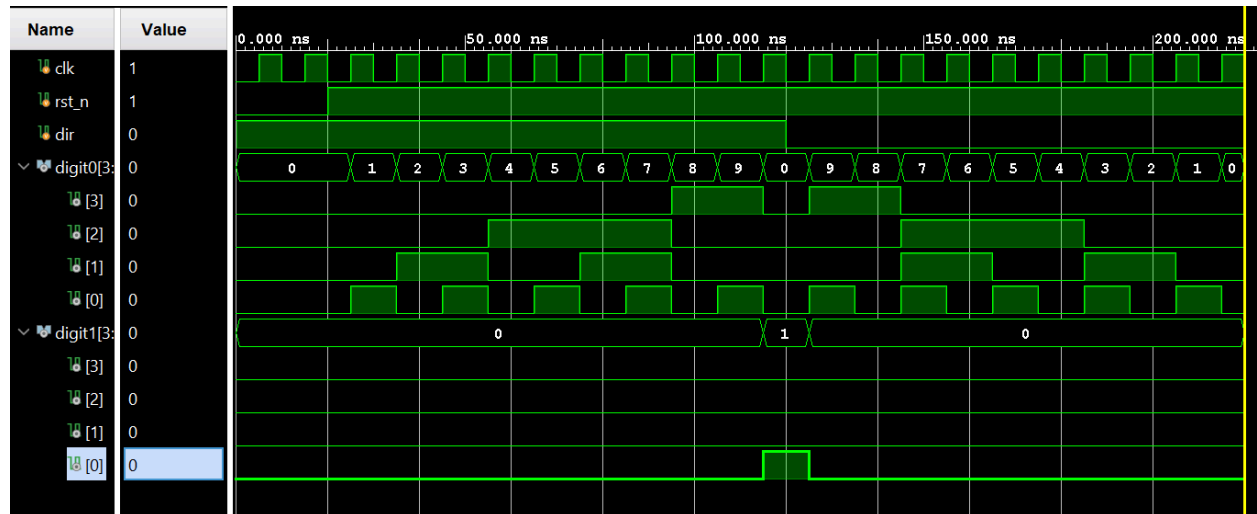bcd_up_down_counter_tb: Confirm up/down counting behavior with reset.



 seg7_scan_tb: Verify multiplexing and segment decoding.



Implementation:

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	26	0	0	63400	0.04
LUT as Logic	26	0	0	63400	0.04
LUT as Memory	0	0	0	19000	0.00
Slice Registers	57	0	0	126800	0.04
Register as Flip Flop	57	0	0	126800	0.04
Register as Latch	0	0	0	126800	0.00
F7 Muxes	4	0	0	31700	0.01
F8 Muxes	0	0	0	15850	0.00

Contributions:

Paul Kim - Source Codes, Testbench, Simulation - 50% contribution

Winson Zhu - Source Codes, Implementation, Hardware Demo - 50% contribution