

# ECE3300L Lab 5

Group B

By Faris Khan (ID #: 012621102)

AND

Nicholas Williams (ID#:016556982)

20 July 2025

## **Introduction**

This lab focuses on the design and implementation of a two-digit BCD up/down counter on the Nexys A7 FPGA board. The system allows a user to control the counting speed via a 5-bit switch input and to select the counting direction (up or down) and reset the counter using two onboard pushbuttons. A 32-bit free-running counter and a 32-to-1 multiplexer are used to generate a variable clock signal, which drives a cascaded BCD counter capable of counting from 00 to 99 in either direction. The output is displayed on a dual-digit 7-segment display using time-multiplexing, where only one digit is illuminated at a time at a rate fast enough to appear steady to the human eye. Additionally, the current BCD value is shown on the onboard LEDs for debugging and binary visualization. This lab reinforces modular design, hardware interfacing, and clock division techniques while providing hands-on experience with Verilog simulation, synthesis, and real-time testing on FPGA hardware.

## **Code**

### **clock\_divider.v**

```
module clock_divider(  
    input clk,  
    input rst_n,  
    output reg [31:0] count  
);  
    always @(posedge clk or negedge rst_n) begin  
        if (!rst_n)  
            count <= 32'd0;  
        else  
            count <= count + 1;  
        end  
    endmodule
```

The clock\_divider module is a 32-bit counter that just keeps counting up every time the clock ticks. If the reset signal is pressed (active low), it resets the count back to zero. We use this counter to slow down the 100 MHz clock by picking one of its bits later on, so we can control how fast the BCD counter updates.

### **mux32x1.v**

```
module mux32x1(  
    input wire [31:0] count,  
    input wire [4:0] sel,  
    output wire clk_out  
);  
    assign clk_out = count[sel];  
endmodule
```

The mux32x1 module takes in the 32-bit output from the clock divider and a 5-bit select input from the switches. It picks one bit out of the 32 based on the value of the select input and sends that out as clk\_out. This lets us change how fast the counter runs by choosing a slower or faster clock pulse from the divider.

## bcd\_up\_down\_counter.v

```
module bcd_up_down_counter (
    input wire clk,
    input wire rst_n,
    input wire dir,
    output reg [3:0] digit0,
    output reg [3:0] digit1
);
    wire rollover_up    = (digit0 == 4'd9) && dir;
    wire rollover_down  = (digit0 == 4'd0) && ~dir;

    always @(posedge clk or negedge rst_n) begin
        if (!rst_n) begin
            digit0 <= 4'd0;
            digit1 <= 4'd0;
        end else begin
            if (dir) begin
                digit0 <= (digit0 == 4'd9) ? 4'd0 : digit0 + 1;
            end else begin
                digit0 <= (digit0 == 4'd0) ? 4'd9 : digit0 - 1;
            end
            if (rollover_up)
                digit1 <= (digit1 == 4'd9) ? 4'd0 : digit1 + 1;
            else if (rollover_down)
                digit1 <= (digit1 == 4'd0) ? 4'd9 : digit1 - 1;
        end
    end
endmodule
```

The `bcd_up_down_counter` module keeps track of a two-digit BCD count. It uses `digit0` for the ones place and `digit1` for the tens place. Depending on the `dir` input, it either counts up or down. If reset is pressed, both digits go back to 0. When counting up, `digit0` goes from 0 to 9 and rolls over to 0 again, while `digit1` increases by 1. When counting down, `digit0` goes from 0 to 9 in reverse, and if it hits 0, `digit1` decreases. It handles rollover logic so the counter correctly goes from 09 → 10 or 00 → 99 depending on direction.

## seg7\_scan.v

```
module seg7_scan (
    input wire clk,
    input wire rst_n,
    input wire [3:0] digit0,    // Units digit BCD
    input wire [3:0] digit1,    // Tens digit BCD
    output reg [7:0] an,
    output reg [6:0] seg
);

    // Scan counter for time multiplexing
    reg [19:0] scan_counter;
    wire scan_clk;

    assign scan_clk = scan_counter[19];

    // Scan counter
    always @(posedge clk or negedge rst_n) begin
        if (!rst_n) begin
            scan_counter <= 20'b0;
        end else begin
            scan_counter <= scan_counter + 1;
        end
    end

    // Current digit selection
    reg [3:0] current_digit;

    // Multiplexer for digit selection and anode control
    always @(posedge clk or negedge rst_n) begin
        if (!rst_n) begin
            an <= 8'b1111_1111; // everything off
            current_digit <= 4'b0;
        end else begin
            case (scan_clk)
                1'b0: begin
                    an <= 8'b1111_1110;    // Enable digit 0 (units), disable others
                    current_digit <= digit0;
                end
                1'b1: begin
                    an <= 8'b1111_1101;    // Enable digit 1 (tens), disable others
                    current_digit <= digit1;
                end
            endcase
        end
    end

    // BCD to 7-segment decoder
    always @(*) begin
        case (current_digit)
            4'd0: seg = 7'b1000000; // 0
            4'd1: seg = 7'b1111001; // 1
            4'd2: seg = 7'b0100100; // 2
            4'd3: seg = 7'b0110000; // 3
            4'd4: seg = 7'b0011001; // 4
            4'd5: seg = 7'b0010010; // 5
            4'd6: seg = 7'b0000010; // 6
            4'd7: seg = 7'b1111000; // 7
            4'd8: seg = 7'b0000000; // 8
            4'd9: seg = 7'b0010000; // 9
            default: seg = 7'b1111111;
        endcase
    end
endmodule
```

The seg7\_scan module controls the two-digit 7-segment display using time-multiplexing. It takes in the BCD values for the ones and tens digits and switches

between them fast enough that they both appear to be lit at the same time. It uses a counter to create a slower clock (scan\_clk) and decides which digit to show based on that. When scan\_clk is 0, it turns on digit0 (the ones place), and when it's 1, it shows digit1 (the tens place). The module also has a decoder that turns the 4-bit BCD number into the correct segment pattern to light up the right number on the display.

## top\_lab5.v

```
module top_lab5(
    input wire CLK,           // 100 MHz board clock
    input wire [4:0] SW,      // speed-select index
    input wire BTN0,         // reset (active low)
    input wire BTN1,         // direction
    output wire [7:0] AN,     // digit enable
    output wire [6:0] SEG,    // segment pins
    output wire [4:0] LED_SW, // debug: SW[4:0]
    output wire [7:0] LED_BCD // debug: {tens, units}
);

    wire rst_n = ~BTN0;
    wire [31:0] clk_count;
    wire clk_div;

    clock_divider u_clkdiv (
        .clk (CLK),
        .rst_n (rst_n),
        .count (clk_count)
    );
    mux32x1 u_mux (
        .count (clk_count),
        .sel (SW),
        .clk_out (clk_div)
    );

    // BCD up/down, driven by BTN1
    wire dir = ~BTN1;
    wire [3:0] units, tens;

    bcd_up_down_counter u_counter (
        .clk (clk_div),
        .rst_n (rst_n),
        .dir (dir),
        .digit0(units),
        .digit1(tens)
    );

    // 7-seg scanner
    seg7_scan u_scan (
        .clk (CLK),
        .rst_n (rst_n),
        .digit0 (units),
        .digit1 (tens),
        .an (AN),
        .seg (SEG)
    );

    // debug LEDs
    assign LED_SW = SW[4:0];
    assign LED_BCD = {tens, units};

endmodule
```

The top\_lab5 module connects everything together for the project. It takes in the main 100 MHz clock, switch inputs, and pushbuttons, then wires them up to the submodules. First, the clock\_divider creates a big 32-bit counter. That counter gets passed into a mux32x1, which uses the switches to pick how fast the BCD counter should run. The selected bit (slower clock) drives the bcd\_up\_down\_counter, which counts up or down

depending on BTN1. The two digits of the counter are passed to the seg7\_scan module to display them on the 7-segment display using time-multiplexing. For debugging, the switch values are shown on LED\_SW, and the current BCD digits are sent to LED\_BCD.



# Testbenches

## tb bcd up down counter.v

```
`timescale 1ns/1ps
module tb_bcd_up_down_counter;
    reg      clk, rst_n, dir;
    wire [3:0] digit0, digit1;

    // Unit under test
    bcd_up_down_counter uut (
        .clk      (clk),
        .rst_n    (rst_n),
        .dir      (dir),
        .digit0   (digit0),
        .digit1   (digit1)
    );

    initial begin
        clk      = 0;
        rst_n    = 0;
        dir      = 1;           // count up
        #20 rst_n = 1;         // release reset


        // count up 12 cycles
        repeat (12) begin
            #10 $display("UP  @%0t  tens=%0d units=%0d", $time, digit1, digit0);
        end

        // switch direction and count down
        dir = 0;
        repeat (12) begin
            #10 $display("DN  @%0t  tens=%0d units=%0d", $time, digit1, digit0);
        end

        end

        // 100 MHz clock
        always #5 clk = ~clk;
    endmodule
```

```
UP  @30000  tens=0 units=1
UP  @40000  tens=0 units=2
UP  @50000  tens=0 units=3
UP  @60000  tens=0 units=4
UP  @70000  tens=0 units=5
UP  @80000  tens=0 units=6
UP  @90000  tens=0 units=7
UP  @100000 tens=0 units=8
UP  @110000 tens=0 units=9
UP  @120000 tens=1 units=0
UP  @130000 tens=1 units=1
UP  @140000 tens=1 units=2
DN  @150000 tens=1 units=1
DN  @160000 tens=1 units=0
DN  @170000 tens=0 units=9
DN  @180000 tens=0 units=8
DN  @190000 tens=0 units=7
DN  @200000 tens=0 units=6
DN  @210000 tens=0 units=5
DN  @220000 tens=0 units=4
DN  @230000 tens=0 units=3
DN  @240000 tens=0 units=2
DN  @250000 tens=0 units=1
DN  @260000 tens=0 units=0
```

 

## Tb\_clock\_divider.v

```
`timescale 1ns/1ps
module tb_clock_divider;
    reg        clk;
    reg        rst_n;
    wire [31:0] count;


    // Unit under test
    clock_divider uut (
        .clk    (clk),
        .rst_n  (rst_n),
        .count  (count)
    );

    initial begin
        clk    = 0;
        rst_n  = 0;
        #20 rst_n = 1;          // release reset

        // print count every 200 ns
        repeat (10) begin
            #200;
            $display("[%0t] count = %0d", $time, count);
        end
        $finish;
    end

    // 100 MHz clock
    always #5 clk = ~clk;
endmodule
```
 
```
[220000] count = 20
[420000] count = 40
[620000] count = 60
[820000] count = 80
```



## Tb\_mux32x1.v


```
`timescale 1ns/1ps
module tb_mux32x1;
    reg [31:0] count;
    reg [4:0] sel;
    wire      clk_out;

    // Unit under test
    mux32x1 uut (
        .count    (count),
        .sel      (sel),
        .clk_out  (clk_out)
    );

    initial begin
        // pick a pattern for count
        count = 32'h1234_5678;
        // sweep through all select values
        for (sel = 0; sel < 32; sel = sel + 1) begin
            #10;
            $display("sel=%0d => clk_out = count[%0d] = %b", sel, sel, clk_out);
        end
        $finish;
    end
endmodule
```

```
sel=1 => clk_out = count[1] = 0
sel=2 => clk_out = count[2] = 0
sel=3 => clk_out = count[3] = 1
sel=4 => clk_out = count[4] = 1
sel=5 => clk_out = count[5] = 1
sel=6 => clk_out = count[6] = 1
sel=7 => clk_out = count[7] = 0
sel=8 => clk_out = count[8] = 0
sel=9 => clk_out = count[9] = 1
sel=10 => clk_out = count[10] = 1
sel=11 => clk_out = count[11] = 0
sel=12 => clk_out = count[12] = 1
sel=13 => clk_out = count[13] = 0
sel=14 => clk_out = count[14] = 1
sel=15 => clk_out = count[15] = 0
sel=16 => clk_out = count[16] = 0
sel=17 => clk_out = count[17] = 0
sel=18 => clk_out = count[18] = 1
sel=19 => clk_out = count[19] = 0
sel=20 => clk_out = count[20] = 1
sel=21 => clk_out = count[21] = 1
sel=22 => clk_out = count[22] = 0
sel=23 => clk_out = count[23] = 0
sel=24 => clk_out = count[24] = 0
sel=25 => clk_out = count[25] = 1
sel=26 => clk_out = count[26] = 0
sel=27 => clk_out = count[27] = 0
sel=28 => clk_out = count[28] = 1
sel=29 => clk_out = count[29] = 0
sel=30 => clk_out = count[30] = 0
sel=31 => clk_out = count[31] = 0
sel=0 => clk_out = count[0] = 0
sel=1 => clk_out = count[1] = 0
sel=2 => clk_out = count[2] = 0
sel=3 => clk_out = count[3] = 1
sel=4 => clk_out = count[4] = 1
sel=5 => clk_out = count[5] = 1
sel=6 => clk_out = count[6] = 1
sel=7 => clk_out = count[7] = 0
sel=8 => clk_out = count[8] = 0
sel=9 => clk_out = count[9] = 1
sel=10 => clk_out = count[10] = 1
sel=11 => clk_out = count[11] = 0
sel=12 => clk_out = count[12] = 1
sel=13 => clk_out = count[13] = 0
sel=14 => clk_out = count[14] = 1
sel=15 => clk_out = count[15] = 0
sel=16 => clk_out = count[16] = 0
sel=17 => clk_out = count[17] = 0
sel=18 => clk_out = count[18] = 1
sel=19 => clk_out = count[19] = 0
sel=20 => clk_out = count[20] = 1
sel=21 => clk_out = count[21] = 1
sel=22 => clk_out = count[22] = 0
sel=23 => clk_out = count[23] = 0
sel=24 => clk_out = count[24] = 0
sel=25 => clk_out = count[25] = 1
sel=26 => clk_out = count[26] = 0
sel=27 => clk_out = count[27] = 0
sel=28 => clk_out = count[28] = 1
sel=29 => clk_out = count[29] = 0
sel=30 => clk_out = count[30] = 0
```

---

 

## tb\_seg7\_scan.v

```
`timescale 1ns/1ps
module tb_seg7_scan;
    reg    clk, rst_n;
    reg [3:0] digit0, digit1;
    wire [7:0] an;
    wire [6:0] seg;


    // Unit under test
    seg7_scan uut (
        .clk      (clk),
        .rst_n    (rst_n),
        .digit0   (digit0),
        .digit1   (digit1),
        .an       (an),
        .seg      (seg)
    );

    initial begin
        clk      = 0;
        rst_n    = 0;
        digit0   = 4'd5;    // units = 5
        digit1   = 4'd2;    // tens  = 2
        #20 rst_n = 1;      // release reset

        // watch a few multiplex cycles
        repeat (16) begin
            #100;
            $display("time=%0t AN=%b SEG=%b", $time, an, seg);
        end
        $finish;
    end
end

 time=120000 AN=11111110 SEG=0010010
time=220000 AN=11111110 SEG=0010010
time=320000 AN=11111110 SEG=0010010
time=420000 AN=11111110 SEG=0010010
time=520000 AN=11111110 SEG=0010010
time=620000 AN=11111110 SEG=0010010
time=720000 AN=11111110 SEG=0010010
time=820000 AN=11111110 SEG=0010010
time=920000 AN=11111110 SEG=0010010
```





## Tb\_top\_lab5.v

```
module tb_top_lab5;
// Inputs
reg CLK;
reg [4:0] SW;
reg BTN0; // pushbutton, active low input to DUT -> rst_n = ~BTN0
reg BTN1; // direction button: 1=Up, 0=Down

// Outputs
wire [7:0] AN;
wire [6:0] SEG;
wire [4:0] LED_SW;
wire [7:0] LED_BCD;

// Instantiate DUT
top_lab5 dut (
    .CLK      (CLK),
    .SW       (SW),
    .BTN0     (BTN0),
    .BTN1     (BTN1),
    .AN       (AN),
    .SEG      (SEG),
    .LED_SW   (LED_SW),
    .LED_BCD  (LED_BCD)
);

// 100 MHz clock
initial begin
    CLK = 0;
    forever #5 CLK = ~CLK;
end

// Display time in nanoseconds
initial begin
    $timeformat(-9, 0, " ns", 12);
end

initial begin
    // INITIAL RESET
    BTN0 = 1'b1;
    SW   = 5'd0;
    BTN1 = 1'b0;


    #20;
    // Release reset: BTN0=0 -> rst_n=1
    BTN0 = 1'b0;
    $display("%0t: Released reset, LED_BCD = %0d (tens=%0d, units=%0d)",
        $time, LED_BCD, LED_BCD[7:4], LED_BCD[3:0]);

    // Select a mid-range speed for visible counting (e.g. SW=4)
    SW = 5'd4;
    $display("%0t: SW set to %0b", $time, SW);


    // Direction up
    BTN1 = 1'b1;
    $display("%0t: Direction = Up", $time);

    // Monitor 10 increments
    repeat (10) begin
        #320;
        $display("%0t: LED_BCD = %0d (tens=%0d, units=%0d)",
            $time, LED_BCD, LED_BCD[7:4], LED_BCD[3:0]);
    end
end
endmodule
```

 
```
# run 1000ns
20 ns: Released reset, LED_BCD = 0 (tens=0, units=0)
20 ns: SW set to 100
20 ns: Direction = Up
340 ns: LED_BCD = 153 (tens=9, units=9)
660 ns: LED_BCD = 152 (tens=9, units=8)
980 ns: LED_BCD = 151 (tens=9, units=7)
```



## Hardware Results

 

 We can see that the corresponding LEDs of the first 4 switches are lit up. LEDs 5-8 are for the ones digit and 9-12 are for the tens digit and we can see that we currently have 1001, or 9, for LEDs 5-8 and 0110, or 6, for LEDs 9-12 which displays 69.




We can see that we currently have 0110, or 6, for LEDs 5-8 and 0011, or 3, for LEDs 9-12 which displays 36.

Cascading, direction and reset functionalities shown in the demo.



# Screenshots

## Schematics

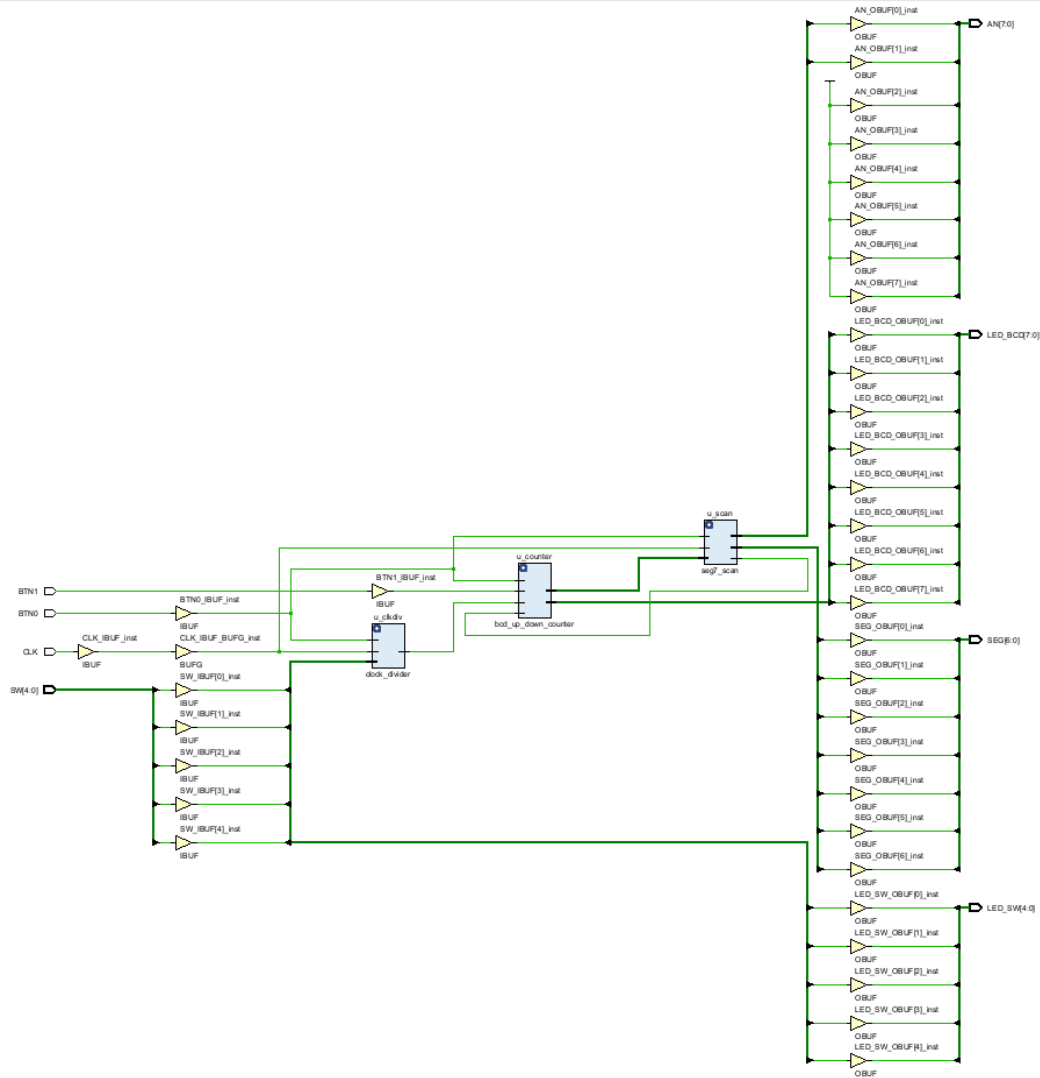

## LUT & FF

LUT	FF
24	66
24	66


## Timing Summary

Setup		Hold		Pulse Width	
Worst Negative Slack (WNS):	7.338 ns	Worst Hold Slack (WHS):	0.252 ns	Worst Pulse Width Slack (WPWS):	4.500 ns
Total Negative Slack (TNS):	0.000 ns	Total Hold Slack (THS):	0.000 ns	Total Pulse Width Negative Slack (TPWS):	0.000 ns
Number of Failing Endpoints:	0	Number of Failing Endpoints:	0	Number of Failing Endpoints:	0
Total Number of Endpoints:	58	Total Number of Endpoints:	58	Total Number of Endpoints:	59
 
## Power Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 0.129 W  
**Design Power Budget:** Not Specified  
**Process:** typical  
**Power Budget Margin:** N/A  
**Junction Temperature:** 25.6°C



## Conclusion

This lab delved into designing and testing a digital system using Verilog and the Nexys A7 FPGA board. We built a working two-digit BCD up/down counter that responds to button presses, changes speed based on switch input, and displays the result on a 7-segment display using multiplexing. By breaking the design into smaller modules like the clock divider, mux, BCD counter, and 7-segment scanner, we were able to test each part individually and then connect everything together in the top module. The LEDs also helped us verify the internal values in binary. Overall, the lab helped reinforce how to handle clock division, binary counting, and real-time output on an FPGA, and it was a solid example of modular digital design.

## **Contributions**

Faris (50%) - Source code, helped with lab report

Nicholas (50%) - Testbench, handled simulations, helped with report, demo