

# **ECE3300L**

## **Lab 2**

**By Justin Wong, Hector Garibay**

Summer 2025

Report Date: June 25, 2025

## Objective

We will design, simulate, and implement a 4-to-16 decoder with an enable input.

When enabled, exactly one of 16 outputs goes HIGH based on the 4-bit input; when disabled, all outputs are LOW.

## Verilog Code:

### Behavioral Code:

```
module decoder4x16_behav (
    input wire [3:0] A,
    input wire      E,
    output reg  [15:0] Y
);
    // [GREEN] reset outputs every combinational evaluation
    always @(*) begin
        Y = 16'b0;

        // [BLUE] decode only when enabled
        if (E) begin
            // [ORANGE] mapping a to y[i]
            case (A)
                4'b0000: Y = 16'b0000_0000_0000_0001; // Y0
                4'b0001: Y = 16'b0000_0000_0000_0010; // Y1
                4'b0010: Y = 16'b0000_0000_0000_0100; // Y2
                4'b0011: Y = 16'b0000_0000_0000_1000; // Y3
                4'b0100: Y = 16'b0000_0000_0001_0000; // Y4
                4'b0101: Y = 16'b0000_0000_0010_0000; // Y5
                4'b0110: Y = 16'b0000_0000_0100_0000; // Y6
                4'b0111: Y = 16'b0000_0000_1000_0000; // Y7
                4'b1000: Y = 16'b0000_0001_0000_0000; // Y8
                4'b1001: Y = 16'b0000_0010_0000_0000; // Y9
                4'b1010: Y = 16'b0000_0100_0000_0000; // Y10
                4'b1011: Y = 16'b0000_1000_0000_0000; // Y11
                4'b1100: Y = 16'b0001_0000_0000_0000; // Y12
                4'b1101: Y = 16'b0010_0000_0000_0000; // Y13
                4'b1110: Y = 16'b0100_0000_0000_0000; // Y14
                4'b1111: Y = 16'b1000_0000_0000_0000; // Y15
                default: Y = 16'b0;
            endcase
        end
    end
endmodule
```

### Gate-Level Code:

```
module decoder4x16_gate (
    input wire [3:0] A, // A[3] -> A[0] from SW3 -> SW0
    input wire      E, // Enable from SW4
    output wire [15:0] Y // outputs to LD15 -> LD0
);
    // block enables
    wire en_low  = E & ~A[3]; // select Y[7:0]
    wire en_high = E &  A[3]; // select Y[15:8]

    // instantiate two 3-to-8 decoders
    dec3to8_gate low_block (.a(A[2:0]), .en(en_low), .y(Y[7:0]));
    dec3to8_gate high_block (.a(A[2:0]), .en(en_high), .y(Y[15:8]));
endmodule

// 3-to-8 decoder gate implementation


module dec3to8_gate (
    input wire [2:0] a,
    input wire      en,
    output wire [7:0] y
);
    /* assign outputs based on enable and inputs.*/
    assign y[0] = en & ~a[2] & ~a[1] & ~a[0];
    assign y[1] = en & ~a[2] & ~a[1] &  a[0];
    assign y[2] = en & ~a[2] &  a[1] & ~a[0];
    assign y[3] = en & ~a[2] &  a[1] &  a[0];
    assign y[4] = en &  a[2] & ~a[1] & ~a[0];
    assign y[5] = en &  a[2] & ~a[1] &  a[0];
    assign y[6] = en &  a[2] &  a[1] & ~a[0];
    assign y[7] = en &  a[2] &  a[1] &  a[0];
endmodule
```

Simulation:

Test bench Code

```
5 | reg [3:0] A;
6 | reg E;
7 | wire [15:0] Y;
8 |
9 |
10 | decoder4x16_behav test(.A(A), .E(E), .Y(Y)); // instantiating wit
11 |
12 |
13 | integer i;
14 |
15 | initial begin
16 |
17 | // Check that outputs stay LOW when disabled
18 | E = 1'b0;
19 | A = 4'b0000;
20 | #10;
21 | if (Y !== 16'b0) $fatal(1, "FAIL: Y not zero when E=0"); // if 1
22 | $display("PASS: E=0 forces Y=0");
23 |
24 | //all 16 input patterns with enable HIGH
25 | E = 1'b1; // set Enable on
26 | // looping through possible input values
27 | for (i = 0; i < 16; i = i + 1) begin
28 |     A = i[3:0];
29 |     #10; // 10 unit delay
30 |     if (Y !== (16'b1 << i)) // checking if output Y is not equal
31 |         //if not, print error
32 |         $fatal(1,
33 |             "FAIL: A=%0h expected=%016b got=%016b",
34 |             A, (16'b1 << i), Y
35 |         );
36 | end
37 | $display("PASS: All 16 combinations decoded correctly");
38 |
39 | // display message that all tests passed
40 | $display("\nALL TESTS PASSED\n");
```

Waveform sample

 

Implementation:

Utilization Table:

Resource	Utilization	Available	Utilization %
LUT	8	63400	0.01
IO	21	210	10.00

Timing Summary

Design Timing Summary			
Setup		Hold	Pulse Width
Worst Negative Slack (WNS):	inf	Worst Hold Slack (WHS):	inf
Total Negative Slack (TNS):	0.000 ns	Total Hold Slack (THS):	0.000 ns
Number of Failing Endpoints:	0	Number of Failing Endpoints:	0
Total Number of Endpoints:	16	Total Number of Endpoints:	16

## Video:

<https://youtu.be/CyE5YjkD8ik>

## Reflection:

In this lab, we developed a Verilog module for the Nexys A7 100T Board. The goal of this lab was to create a 4-16 decoder with an enable switch. This was accomplished by creating a Verilog module. We simulated our code using a separate testbench that we created. When the enable is LOW, all LEDs should be turned off, when the enable is HIGH, a single LED will turn on. The combination of the four switches on the board represents a number in binary. LEDs 2-16 are used to represent a 4-bit number.

## Contributions:

Justin Wong: XDC, decoder4x16, behavioral code, testbench code, report. 50% for all.

Hector Garibay: XDC, decoder4x16, behavioral code, testbench code, report. 50% for all.