



Department of Electrical and Computer Engineering

ECE 3300L Section 1

Lab 4 – Switch-to-7-Segment Display Interface on Nexys A7

Bryan Liu ID: 016695471

Jaden Yeremenko ID: 016414528

July 9, 2025

## Design:

## Src code:

```
`timescale 1ns/1ps
module seg7_driver(
    input      clk,
    input      rst_n,
    input  [15:0] SW,          // Eight 4-bit values
    output reg [6:0] Cnode,    // Segments a-g (active low)
    output      dp,           // Decimal point (tie-off)
    output  [7:0] AN,          // Digit enables (active low)
    output  [15:0] LED
);

    // 1. Scan counter for ~200 Hz digit rate
    reg [19:0] cnt;
    always @(posedge clk or negedge rst_n)
        if (!rst_n) cnt <= 0;
        else      cnt <= cnt + 1;
    wire [2:0] scan = cnt[19:17];

    // 2. Pick the current 4-bit nibble
    reg [3:0] digit;
    always @(*) begin
        case (scan)
            3'd0: digit = SW[3:0];
            3'd1: digit = SW[7:4];
            3'd2: digit = SW[11:8];
            3'd3: digit = SW[15:12];
            3'd4: digit = SW[3:0];
            3'd5: digit = SW[7:4];
            3'd6: digit = SW[11:8];
            3'd7: digit = SW[15:12];
            default: digit = 4'd0;
        endcase
    end

    // 3. 4-bit → 7-segment (common-anode, active-low)
    always @(*) begin
        case (digit)
            4'd0: Cnode = 7'b0000001;
            4'd1: Cnode = 7'b1001111;
            4'd2: Cnode = 7'b0010010;
```

```

4'd3: Cnode = 7'b0000110;
4'd4: Cnode = 7'b1001100;
4'd5: Cnode = 7'b0100100;
4'd6: Cnode = 7'b0100000;
4'd7: Cnode = 7'b0001111;
4'd8: Cnode = 7'b0000000;
4'd9: Cnode = 7'b0001100;
4'd10: Cnode = 7'b0001000;
4'd11: Cnode = 7'b1100000;
4'd12: Cnode = 7'b0110001;
4'd13: Cnode = 7'b1000010;
4'd14: Cnode = 7'b0110000;
4'd15: Cnode = 7'b0111000;
default: Cnode = 7'b1111111;
endcase
end


// 4. Decimal point always off
assign dp = 1'b1;

// 5. Enable one AN at a time (active-low)
reg [7:0] AN_tmp;
always @(*) begin
    AN_tmp = 8'hFF;
    AN_tmp[scan] = 1'b0;
end
assign AN = AN_tmp;
assign LED = SW;
endmodule


```

Simulation:

Waveform:

 

Schematic:

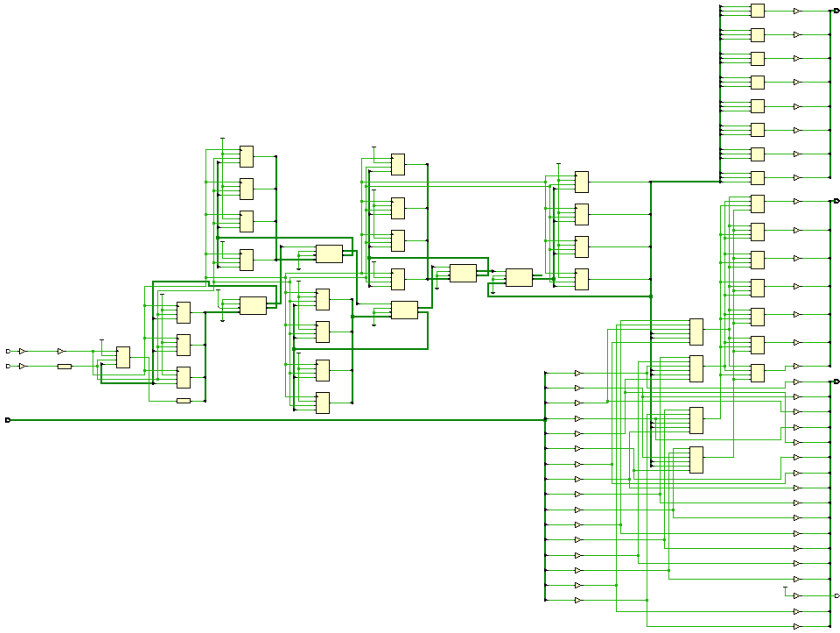

# Implementation:

## Design Timing Summary


Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 7.437 ns	Worst Hold Slack (WHS): 0.324 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 20	Total Number of Endpoints: 20	Total Number of Endpoints: 21
All user specified timing constraints are met.		

## Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.		<b>On-Chip Power</b>	
<b>Total On-Chip Power:</b>	<b>0.126 W</b>		
<b>Design Power Budget:</b>	<b>Not Specified</b>		
<b>Process:</b>	typical		
<b>Power Budget Margin:</b>	N/A		
<b>Junction Temperature:</b>	<b>25.6°C</b>		
Thermal Margin:	59.4°C (12.9 W)		
Ambient Temperature:	25.0 °C		
Effective ΘJA:	4.6°C/W		
Power supplied to off-chip devices:	0 W		
Confidence level:	Low		
<a href="#">Launch Power Constraint Advisor</a> to find and fix invalid switching activity			

Summary

Resource	Utilization	Available	Utilization %
LUT	14	63400	0.02
FF	20	126800	0.02
IO	50	210	23.81

 

**Contributions:**

**Bryan Liu:** Src code + Testbench code + xdc constraint file: 50%

**Jaden Yermenko:** Synthesis + Implementation +Testing and Debugging: 50%