

Lab 5  
3300L.E01

BCD Up/Down Counter on  
7-Segment Display

Group U  
Justin Herrera - Pandarb004  
Nathan Rahbar - 9athan

# Design

## Constraints

For Lab 4, our team implemented the 7 segment displays on the Nexys A7, which were controlled through switches. We had a constraints file in which we initialized our switches, buttons, LEDs, and 7 segment displays.

```
## Clock signal
set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 } [get_ports { CLK }];
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {CLK}];

## Switches
set_property -dict { PACKAGE_PIN J15      IOSTANDARD LVCMOS33 } [get_ports { SW[0] }];
set_property -dict { PACKAGE_PIN L16      IOSTANDARD LVCMOS33 } [get_ports { SW[1] }];
set_property -dict { PACKAGE_PIN M13      IOSTANDARD LVCMOS33 } [get_ports { SW[2] }];
set_property -dict { PACKAGE_PIN R15      IOSTANDARD LVCMOS33 } [get_ports { SW[3] }];
set_property -dict { PACKAGE_PIN R17      IOSTANDARD LVCMOS33 } [get_ports { SW[4] }];

## LEDs
set_property -dict { PACKAGE_PIN H17      IOSTANDARD LVCMOS33 } [get_ports { LED[0] }];
set_property -dict { PACKAGE_PIN K15      IOSTANDARD LVCMOS33 } [get_ports { LED[1] }];
set_property -dict { PACKAGE_PIN J13      IOSTANDARD LVCMOS33 } [get_ports { LED[2] }];
set_property -dict { PACKAGE_PIN N14      IOSTANDARD LVCMOS33 } [get_ports { LED[3] }];
set_property -dict { PACKAGE_PIN R18      IOSTANDARD LVCMOS33 } [get_ports { LED[4] }];
set_property -dict { PACKAGE_PIN V17      IOSTANDARD LVCMOS33 } [get_ports { LED[5] }];
set_property -dict { PACKAGE_PIN U17      IOSTANDARD LVCMOS33 } [get_ports { LED[6] }];
set_property -dict { PACKAGE_PIN U16      IOSTANDARD LVCMOS33 } [get_ports { LED[7] }];
set_property -dict { PACKAGE_PIN V16      IOSTANDARD LVCMOS33 } [get_ports { LED[8] }];
set_property -dict { PACKAGE_PIN T15      IOSTANDARD LVCMOS33 } [get_ports { LED[9] }];
set_property -dict { PACKAGE_PIN U14      IOSTANDARD LVCMOS33 } [get_ports { LED[10] }];
set_property -dict { PACKAGE_PIN T16      IOSTANDARD LVCMOS33 } [get_ports { LED[11] }];
set_property -dict { PACKAGE_PIN V15      IOSTANDARD LVCMOS33 } [get_ports { LED[12] }];
```

```

## 7-Segment Display (Critical Updates)
# Segment lines
set_property -dict { PACKAGE_PIN T10    IOSTANDARD LVCMOS33 } [get_ports { SEG[0] }];
set_property -dict { PACKAGE_PIN R10    IOSTANDARD LVCMOS33 } [get_ports { SEG[1] }];
set_property -dict { PACKAGE_PIN K16    IOSTANDARD LVCMOS33 } [get_ports { SEG[2] }];
set_property -dict { PACKAGE_PIN K13    IOSTANDARD LVCMOS33 } [get_ports { SEG[3] }];
set_property -dict { PACKAGE_PIN P15    IOSTANDARD LVCMOS33 } [get_ports { SEG[4] }];
set_property -dict { PACKAGE_PIN T11    IOSTANDARD LVCMOS33 } [get_ports { SEG[5] }];
set_property -dict { PACKAGE_PIN L18    IOSTANDARD LVCMOS33 } [get_ports { SEG[6] }];

# Anode lines - NOW CONTROLLING ALL DIGITS
set_property -dict { PACKAGE_PIN J17    IOSTANDARD LVCMOS33 } [get_ports { AN[0] }]; # Rightmost digit
set_property -dict { PACKAGE_PIN J18    IOSTANDARD LVCMOS33 } [get_ports { AN[1] }];
set_property -dict { PACKAGE_PIN T9     IOSTANDARD LVCMOS33 } [get_ports { AN[2] }];
set_property -dict { PACKAGE_PIN J14    IOSTANDARD LVCMOS33 } [get_ports { AN[3] }];
set_property -dict { PACKAGE_PIN P14    IOSTANDARD LVCMOS33 } [get_ports { AN[4] }];
set_property -dict { PACKAGE_PIN T14    IOSTANDARD LVCMOS33 } [get_ports { AN[5] }];
set_property -dict { PACKAGE_PIN K2     IOSTANDARD LVCMOS33 } [get_ports { AN[6] }];
set_property -dict { PACKAGE_PIN U13    IOSTANDARD LVCMOS33 } [get_ports { AN[7] }]; # Leftmost digit

## Buttons
set_property -dict { PACKAGE_PIN N17    IOSTANDARD LVCMOS33 } [get_ports { BTN0 }];
set_property -dict { PACKAGE_PIN M18    IOSTANDARD LVCMOS33 } [get_ports { BTN1 }];

```

## Driver Module

```

s\timescale 1ns / 1ps

module top_lab5 (
    input        CLK,
    input        BTN0,
    input        BTN1,
    input  [4:0]  SW,
    output [12:0] LED,
    output [1:0]  AN,
    output [6:0]  SEG
);
    wire [31:0] cnt;
    wire      clk_out;
    wire [3:0] lsb0;
    wire [3:0] lsb1;

    clock_divider u_div (
        .clk (CLK),
        .rst_n (!BTN0),
        .cnt (cnt)
    );

    mux32x1 u_mux (
        .cnt (cnt),
        .sel (SW),
        .clk_out (clk_out)
    );

    bcd_up_down_counter u_bcd (
        .clk (clk_out),
        .rst_n (!BTN0),
        .dir (BTN1),
        .lsb0 (lsb0),
        .lsb1 (lsb1)
    );

    seg7_scan u_scan (
        .clk (CLK),
        .rst_n (!BTN0),
        .lsb0 (lsb0),

```


```

seg7_scan u_scan (
    .clk (CLK),
    .rst_n (!BTN0),
    .lsb0 (lsb0),
    .lsb1 (lsb1),
    .seg (SEG),
    .an (AN)
);

assign LED[4:0]      = SW;
assign LED[8:5]      = lsb0;
assign LED[12:9]     = lsb1;

```

## Testbench

 

## Test Bench Code

```
timescale 1ns / 1ps

module bcd_up_down_counter_tb();
    reg clk = 0;
    reg rst_n;
    reg dir;
    wire [3:0] lsb0, lsb1;

    bcd_up_down_counter tb (
        .clk(clk),
        .rst_n(rst_n),
        .dir(dir),
        .lsb0(lsb0),
        .lsb1(lsb1)
    );


    always #5 clk = ~clk;

    initial begin
        rst_n = 0; dir = 1; #20;
        rst_n = 1; #100;


        dir = 0; #100;
        $finish;
    end
endmodule
```

Our test bench is used to test the driver module.

## Implementation

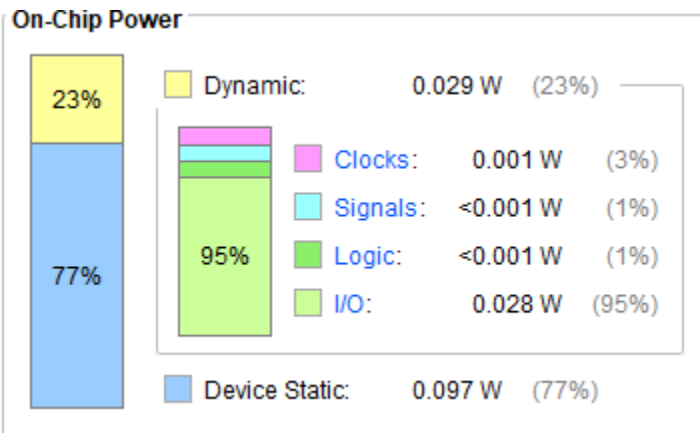

Resource	Utilization	Available	Utilization %
LUT	25	63400	0.04
FF	56	126800	0.04
IO	30	210	14.29

 

In our implementation, we were able to analyze utilization and see our Flip Flop and LUT counts. This is a simple design, so utilization was not particularly high. We do see 95% of power utilization comes from I/O, which makes sense because we use all switches.

## Contributions

Justin - Testbench, Report. - 50%

Nathan - Driver Module, Constraints. - 50%

## Demo

<https://youtu.be/rcLzSD2aFzM>