

# **ECE3300L**

## **Lab 7**

**By Justin Wong, Hector Garibay**

Summer 2025

Report Date: July 6, 2025

# Objective

The objective of this lab is to design and implement a 16-bit combinational barrel shifter on an FPGA that supports logical and rotational shifts in both directions, left and right, by a variable amount from 0 to 15. Inputs are provided via slide switches and push buttons, with outputs displayed on a 7-segment display. The system includes a debounced control interface, an asynchronous reset, and visual feedback through LEDs.

## Top Lab Code Snippet:

```
// Debounced toggles
wire dir_toggle, rot_toggle, shamt0_toggle, shamt1_toggle;
debounce_toggle deb_dir(.CLK_1KHZ(clk_1khz), .BTN(BTNU), .BTN_TOGGLE(dir_toggle));
debounce_toggle deb_rot(.CLK_1KHZ(clk_1khz), .BTN(BTND), .BTN_TOGGLE(rot_toggle));
debounce_toggle deb_shamt0(.CLK_1KHZ(clk_1khz), .BTN(BTNL), .BTN_TOGGLE(shamt0_toggle));
debounce_toggle deb_shamt1(.CLK_1KHZ(clk_1khz), .BTN(BTNR), .BTN_TOGGLE(shamt1_toggle));

// SHAMT[3:2] from btnc
wire [1:0] shamt_upper;
shamt_counter cnt(
    .CLK(clk_1khz),
    .BTNC(BTNC),
    .shamt_upper(shamt_upper)
);

wire [3:0] shamt = {shamt_upper, shamt1_toggle, shamt0_toggle};

// Barrel shifter
wire [15:0] barrel_out;
barrel_shifter16 shifter(
    .data_in(SW),
    .shamt(shamt),
    .dir(dir_toggle),
    .rotate(rot_toggle),
    .data_out(barrel_out)
);

// hex to 7seg
wire [6:0] seg0, seg1, seg2, seg3;
hex_to_7seg h0(.hex_in(barrel_out[3:0]), .SEG(seg0));
hex_to_7seg h1(.hex_in(barrel_out[7:4]), .SEG(seg1));
hex_to_7seg h2(.hex_in(barrel_out[11:8]), .SEG(seg2));
hex_to_7seg h3(.hex_in(barrel_out[15:12]), .SEG(seg3));
wire [6:0] blank = 7'b1111111;
```

## debounce\_toggle Snippet:

```
module debounce_toggle(  
    input CLK_1KHZ,  
    input BTN,  
    output reg BTN_TOGGLE  
);  
    reg [2:0] shift_reg = 0;  
    reg last_state = 0;  
    reg BTN_TOGGLE = 0;  
  
    always @(posedge CLK_1KHZ) begin  
        shift_reg <= {shift_reg[1:0], BTN};  
        if (shift_reg == 3'b111 && !last_state) begin  
            BTN_TOGGLE <= ~BTN_TOGGLE;  
            last_state <= 1;  
        end else if (shift_reg == 3'b000) begin  
            last_state <= 0;  
        end  
    end  
end  
endmodule
```

## clock\_divider\_fixed Snippet:

```
`timescale 1ns / 1ps  
module clock_divider_fixed(  
    input CLK,  
    output reg CLK_2HZ,  
    output reg CLK_1KHZ  
);  
    parameter div_2hz = 26'd25_000_000;  
    parameter div_1khz = 17'd50_000;  
    reg [25:0] cnt_2hz = 0;  
    reg [16:0] cnt_1khz = 0;  
  
    always @(posedge CLK) begin  
        if (cnt_2hz == div_2hz-1) begin  
            cnt_2hz <= 0;  
            CLK_2HZ <= ~CLK_2HZ; // toggle output  
        end else begin  
            cnt_2hz <= cnt_2hz + 1; // else count up  
        end  
    end  
  
    always @(posedge CLK) begin  
        if (cnt_1khz == div_1khz-1) begin  
            cnt_1khz <= 0;  
            CLK_1KHZ <= ~CLK_1KHZ; // toggle output  
        end else begin  
            cnt_1khz <= cnt_1khz + 1; // else count up  
        end  
    end  
end  
endmodule
```

## shamt\_counter Code:

```
module shamt_counter(  
    input CLK,  
    input BTNC,  
    output reg [1:0] shamt_upper  
);  
    reg btnc_last = 0;  
    always @(posedge CLK) begin  
        btnc_last <= BTNC;  
        if (BTNC & ~btnc_last)  
            shamt_upper <= shamt_upper + 1;  
    end  
endmodule
```

## barrel\_shifter16 Code:

```
    output [15:0] data_out  
);  
  
    wire [15:0] stage1, stage2, stage3, stage4;  
  
    // shift 1 bit  
    assign stage1 = shamt[0] ?  
        (dir ?  
            (rotate ? {data_in[0], data_in[15:1]} : {1'b0, data_in[15:1]}) :  
            (rotate ? {data_in[14:0], data_in[15]} : {data_in[14:0], 1'b0})  
        ) : data_in;  
  
    //shift 2 bits  
    assign stage2 = shamt[1] ?  
        (dir ?  
            (rotate ? {stage1[1:0], stage1[15:2]} : {2'b00, stage1[15:2]}) :  
            (rotate ? {stage1[13:0], stage1[15:14]} : {stage1[13:0], 2'b00})  
        ) : stage1;  
  
    //shift 4 bits  
    assign stage3 = shamt[2] ?  
        (dir ?  
            (rotate ? {stage2[3:0], stage2[15:4]} : {4'b0000, stage2[15:4]}) :  
            (rotate ? {stage2[11:0], stage2[15:12]} : {stage2[11:0], 4'b0000})  
        ) : stage2;  
  
    //shift 8 bits  
    assign stage4 = shamt[3] ?  
        (dir ?  
            (rotate ? {stage3[7:0], stage3[15:8]} : {8'b00000000, stage3[15:8]}) :  
            (rotate ? {stage3[7:0], stage3[15:8]} : {stage3[7:0], 8'b00000000})  
        ) : stage3;  
  
    assign data_out = stage4;  
  
endmodule
```

## Hex\_to\_7seg Code:

```
module hex_to_7seg(  
    input [3:0] hex_in,  
    output reg [6:0] SEG  
);  
    always @(*) begin  
        case(hex_in)  
            4'h0: SEG = 7'b1000000;  
            4'h1: SEG = 7'b1111001;  
            4'h2: SEG = 7'b0100100;  
            4'h3: SEG = 7'b0110000;  
            4'h4: SEG = 7'b0011001;  
            4'h5: SEG = 7'b0010010;  
            4'h6: SEG = 7'b0000010;  
            4'h7: SEG = 7'b1111000;  
            4'h8: SEG = 7'b0000000;  
            4'h9: SEG = 7'b0010000;  
            4'hA: SEG = 7'b0001000;  
            4'hB: SEG = 7'b0000011;  
            4'hC: SEG = 7'b1000110;  
            4'hD: SEG = 7'b0100001;  
            4'hE: SEG = 7'b0000110;  
            4'hF: SEG = 7'b0001110;  
        endcase  
    end  
endmodule
```

## Test Bench Code Snippet

### barrel\_shifter16\_tb

```
initial
begin
    data_in = 16'b1010010110100101;
    shamt = 4'd0;    //left shift
    dir = 0;
    rotate = 0;
    #100

    shamt = 4'd0;    //right shift
    dir = 1;
    rotate = 0;
    #100

    shamt = 4'd0;    //rotate left
    dir = 0;
    rotate = 1;
    #100

    shamt = 4'd0;    //rotate right
    dir = 1;
    rotate = 1;
    #100
```

### debounce\_toggle\_tb

```
reg CLK_1KHZ;
reg BTN;

wire BTN_TOGGLE;

debounce_toggle dut(
    .CLK_1KHZ(CLK_1KHZ),
    .BTN(BTN),
    .BTN_TOGGLE(BTN_TOGGLE)
);

always #5 CLK_1KHZ = ~CLK_1KHZ;
initial begin
    CLK_1KHZ = 0;
    BTN = 0;

    #50
    BTN = 1;    //normal press
    #100
    BTN = 0;
    #500

    BTN = 1;    //bounce
    #10
    BTN = 0;
    #10
    BTN = 1;
    #10
    BTN = 0;
    #10


    $finish;
end
endmodule
```

## 7seg-scan8\_tb


```
module seg7_scan8(  
    input CLK_1KHZ,          // 1kHz clock  
    input [6:0] SEG0,         // Segment data for digit 0  
    input [6:0] SEG1,         // Segment data for digit 1  
    input [6:0] SEG2,         // Segment data for digit 2  
    input [6:0] SEG3,         // Segment data for digit 3  
    input [6:0] SEG4,         // Segment data for digit 4  
    input [6:0] SEG5,         // Segment data for digit 5  
    input [6:0] SEG6,         // Segment data for digit 6  
    input [6:0] SEG7,         // Segment data for digit 7  
    output reg [7:0] AN,       // Anode enable signals  
    output reg [6:0] SEG       // Current segment output  
);  
  
    reg [2:0] scan_cnt = 0;    // 3-bit counter for scanning  
  
    // Increment scan counter on each clock edge  
    always @(posedge CLK_1KHZ) begin  
        scan_cnt <= scan_cnt + 1;  
    end  
  
    always @(*) begin  
        case(scan_cnt)  
            3'd0: begin AN = 8'b11111110; SEG = SEG0; end // Enable digit 0  
            3'd1: begin AN = 8'b11111101; SEG = SEG1; end // Enable digit 1  
            3'd2: begin AN = 8'b11111011; SEG = SEG2; end // Enable digit 2  
            3'd3: begin AN = 8'b11110111; SEG = SEG3; end // Enable digit 3  
            3'd4: begin AN = 8'b11101111; SEG = SEG4; end // Enable digit 4  
            3'd5: begin AN = 8'b11011111; SEG = SEG5; end // Enable digit 5  
            3'd6: begin AN = 8'b10111111; SEG = SEG6; end // Enable digit 6  
            3'd7: begin AN = 8'b01111111; SEG = SEG7; end // Enable digit 7  
        endcase  
    end  
endmodule
```

## Simulation:


### Debounce TB waveform

 

### Barrel Shifter TB waveform

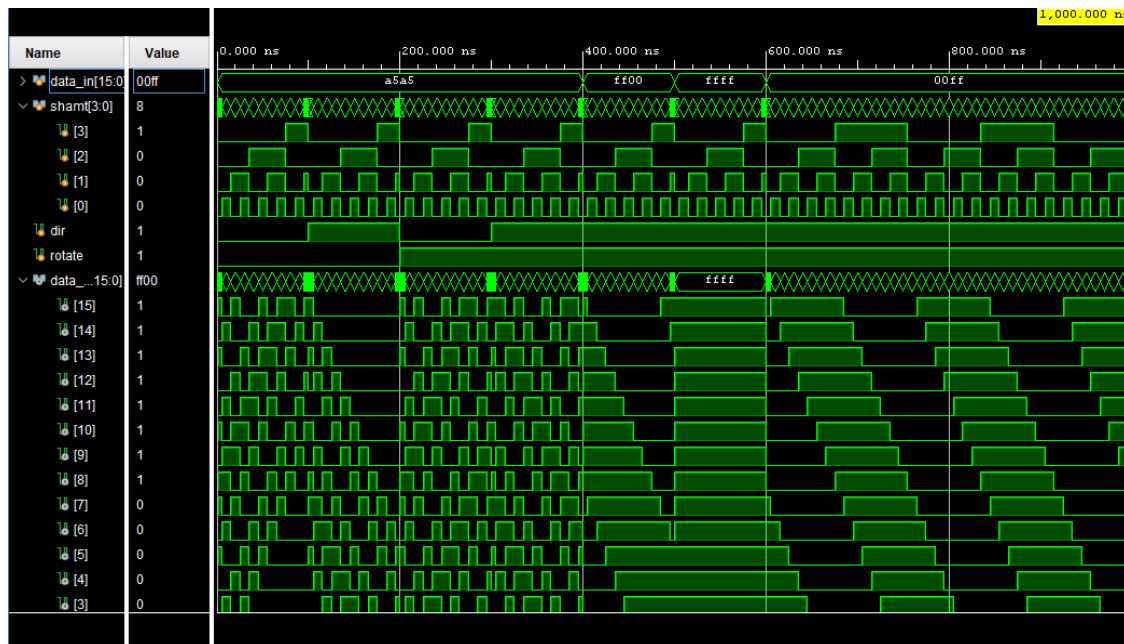

### seg7\_scan8 testbench

 



## Implementation:

Utilization Table:

Name	Slice LUTs (63400)	Slice Registers (126800)	Slice (15850)	LUT as Logic (63400)	Bonded IOB (210)	BUFGCTRL (32)
top_lab7	103	44	38	103	45	1
deb_shamt0 (debounce_toggle_1)	84	5	29	84	0	0

Resource	Utilization	Available	Utilization %
LUT	103	63400	0.16
FF	44	126800	0.03
IO	45	210	21.43

Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 6.266 ns	Worst Hold Slack (WHS): 0.262 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 35	Total Number of Endpoints: 35	Total Number of Endpoints: 19

All user specified timing constraints are met.

## Video:

<https://youtu.be/gB2LnxQ3D1g>

## Contributions:

Justin Wong: XDC, Driver Code, testbench code, report. 50% for all.

Hector Garibay: XDC, Driver Code, testbench code, report. 50% for all.