

3300 Lab 3

16x1 Multiplexer Using Nested 2x1 MUXes with Debounced Toggle Select Control

Group C

Rohan Walia

Parsa Ghasemi

7/2/25

Code:

```
module mux2x1 (  
    input a, b,  
    input sel,  
    output y  
);  
    wire nsel, a1, b1;  
    not (nsel, sel);  
    and (a1, a, nsel);  
    and (b1, b, sel);  
    or (y, a1, b1);  
endmodule
```

```
module mux16x1 (  
    input [15:0] in,  
    input [3:0] sel,  
    output out  
);  
    wire [15:0] level1;  
    wire [7:0] level2;  
    wire [3:0] level3;  
  
    genvar i;  
    generate  
        for (i = 0; i < 8; i = i + 1)  
            mux2x1 m1 (.a(in[2*i]), .b(in[2*i+1]), .sel(sel[0]), .y(level1[i]));  
        for (i = 0; i < 4; i = i + 1)  
            mux2x1 m2 (.a(level1[2*i]), .b(level1[2*i+1]), .sel(sel[1]), .y(level2[i]));  
        for (i = 0; i < 2; i = i + 1)  
            mux2x1 m3 (.a(level2[2*i]), .b(level2[2*i+1]), .sel(sel[2]), .y(level3[i]));  
        mux2x1 m4 (.a(level3[0]), .b(level3[1]), .sel(sel[3]), .y(out));  
    endgenerate  
endmodule
```

```

module debounce (
    input clk,
    input btn_in,
    output reg btn_clean
);
    reg [2:0] shift_reg;

    always @(posedge clk) begin
        shift_reg <= {shift_reg[1:0], btn_in};
        if (shift_reg == 3'b111)
            btn_clean <= 1;
        else if (shift_reg == 3'b000)
            btn_clean <= 0;
        end
    endmodule

```

```

module toggle_switch (
    input clk,
    input rst,
    input btn_raw,
    output reg state
);
    wire btn_clean;
    reg btn_prev;

    debounce db (.clk(clk), .btn_in(btn_raw), .btn_clean(btn_clean));

    always @(posedge clk) begin
        if (rst) begin
            state <= 0;
            btn_prev <= 0;
        end else begin
            if (btn_clean && !btn_prev)
                state <= ~state;
            btn_prev <= btn_clean;
        end
    end
endmodule

```

```

module top_mux_lab3 (
    input clk,
    input rst,
    input [15:0] SW,
    input btnU, btnD, btnL, btnR,
    output LED0
);
    wire [3:0] sel;

    toggle_switch t0 (.clk(clk), .rst(rst), .btn_raw(btnD), .state(sel[0]));
    toggle_switch t1 (.clk(clk), .rst(rst), .btn_raw(btnR), .state(sel[1]));
    toggle_switch t2 (.clk(clk), .rst(rst), .btn_raw(btnL), .state(sel[2]));
    toggle_switch t3 (.clk(clk), .rst(rst), .btn_raw(btnU), .state(sel[3]));

    mux16x1 mux (.in(SW), .sel(sel), .out(LED0));
endmodule

```

```

module tb_top_mux_lab3;

    reg clk, rst, btnU, btnD, btnL, btnR;
    reg [15:0] SW;
    wire LED0;

    top_mux_lab3 uut(
        .clk(clk), .rst(rst),
        .btnU(btnU), .btnD(btnD), .btnL(btnL), .btnR(btnR),
        .SW(SW),
        .LED0(LED0)
    );

    // 100 MHz clock
    initial clk = 0;
    always #5 clk = ~clk;

    // Declare integer for loop
    integer i;

    // Tasks for each button
    task pressD; begin btnD = 1; #60; btnD = 0; #100; end endtask
    task pressR; begin btnR = 1; #60; btnR = 0; #100; end endtask
    task pressL; begin btnL = 1; #60; btnL = 0; #100; end endtask
    task pressU; begin btnU = 1; #60; btnU = 0; #100; end endtask

    initial begin
        SW = 0;
        btnU = 0; btnD = 0; btnL = 0; btnR = 0;
        rst = 1; #20; rst = 0;

        for (i = 0; i < 16; i = i + 1) begin
            // Reset selector logic
            rst = 1; #10; rst = 0;

            // Set current switch high
            SW = 16'b1 << i;

            // Press buttons to set sel = i
            if (i[0]) pressD();
            if (i[1]) pressR();
            if (i[2]) pressL();
            if (i[3]) pressU();
        end
    end
endmodule

```

```

        #100;

        $display("Testing sel = %0d | SW[%0d] = %b | LED0 = %b", i, i, SW[i], LED0);

        // Clear switch for next test
        SW = 0;
        #100;
    end


    $finish;
end

endmodule


```

This project implements a 16-to-1 multiplexer on the Nexys A7-100T FPGA using nested 2-to-1 muxes and debounced toggle controls. The design is modular, with a mux2x1 acting as the basic building block. These are nested in the mux16x1 module to select one of 16 input bits (SW[15:0]) based on a 4-bit select signal. The select signal is controlled using four pushbuttons (btnU, btnD, btnL, btnR), each connected to a toggle_switch module that toggles its state on each press, with clean signal edges ensured by the debounce module. The selected input value is displayed on LED0, allowing interactive switching between inputs via buttons. The top_mux_lab3 module integrates all components and connects them to the FPGA's physical interfaces.


Waveform screenshot (testing 0,1,2)

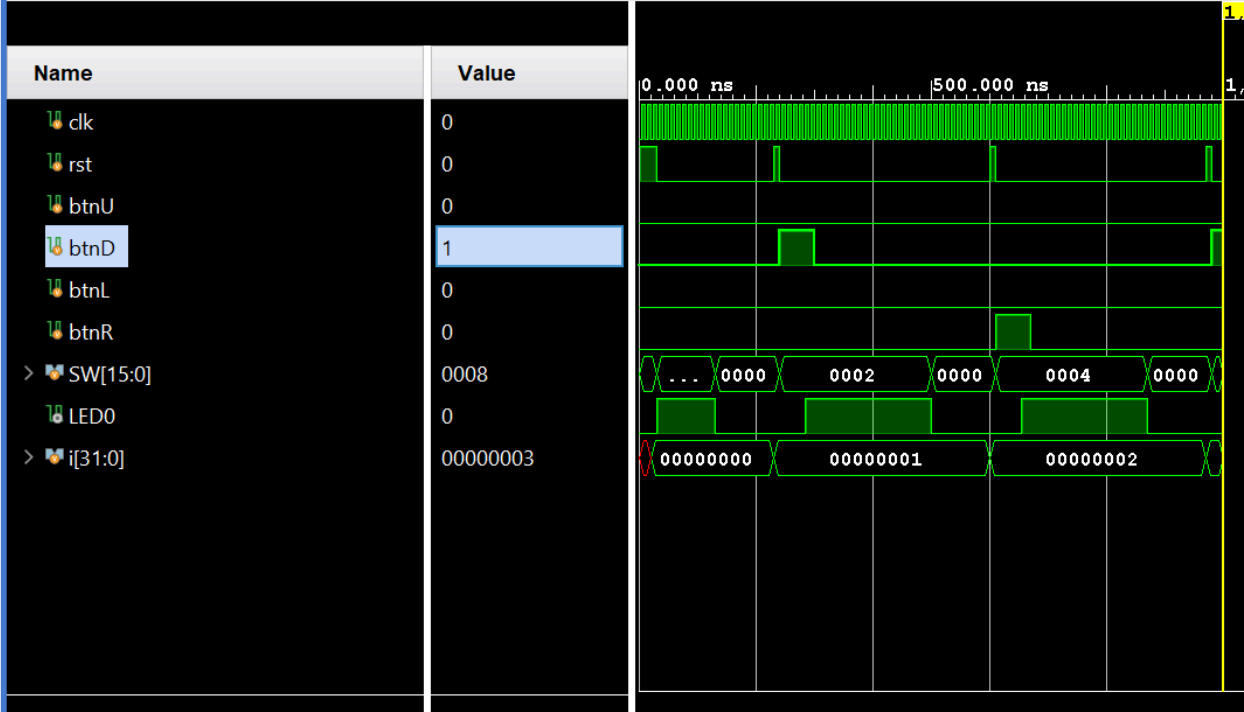


LUTs and FF screenshot:

 

Timing screenshot:

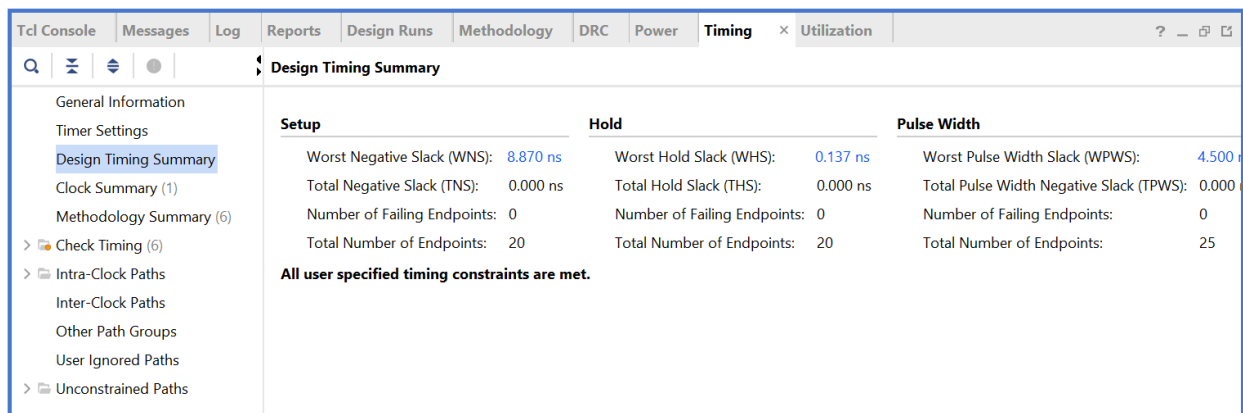

Power screenshot:

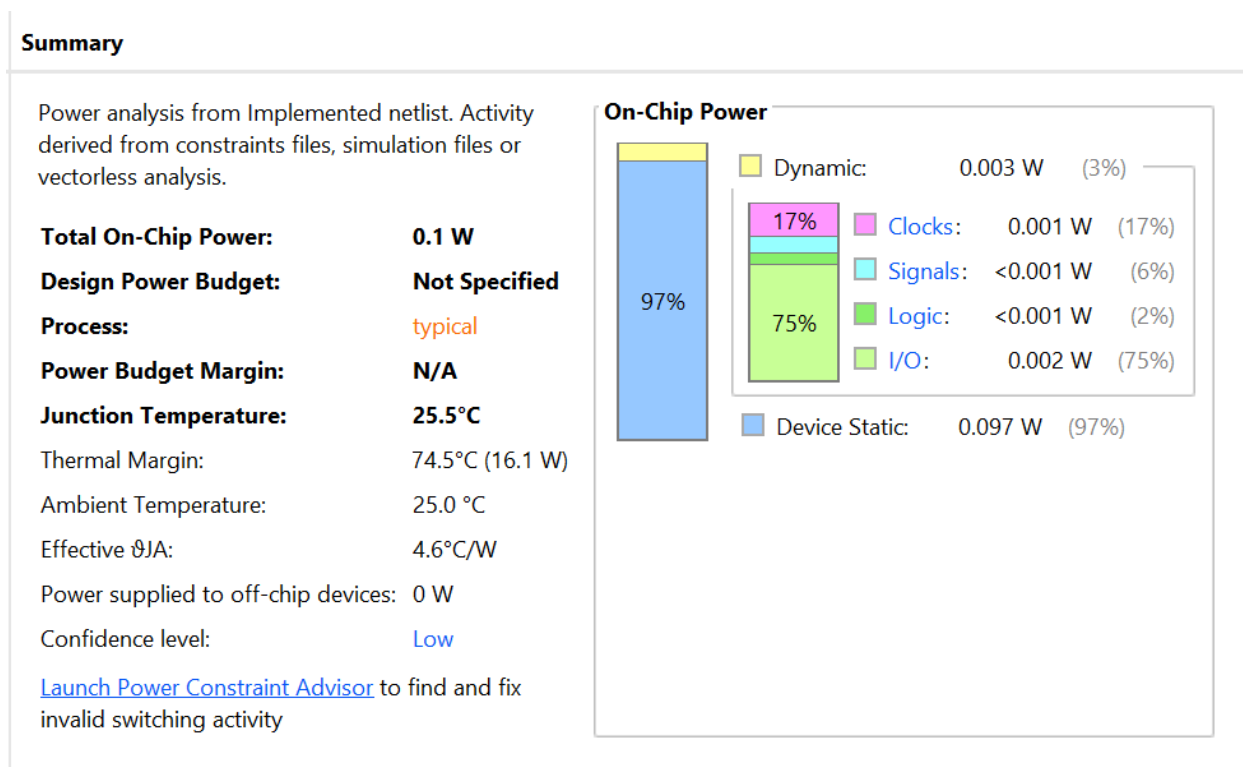

Contribution:

Rohan Walia (50%): Implementation, demo, testing, report

Parsa Ghasemi (50%): testbench code, verilog, report

Demo link: <https://youtu.be/ATRwbOBZEgo>