

Lab 2 Report

by

Jonathan Huynh #016137719

Adam Godfrey #015981472

Instructor: Dr. Mohamed Aly




Class: ECE 3300L.E02-OU - Verilog Design

June 25th, 2025

Summary:

In lab 2, we are tasked with designing, simulating, and implementing a 4-to-16 decoder along with an enable input on our Digilent Nexys A7-100T board.

Design:

<u>Behavior Level Snippet:</u>	<u>Gate Level Snippet:</u>
<pre>always @(*) begin Y = 16'b0; //  reset all outputs to 0 if (E) begin //  only decode when enabled case (A) 4'b0000: Y = 16'b0000_0000_0000_0001; //  output 0 4'b0001: Y = 16'b0000_0000_0000_0010; 4'b0010: Y = 16'b0000_0000_0000_0100; 4'b0011: Y = 16'b0000_0000_0000_1000; 4'b0100: Y = 16'b0000_0000_0001_0000; 4'b0101: Y = 16'b0000_0000_0010_0000; 4'b0110: Y = 16'b0000_0000_0100_0000; 4'b0111: Y = 16'b0000_0000_1000_0000; 4'b1000: Y = 16'b0000_0001_0000_0000; 4'b1001: Y = 16'b0000_0010_0000_0000; 4'b1010: Y = 16'b0000_0100_0000_0000; 4'b1011: Y = 16'b0000_1000_0000_0000; 4'b1100: Y = 16'b0001_0000_0000_0000; 4'b1101: Y = 16'b0010_0000_0000_0000; 4'b1110: Y = 16'b0100_0000_0000_0000; 4'b1111: Y = 16'b1000_0000_0000_0000; endcase end end</pre>	<pre>assign Y[0] = E & ~A[3] & ~A[2] & ~A[1] & ~A[0]; assign Y[1] = E & ~A[3] & ~A[2] & ~A[1] & A[0]; assign Y[2] = E & ~A[3] & ~A[2] & A[1] & ~A[0]; assign Y[3] = E & ~A[3] & ~A[2] & A[1] & A[0]; assign Y[4] = E & ~A[3] & A[2] & ~A[1] & ~A[0]; assign Y[5] = E & ~A[3] & A[2] & ~A[1] & A[0]; assign Y[6] = E & ~A[3] & A[2] & A[1] & ~A[0]; assign Y[7] = E & ~A[3] & A[2] & A[1] & A[0]; assign Y[8] = E & A[3] & ~A[2] & ~A[1] & ~A[0]; assign Y[9] = E & A[3] & ~A[2] & ~A[1] & A[0]; assign Y[10] = E & A[3] & ~A[2] & A[1] & ~A[0]; assign Y[11] = E & A[3] & ~A[2] & A[1] & A[0]; assign Y[12] = E & A[3] & A[2] & ~A[1] & ~A[0]; assign Y[13] = E & A[3] & A[2] & ~A[1] & A[0]; assign Y[14] = E & A[3] & A[2] & A[1] & ~A[0]; assign Y[15] = E & A[3] & A[2] & A[1] & A[0];</pre>


Simulation:

Testbench Description:


The testbench `tb_decoder4x16` is designed to verify the correct functionality of a 4-to-16 line decoder module (`decoder4x16_behav`). The decoder takes a 4-bit input `A`, an enable signal `E`, and produces a 16-bit one-hot output `Y`.

- Enable = 1 (Active Phase):
 - When the enable signal `E` is asserted (`E = 1`), the testbench iterates through all 16 possible values of the 4-bit input `A` (from 0000 to 1111)
 - For each input value, it checks that the decoder output `Y` produces a one-hot encoding by comparing it to $1 \ll A$
 - If the output does not match, the simulation halts with a failure message; otherwise, a success message is displayed.
- Enable = 0 (Disabled Phase):
 - After verifying all valid inputs with the decoder enabled, the testbench disables the decoder by setting `E = 0`
 - It again iterates over all values of `A` to ensure that the output `Y` remains zero regardless of the input
 - Any non-zero output is treated as an error and flagged.

Sample Waveform:

 

Zoomed in to 3 periods:

 

Implementation:

Resource Utilization Table

<u>Resource</u>	<u>Used</u>	<u>Available</u>	<u>Utilization</u>
LUTs	8	63,400	0.0126%
Registers (FFs)	0	126,800	0%
Bonded IOB	21	210	10%

Timing Summary:

Worst Negative Slack (WNS)	inf
Total Negative Slack (TNS)	0
Worst Hold Slack (WHS)	inf

Contributions:

<u>Team Member</u>	<u>Contribution</u>	<u>% Effort</u>
Jonathan Huynh	Demo, Debugging, Synthesis, Simulation, Written Report	50%
Adam Godfrey	Verilog Code, Test Bench, Written Report	50%

Link To Video:

<https://youtu.be/pE-wBqzjdYA>