



Department of Electrical and Computer Engineering

ECE 3300L Section 1

Lab 7 – 16-bit Barrel Shifter / Rotator & 4-Digit 7-Segment Display


Bryan Liu ID: 016695471

Jaden Yeremenko ID: 016414528



August 6, 2025

**Design:**

Schematic:

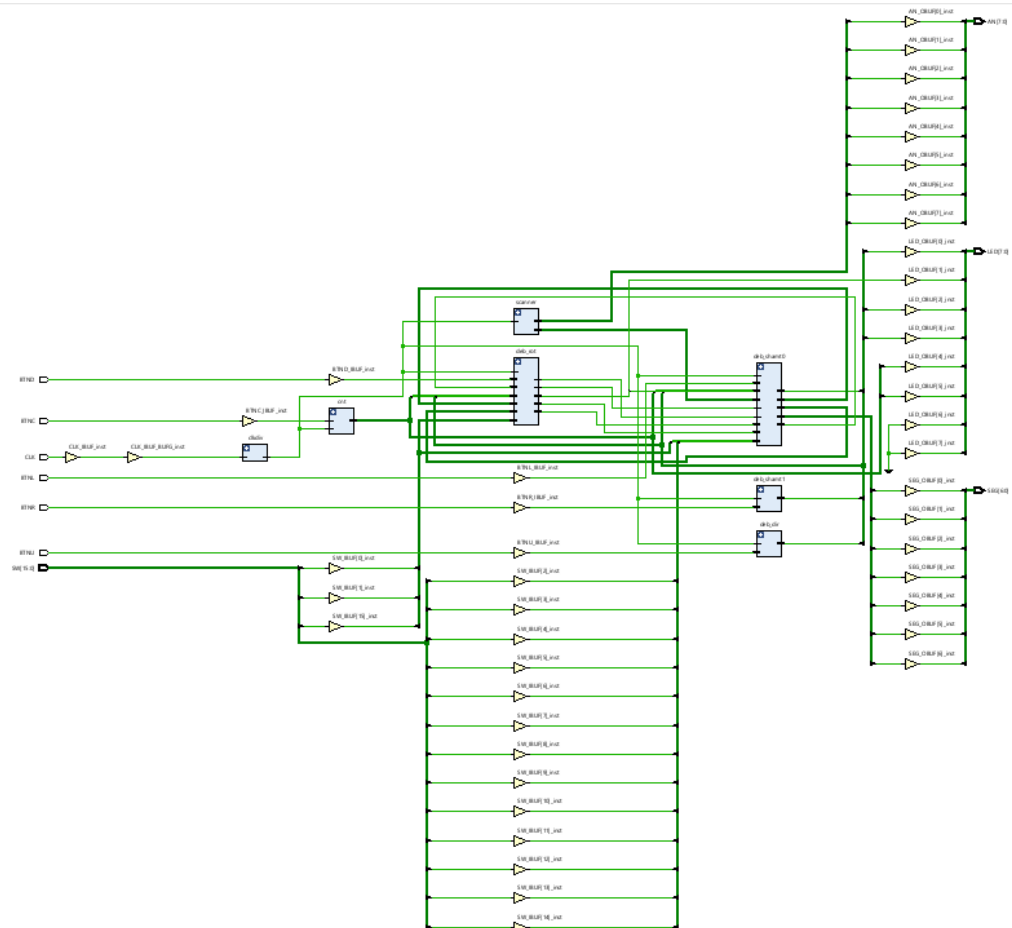


### Simulation:

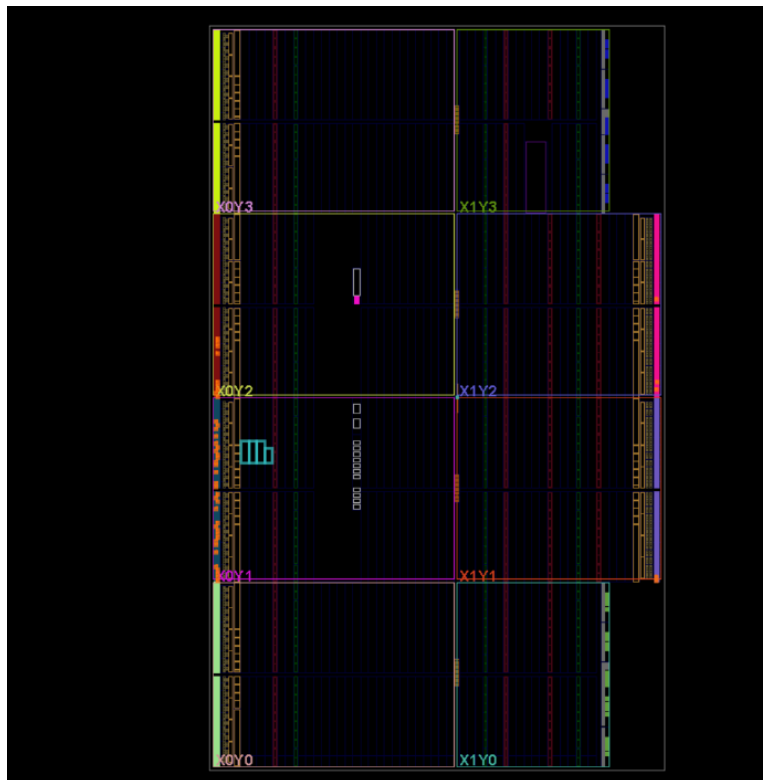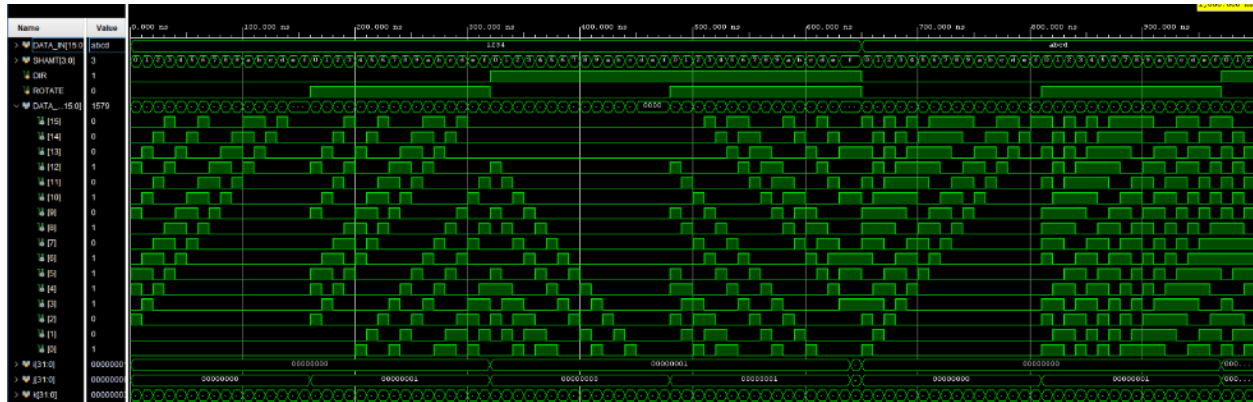

Implementation:

Power analysis from implemented netlist/verilog derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	0.13 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	25.6°C
Thermal Margin:	59.4°C (12.9 W)

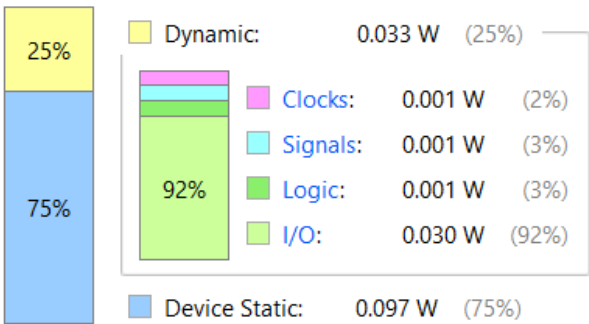

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 6.479 ns	Worst Hold Slack (WHS): 0.249 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 35	Total Number of Endpoints: 35	Total Number of Endpoints: 19

All user specified timing constraints are met.

**Contributions:**

**Bryan Liu:** Coding main, Simulation, some testing: 50%

**Jaden Yermenko:** Testbench Coding, Implementation, some testing: 50%