



Cal Poly
Pomona

College of Engineering

California Polytechnic State University, Pomona

ECE3300L

Experiment #2

GROUP K

Hoang, Dalton - 016062800

Siu, Andy - 016205137

June 23rd, 2025

Introduction: The purpose of this lab is to design and implement a 4-to-16 line decoder with an enable signal using Verilog HDL on the Digilent Nexys A7-100T FPGA development board. When the enable input is active, the decoder asserts one of the sixteen outputs corresponding to the 4-bit binary input. When the enable input is disabled, all outputs remain low.


Design (Initializing Gates):

```
22 |
23 | module decoder4x16_gate(
24 |     input [3:0] sw,      // sw[3:0] as input A
25 |     input sw4,          // sw[4] as Enable
26 |     output [15:0] led    // led[15:0] as Y
27 | );
28 |
29 |     assign led[0] = sw4 & ~sw[3] & ~sw[2] & ~sw[1] & ~sw[0];
30 |     assign led[1] = sw4 & ~sw[3] & ~sw[2] & ~sw[1] & sw[0];
31 |     assign led[2] = sw4 & ~sw[3] & ~sw[2] & sw[1] & ~sw[0];
32 |     assign led[3] = sw4 & ~sw[3] & ~sw[2] & sw[1] & sw[0];
33 |     assign led[4] = sw4 & ~sw[3] & sw[2] & ~sw[1] & ~sw[0];
34 |     assign led[5] = sw4 & ~sw[3] & sw[2] & ~sw[1] & sw[0];
35 |     assign led[6] = sw4 & ~sw[3] & sw[2] & sw[1] & ~sw[0];
36 |     assign led[7] = sw4 & ~sw[3] & sw[2] & sw[1] & sw[0];
37 |     assign led[8] = sw4 & sw[3] & ~sw[2] & ~sw[1] & ~sw[0];
38 |     assign led[9] = sw4 & sw[3] & ~sw[2] & ~sw[1] & sw[0];
39 |     assign led[10] = sw4 & sw[3] & ~sw[2] & sw[1] & ~sw[0];
40 |     assign led[11] = sw4 & sw[3] & ~sw[2] & sw[1] & sw[0];
41 |     assign led[12] = sw4 & sw[3] & sw[2] & ~sw[1] & ~sw[0];
42 |     assign led[13] = sw4 & sw[3] & sw[2] & ~sw[1] & sw[0];
43 |     assign led[14] = sw4 & sw[3] & sw[2] & sw[1] & ~sw[0];
44 |     assign led[15] = sw4 & sw[3] & sw[2] & sw[1] & sw[0];
45 |
46 | endmodule
47 |
```

Design (Encoder Behavior):

```
20 | ///////////////////////////////////////////////////////////////////
21 |
22 |
23 | module decoder4x16_behav(
24 |     input [3:0] sw,
25 |     input sw4,
26 |     output reg [15:0] led
27 | );
28 |
29 | always @(*) begin
30 |     led = 16'b0; // reset all outputs to 0
31 |     if (sw4) begin // only decode if enabled
32 |         case (sw)
33 |             4'b0000: led = 16'b0000_0000_0000_0001; //output 0
34 |             4'b0001: led = 16'b0000_0000_0000_0010; //output 1
35 |             4'b0010: led = 16'b0000_0000_0000_0100; //output 2
36 |             4'b0011: led = 16'b0000_0000_0000_1000; //output 3
37 |             4'b0100: led = 16'b0000_0000_0001_0000; //output 4
38 |             4'b0101: led = 16'b0000_0000_0010_0000; //output 5
39 |             4'b0110: led = 16'b0000_0000_0100_0000; //output 6
40 |             4'b0111: led = 16'b0000_0000_1000_0000; //output 7
41 |             4'b1000: led = 16'b0000_0001_0000_0000; //output 8
42 |             4'b1001: led = 16'b0000_0010_0000_0000; //output 9
43 |             4'b1010: led = 16'b0000_0100_0000_0000; //output 10
44 |             4'b1011: led = 16'b0000_1000_0000_0000; //output 11
45 |             4'b1100: led = 16'b0001_0000_0000_0000; //output 12
46 |             4'b1101: led = 16'b0010_0000_0000_0000; //output 13
47 |             4'b1110: led = 16'b0100_0000_0000_0000; //output 14
48 |             4'b1111: led = 16'b1000_0000_0000_0000; //output 15
49 |         endcase
50 |     end
51 | end
52 |
53 | endmodule
54 |
```

Simulation:

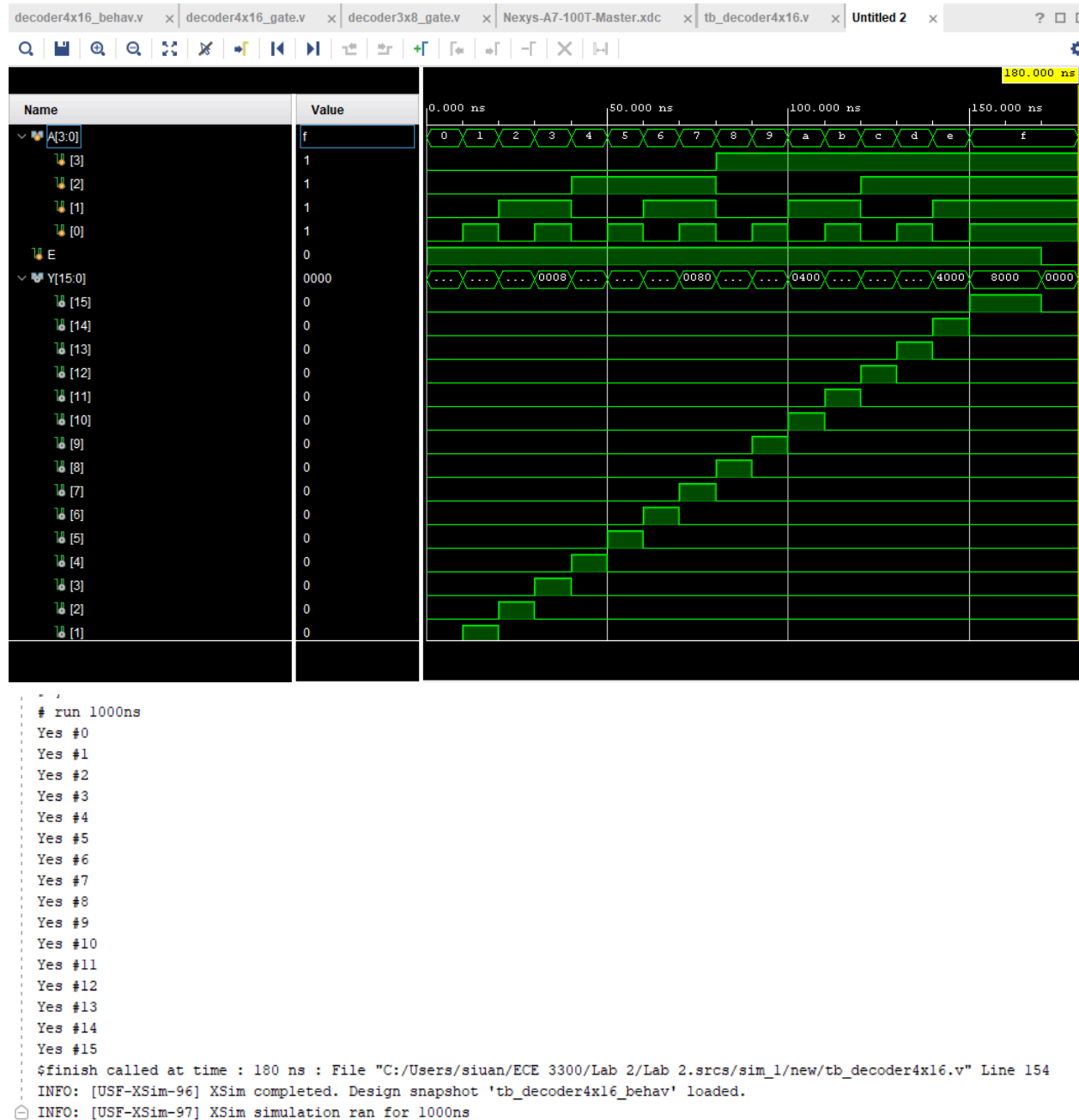

Implementation:

```
28
29 1. Slice Logic
30 -----
31
32 +-----+-----+-----+-----+-----+
33 | Site Type | Used | Fixed | Prohibited | Available | Util% |
34 +-----+-----+-----+-----+-----+
35 | Slice LUTs | 8 | 0 | 0 | 63400 | 0.01 |
36 | LUT as Logic | 8 | 0 | 0 | 63400 | 0.01 |
37 | LUT as Memory | 0 | 0 | 0 | 19000 | 0.00 |
38 | Slice Registers | 0 | 0 | 0 | 126800 | 0.00 |
39 | Register as Flip Flop | 0 | 0 | 0 | 126800 | 0.00 |
40 | Register as Latch | 0 | 0 | 0 | 126800 | 0.00 |
41 | F7 Muxes | 0 | 0 | 0 | 31700 | 0.00 |
42 | F8 Muxes | 0 | 0 | 0 | 15850 | 0.00 |
43 +-----+-----+-----+-----+-----+
44 * Warning! LUT value is adjusted to account for LUT combining.
45
46
47
118
119 5. IO and GT Specific
120 -----
121
122 +-----+-----+-----+-----+-----+
123 | Site Type | Used | Fixed | Prohibited | Available | Util% |
124 +-----+-----+-----+-----+-----+
125 | Bonded IOB | 21 | 21 | 0 | 210 | 10.00 |
126 | IOB Master Pads | 8 | 8 | 0 | 80 | 10.00 |
127 | IOB Slave Pads | 13 | 13 | 0 | 130 | 10.00 |
128 | Bonded IPADs | 0 | 0 | 0 | 2 | 0.00 |
129 | PHY_CONTROL | 0 | 0 | 0 | 6 | 0.00 |
130 | PHASER_REF | 0 | 0 | 0 | 6 | 0.00 |
131 | OUT_FIFO | 0 | 0 | 0 | 24 | 0.00 |
132 | IN_FIFO | 0 | 0 | 0 | 24 | 0.00 |
133 | IDELAYCTRL | 0 | 0 | 0 | 6 | 0.00 |
134 | IBUFDS | 0 | 0 | 0 | 202 | 0.00 |
135 | PHASER_OUT/PHASER_OUT_PHY | 0 | 0 | 0 | 24 | 0.00 |
136 | PHASER_IN/PHASER_IN_PHY | 0 | 0 | 0 | 24 | 0.00 |
137 | IDELAYE2/IDELAYE2_FINEDELAY | 0 | 0 | 0 | 300 | 0.00 |
138 | ILOGIC | 0 | 0 | 0 | 210 | 0.00 |
139 | OLOGIC | 0 | 0 | 0 | 210 | 0.00 |
140 +-----+-----+-----+-----+-----+
141
```

General Information

Timer Settings

Design Timing Summary

Methodology Summary

Check Timing (0)

Intra-Clock Paths

Inter-Clock Paths

Other Path Groups

User Ignored Paths

Unconstrained Paths

Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): inf	Worst Hold Slack (WHS): inf	Worst Pulse Width Slack (WPWS): NA
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): NA
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: NA
Total Number of Endpoints: 16	Total Number of Endpoints: 16	Total Number of Endpoints: NA

There are no user specified timing constraints.

Video Link: <https://youtube.com/shorts/Re0NGSusW10> (51 seconds)

Contributions:

Andy Siu: 50%

Dalton Hoang: 50%