
ECE 3300L California State Polytechnic University, Pomona Group G Nathaniel Garcia and Mikael Parsmyan Lab Report #8

08/12/2025


Explanation:

We have a simple 4-slot system that allows you to load four different values, one at a time, with the LOAD button. You load values into the slots in this way: PWM resolution (RES) followed by the brightness levels for the Red, Green, and Blue LEDs. You simply press the input button each time to load each value into the next slot, allowing you to change each value independently. The RES defines how many steps the PWM has to use to control the brightness; in code, it is actually RES + 1 because the PWM counts from 0 up to that number making the brightness of the LED smoother and more likely darker.

Block Diagram:

 


Pwm_core_tb:

 


Hardware Utilization:

| Name 1 | Slice LUTs (63400) | Slice Registers (126800) | Slice (15850) | LUT as Logic (63400) | Bonded IOB (210) | BUFGCTRL (32) |
|-----------------------------|-----------------------|-----------------------------|------------------|-------------------------|---------------------|------------------|
| ∨ N top_lab8 | 113 | 152 | 62 | 113 | 18 | 3 |
| u_db (debounce_onepulse) | 7 | 10 | 3 | 7 | 0 | 0 |
| u_div (clock_divider_fixed) | 37 | 32 | 19 | 37 | 0 | 0 |
| u_fsm (load_fsm) | 5 | 2 | 2 | 5 | 0 | 0 |
| u_pwm (pwm_core) | 64 | 12 | 22 | 64 | 0 | 0 |

| Resource | Utilization | Available | Utilization % |
|----------|-------------|-----------|---------------|
| LUT | 113 | 63400 | 0.18 |
| FF | 152 | 126800 | 0.12 |
| Ю | 18 | 210 | 8.57 |

 

Board Picture:

 

Contributions:

Both worked on the Lab documents

Mikael: Verilog source files, Testbench file

Nathaniel: Simulations, Xdc file and Demo