

**CALIFORNIA STATE POLYTECHNIC
UNIVERSITY, POMONA
COLLEGE OF ENGINEERING**

LAB 7

16-bit Barrel Shifter / Rotator & 4-Digit 7-Segment Display

ECE 3300L Summer 2025

Digital Circuit Design using Verilog

Professor Mohamed Aly

By: Clay Kim and Changwe Musonda

Objective

The objective of this lab was to design, simulate, and implement a 16-bit barrel shifter and rotator on a Nexys A7-100T FPGA. The system is required to perform logical shifts and rotations in both left and right directions, with the shift amount determined by a combination of on-board controls. The 16-bit input data is provided by slide switches, and the 16-bit output result is displayed as four hexadecimal digits on the board's 7-segment display. This project integrates concepts of combinational logic design, input debouncing and latching, clock management, and multi-digit display scanning.

Hardware Pin Mapping

- CLK: 100MHz On-board master clock
- SW15–SW0: SW[15:0] 16-bit input word for the barrel shifter.
- BTNC: BTN0 Asynchronous reset for the system (active low). Also advances SHAMT[3:2].
- BTNU, BTND, BTNL, BTNR: BTN[4:1] Debounced control toggles for DIR, ROT, and SHAMT[1:0].
- AN3–AN0: AN[3:0] Digit enables for the four right-most 7-segment display digits.
- SEG6–SEG0: SEG[6:0] Cathode drivers for the seven segments (A-G).
- LED7–LED0: LED[7:0] Optional debug display for DIR, ROT, and SHAMT values.

Verilog Code

top_lab7

```
module top_lab7(  
    input CLK,  
    input [15:0] SW,  
    input BTNU, BTND, BTNL, BTNR, BTNC,  
    output [7:0] LED,  
    output [7:0] AN,  
    output [6:0] SEG  
);  
  
    // Clock divider (no reset needed)  
    wire clk_2hz, clk_1khz;  
    clock_divider_fixed clkdiv(
```

```

        .CLK(CLK),

        .CLK_2HZ(clk_2hz),

        .CLK_1KHZ(clk_1khz)
    );

    // Debounced toggles for all 4 control buttons (no reset)

    wire dir_toggle, rot_toggle, shamt0_toggle, shamt1_toggle;

    debounce_toggle deb_dir(.CLK_1KHZ(clk_1khz), .BTN_RAW(BTNU),
    .BTN_TOGGLE(dir_toggle));

    debounce_toggle deb_rot(.CLK_1KHZ(clk_1khz), .BTN_RAW(BTND),
    .BTN_TOGGLE(rot_toggle));

    debounce_toggle deb_shamt0(.CLK_1KHZ(clk_1khz), .BTN_RAW(BTNL),
    .BTN_TOGGLE(shamt0_toggle));

    debounce_toggle deb_shamt1(.CLK_1KHZ(clk_1khz), .BTN_RAW(BTNR),
    .BTN_TOGGLE(shamt1_toggle));

    // SHAMT[3:2] via BTNC press (no reset)

    wire [1:0] shamt_high;

    shamt_counter cnt(
        .CLK(clk_1khz),
        .BTNC(BTNC),
        .SHAMT_HIGH(shamt_high)
    );

    // Build SHAMT[3:0]

    wire [3:0] shamt = {shamt_high, shamt1_toggle, shamt0_toggle};

    // Barrel shifter

    wire [15:0] barrel_out;

    barrel_shifter16 shifter(

```

```

        .DATA_IN(SW),
        .SHAMT(shamt),
        .DIR(dir_toggle),
        .ROTATE(rot_toggle),
        .DATA_OUT(barrel_out)
    );

// HEX to 7-seg (only rightmost 4 digits show output, others blank)
wire [6:0] seg0, seg1, seg2, seg3;
hex_to_7seg h0(.HEX(barrel_out[3:0]), .SEG(seg0));
hex_to_7seg h1(.HEX(barrel_out[7:4]), .SEG(seg1));
hex_to_7seg h2(.HEX(barrel_out[11:8]), .SEG(seg2));
hex_to_7seg h3(.HEX(barrel_out[15:12]), .SEG(seg3));
wire [6:0] blank = 7'b1111111;

// 8-digit display scanner
seg7_scan8 scanner(
    .CLK_1KHZ(clk_1khz),
    .SEG0(seg0), .SEG1(seg1), .SEG2(seg2), .SEG3(seg3),
    .SEG4(blank), .SEG5(blank), .SEG6(blank), .SEG7(blank),
    .AN(AN), .SEG(SEG)
);

// Debug LEDs (show DIR, ROT, SHAMT)
assign LED[7:0] = {2'b00, shamt, rot_toggle, dir_toggle};

endmodule

```

barrel_shifter16

```
module barrel_shifter16(
    input [15:0] DATA_IN,
    input [3:0] SHAMT,
    input DIR,      // 0 = left, 1 = right
    input ROTATE,   // 0 = logical, 1 = rotate
    output [15:0] DATA_OUT
);
    wire [15:0] stage1, stage2, stage3, stage4;

    assign stage1 = SHAMT[0] ?
        (DIR ?
            (ROTATE ? {DATA_IN[0], DATA_IN[15:1]} : {1'b0, DATA_IN[15:1]}) :
            (ROTATE ? {DATA_IN[14:0], DATA_IN[15]} : {DATA_IN[14:0], 1'b0})
        )
        : DATA_IN;

    assign stage2 = SHAMT[1] ?
        (DIR ?
            (ROTATE ? {stage1[1:0], stage1[15:2]} : {2'b00, stage1[15:2]}) :
            (ROTATE ? {stage1[13:0], stage1[15:14]} : {stage1[13:0], 2'b00})
        )
        : stage1;

    assign stage3 = SHAMT[2] ?
        (DIR ?
            (ROTATE ? {stage2[3:0], stage2[15:4]} : {4'b0000, stage2[15:4]}) :
            (ROTATE ? {stage2[11:0], stage2[15:12]} : {stage2[11:0], 4'b0000})
        )
```

```

: stage2;

assign stage4 = SHAMT[3] ?
    (DIR ?
        (ROTATE ? {stage3[7:0], stage3[15:8]} : {8'b00000000, stage3[15:8]}) :
        (ROTATE ? {stage3[7:0], stage3[15:8]} : {stage3[7:0], 8'b00000000})
    )
: stage3;

assign DATA_OUT = stage4;
endmodule

```

clock_divider_fixed

```

module clock_divider_fixed(
    input CLK,
    output reg CLK_2HZ,
    output reg CLK_1KHZ
);
    parameter DIV_2HZ = 26'd25_000_000; // for 2Hz (toggle)
    parameter DIV_1KHZ = 17'd50_000; // for 1kHz

    reg [25:0] cnt_2hz = 0;
    reg [16:0] cnt_1khz = 0;

    always @(posedge CLK) begin
        if (cnt_2hz == DIV_2HZ-1) begin
            cnt_2hz <= 0;

```

```

        CLK_2HZ <= ~CLK_2HZ;
    end else begin
        cnt_2hz <= cnt_2hz + 1;
    end
end

always @(posedge CLK) begin
    if (cnt_1khz == DIV_1KHZ-1) begin
        cnt_1khz <= 0;
        CLK_1KHZ <= ~CLK_1KHZ;
    end else begin
        cnt_1khz <= cnt_1khz + 1;
    end
end
endmodule

```

debounce_toggle

```

module debounce_toggle(
    input CLK_1KHZ,
    input BTN_RAW,
    output reg BTN_TOGGLE
);
    reg [2:0] shift_reg = 0;
    reg last_state = 0;

    always @(posedge CLK_1KHZ) begin
        shift_reg <= {shift_reg[1:0], BTN_RAW};
    end
endmodule

```

```

    if (shift_reg == 3'b111 && !last_state) begin
        BTN_TOGGLE <= ~BTN_TOGGLE;
        last_state <= 1;
    end else if (shift_reg == 3'b000) begin
        last_state <= 0;
    end
end
end
endmodule

```

hex_to_7seg

```

module hex_to_7seg(
    input [3:0] HEX,
    output reg [6:0] SEG
);
    always @(*) begin
        case(HEX)
            4'h0: SEG = 7'b1000000;
            4'h1: SEG = 7'b1111001;
            4'h2: SEG = 7'b0100100;
            4'h3: SEG = 7'b0110000;
            4'h4: SEG = 7'b0011001;
            4'h5: SEG = 7'b0010010;
            4'h6: SEG = 7'b0000010;
            4'h7: SEG = 7'b1111000;
            4'h8: SEG = 7'b0000000;
            4'h9: SEG = 7'b0010000;
            4'hA: SEG = 7'b0001000;

```



```

    4'hB: SEG = 7'b0000011;
    4'hC: SEG = 7'b1000110;
    4'hD: SEG = 7'b0100001;
    4'hE: SEG = 7'b0000110;
    4'hF: SEG = 7'b0001110;

endcase

end

endmodule


seg7_scan8
module seg7_scan8(
    input CLK_1KHZ,
    input [6:0] SEG0, SEG1, SEG2, SEG3, SEG4, SEG5, SEG6, SEG7,
    output reg [7:0] AN,
    output reg [6:0] SEG
);

    reg [2:0] scan_cnt = 0;

    always @(posedge CLK_1KHZ) begin
        scan_cnt <= scan_cnt + 1;
    end

    always @(*) begin
        case(scan_cnt)
            3'd0: begin AN = 8'b11111110; SEG = SEG0; end // rightmost digit
            3'd1: begin AN = 8'b11111101; SEG = SEG1; end
            3'd2: begin AN = 8'b11111011; SEG = SEG2; end
            3'd3: begin AN = 8'b11110111; SEG = SEG3; end
            3'd4: begin AN = 8'b11101111; SEG = SEG4; end // blank

```

```
    3'd5: begin AN = 8'b11011111; SEG = SEG5; end // blank
    3'd6: begin AN = 8'b10111111; SEG = SEG6; end // blank
    3'd7: begin AN = 8'b01111111; SEG = SEG7; end // blank
endcase
end
endmodule
```

shamt_counter

```
module shamt_counter(
    input CLK,
    input BTNC,
    output reg [1:0] SHAMT_HIGH
);
    reg btnc_last = 0;
    always @(posedge CLK) begin
        btnc_last <= BTNC;
        if (BTNC & ~btnc_last)
            SHAMT_HIGH <= SHAMT_HIGH + 1;
    end
endmodule
```

Testbench Code

barrel_shifter16_tb

```
module barrel_shifter16_tb();

    reg [15:0] DATA_IN;
    reg [3:0] SHAMT;
    reg DIR;
    reg ROTATE;
    wire [15:0] DATA_OUT;

    integer i, j, k;

    barrel_shifter16 dut (
        .DATA_IN(DATA_IN),
        .SHAMT(SHAMT),
        .DIR(DIR),
        .ROTATE(ROTATE),
        .DATA_OUT(DATA_OUT)
    );

    initial begin

        DATA_IN <= 16'h1234;

        for (i = 0; i <= 1; i = i + 1) begin
            DIR <= i;
            for (j = 0; j <= 1; j = j + 1) begin
                ROTATE <= j;
                for (k = 0; k < 16; k = k + 1) begin
```

```

        SHAMT <= k;

        #10;

    end

end

end

#10;

DATA_IN <= 16'hABCD;


for (i = 0; i <= 1; i = i + 1) begin
    DIR <= i;

    for (j = 0; j <= 1; j = j + 1) begin
        ROTATE <= j;

        for (k = 0; k < 16; k = k + 1) begin
            SHAMT <= k;

            #10;

        end

    end

end

end

#20;

$finish;

end

endmodule

```

debounce_toggle_tb

```

module debounce_toggle_tb();

```

```

    reg CLK_1KHZ = 0;

```

```
reg BTN_RAW = 0;
```

```
wire btn_toggle;
```

```
always #5_000 CLK_1KHZ = ~CLK_1KHZ;
```

```
debounce_toggle dut (  
    .CLK_1KHZ (CLK_1KHZ),  
    .BTN_RAW (BTN_RAW),  
    .BTN_TOGGLE(btn_toggle)  
);
```

```
initial begin
```

```
    #20_000;
```

```
    BTN_RAW = 1; #500;
```

```
    BTN_RAW = 0; #400;
```

```
    BTN_RAW = 1; #800;
```

```
    BTN_RAW = 0; #600;
```

```
    BTN_RAW = 1;
```

```
    #100_000;
```

```
    BTN_RAW = 0; #500;
```

```
    BTN_RAW = 1; #400;
```

```
    BTN_RAW = 0; #800;
```

```
    BTN_RAW = 1; #600;
```

```
    BTN_RAW = 0;
```

```
    #100_000;
```

```
    BTN_RAW = 1; #200_000;
```

```
BTN_RAW = 0; #200_000;
```

```
BTN_RAW = 1; #200;
```

```
BTN_RAW = 0; #100_000;
```

```
BTN_RAW = 1; #200_000;
```

```
BTN_RAW = 0; #200_000;
```

```
#50_000;
```

```
$finish;
```

```
end
```

```
endmodule
```

seg7_scan8_tb

```
module seg7_scan8_tb();
```

```
    reg clk_1kHz = 0;
```

```
    reg [6:0] SEG0, SEG1, SEG2, SEG3, SEG4, SEG5, SEG6, SEG7;
```

```
    wire [7:0] AN;
```

```
    wire [6:0] SEG;
```

```
    seg7_scan8 dut (
```

```
        .CLK_1KHZ(clk_1kHz),
```

```
        .SEG0(SEG0), .SEG1(SEG1), .SEG2(SEG2), .SEG3(SEG3),
```

```
        .SEG4(SEG4), .SEG5(SEG5), .SEG6(SEG6), .SEG7(SEG7),
```

```
        .AN(AN),
```

```
        .SEG(SEG)
```

```
    );
```

```
always #500_000 clk_1kHz = ~clk_1kHz;
```

```
initial begin
```

```
    SEG0 = 7'b1000000; // 0
```

```
    SEG1 = 7'b1111001; // 1
```

```
    SEG2 = 7'b0100100; // 2
```

```
    SEG3 = 7'b0110000; // 3
```

```
    SEG4 = 7'b0011001; // 4
```

```
    SEG5 = 7'b0010010; // 5
```

```
    SEG6 = 7'b0000010; // 6
```

```
    SEG7 = 7'b1111000; // 7
```

```
    #20000; // 20 ms
```

```
    $finish;
```


```
end
```

```
endmodule
```


Synthesis and Implementation

Screenshots


barrel_shifter16_tb

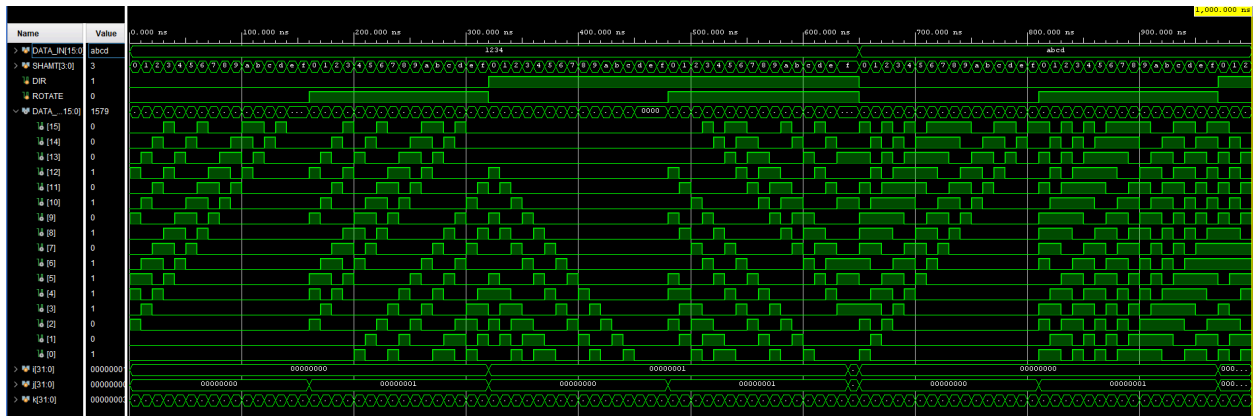


debounce_toggle_tb

 

seg7_scan8_tb

 

Vivado Utilization

 

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	0.13 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	25.6°C
Thermal Margin:	59.4°C (12.9 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	4.6°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

25%

75%

Clocks: 0.001 W (2%)

Signals: 0.001 W (3%)

Logic: 0.001 W (3%)

I/O: 0.030 W (92%)

Dynamic: 0.033 W (25%)

Device Static: 0.097 W (75%)

DRC	Methodology	Power	Timing	Utilization			
Q	≡	≡	%	Hierarchy			
Name	^1	Slice LUTs (63400)	Slice Registers (126800)	Slice (15850)	LUT as Logic (63400)	Bonded IOB (210)	BUFGCTRL (32)
▼ N top_lab7		103	44	39	103	45	1
clkdiv (clock_divider_fixed)		5	18	7	5	0	0
cnt (shamt_counter)		1	3	1	1	0	0
deb_dir (debounce_toggle)		1	5	2	1	0	0
deb_rot (debounce_toggle_0)		5	5	4	5	0	0
deb_shamt0 (debounce_toggle_1)		84	5	28	84	0	0
deb_shamt1 (debounce_toggle_2)		1	5	2	1	0	0
scanner (seg7_scan8)		6	3	4	6	0	0

Partner Contribution

Clay Kim: Testbench and Simulation

Changwe Musonda: Demonstration video and implementation

Reflections

This lab successfully culminated in the implementation of a 16-bit barrel shifter and rotator on a Nexys A7 FPGA. The core of the design was a purely combinational module that performed logical shifts and rotations on the 16-bit input from SW[15:0]. By structuring the logic into four logarithmic stages of 2-to-1 multiplexers, the system could permute the input word in a single clock cycle. This design effectively demonstrated how complex permutation operations can be built from simple, repeated hardware blocks, with DIR and ROTATE signals dynamically controlling the data path.

A robust user interface was created using debounced push-buttons with edge-to-toggle logic to generate stable control signals. A key feature was the use of BTNC to drive a 2-bit counter, allowing all 16 shift positions (SHAMT[3:0]) to be tested without consuming extra switches. The final 16-bit result was displayed in hexadecimal on four 7-segment digits, managed by a scanner and a dual-rate clock divider that provided both a slow ~2 Hz clock for visual demonstration and a fast ~1 kHz clock for a flicker-free display. Overall, the project was a comprehensive exercise in integrating core logic with practical I/O handling and system timing.