

ECE 3300L

Lab Report #5

Group A

Edwin Estrada (#015897050)

Michelle Lau (#016027427)

July 20, 2025

Design

Clock Divider

```
3 | module clock_divider (  
4 |     input clk,  
5 |     input rst_n,  
6 |     output reg [31:0] cnt  
7 | );  
8 |     always @(posedge clk or negedge rst_n)  
9 |         if (!rst_n)  
10 |             cnt <= 32'd0;  
11 |         else  
12 |             cnt <= cnt + 1;  
13 | endmodule
```

Our program has two clocks. This clock handles increment/decrements once per cycle. To create a clock with 32 levels of speed, a 32 bit register to hold the count is created. If that's the input for a 32x1 mux, selected by 5 switches, the speed of the clock can be manipulated depending on the bit selected. If the LSB of cnt is selected, the increment/decrement operation is done 100 million times per second (since the board has 100Mhz base clock). If the MSB of cnt is selected, the increment/decrement operation is done once every ~43 seconds.

32x1 Mux

```
3 | module mux32x1 (  
4 |     input [31:0] cnt,  
5 |     input [4:0] sel,  
6 |     output clk_out  
7 | );  
8 |     assign clk_out = cnt[sel];  
9 | endmodule
```

As explained in the module above, the 32x1 mux is used to control the speed of the clock dedicated to incrementing/decrementing the counter.

BCD Up/Down Counter

```

3  module bcd_up_down_counter(
4      input clk,
5      input rst_n,
6      input dir,
7      output reg [3:0] digit0,
8      output reg [3:0] digit1
9  );
10
11      reg [3:0] next_digit0, next_digit1;
12      reg carry;
13
14      always @(posedge clk or negedge rst_n) begin
15          if (!rst_n) begin
16              digit0 <= 0;
17              digit1 <= 0;
18          end else begin
19              digit0 <= next_digit0;
20              digit1 <= next_digit1;
21          end
22      end
23
24      always @(*) begin
25          next_digit0 = digit0;
26          next_digit1 = digit1;
27          carry = 0;
28
29          if (dir) begin
30              if (digit0 == 9) begin
31                  next_digit0 = 0;
32                  if (digit1 == 9)
33                      next_digit1 = 0;
34                  else
35                      next_digit1 = digit1 + 1;
36              end else begin
37                  next_digit0 = digit0 + 1;
38              end
39          end else begin
40              if (digit0 == 0) begin
41                  next_digit0 = 9;
42                  if (digit1 == 0)
43                      next_digit1 = 9;
44                  else
45                      next_digit1 = digit1 - 1;
46              end else begin
47                  next_digit0 = digit0 - 1;
48              end
49          end
50      end
51  endmodule

```

This module handles the next number to display when the clock mentioned above is positive edge triggered. If the counter is incrementing, check if the ones digit is a 9. If it is, set the ones digit to 0 and check if the tens digit is 9. If it's not, increment the tens digit. Otherwise, set the tens digit to 0. If the counter is decrementing, check if the ones digit is 0. If the ones digit is 0, set the ones digit to 9 and check if the tens digit is 0. If it is, set the tens digit to 9. Otherwise, decrement the tens digit.

7 Segment Display Driver

```

3  module seg7_scan(
4      input clk,
5      input rst_n,
6      input [3:0] digit0, digit1,
7      output reg [6:0] seg,
8      output reg [7:0] an
9  );
10     reg [19:0] refresh_counter;
11     wire sel = refresh_counter[19];
12
13     always @(posedge clk or negedge rst_n) begin
14         if(!rst_n)
15             refresh_counter <= 0;
16         else
17             refresh_counter <= refresh_counter + 1;
18     end
19
20     wire [3:0] digit = sel ? digit1 : digit0;
21
22     always @(digit) begin
23         case (digit)
24             4'd0: seg = 7'b0000001;
25             4'd1: seg = 7'b1001111;
26             4'd2: seg = 7'b0010010;
27             4'd3: seg = 7'b0000110;
28             4'd4: seg = 7'b1001100;
29             4'd5: seg = 7'b0100100;
30             4'd6: seg = 7'b0100000;
31             4'd7: seg = 7'b0001111;
32             4'd8: seg = 7'b0000000;
33
34             4'd9: seg = 7'b0001100;
35             default: seg = 7'b1111111;
36         endcase
37     end
38
39     always @(sel) begin
40         case (sel)
41             1'b0: an = 8'b11111110;
42             1'b1: an = 8'b11111101;
43         endcase
44     end
45 endmodule

```

The seven seg driver includes the second clock. This clock handles which digit on the seven seg display to turn on, alternating between two digits. If the driver alternates between the two digits fast enough, an optical illusion occurs where it looks like the display is displaying two different numbers at the same time. In addition to selecting the digit on the display to turn on, the sel register also decides the number to display on its respective digit.

High Level Implementation

```
3  module top_lab5 (
4      input      CLK,
5      input      rst_n,
6      input      BTN,
7      input  [4:0] SW,
8      output [6:0] SEG,
9      output [7:0] AN,
10     output [9:0] LED
11 );
12
13     wire [31:0] cnt;
14     clock_divider u_div (
15         .clk (CLK),
16         .rst_n (!rst_n),
17         .cnt (cnt)
18     );
19
20     wire clk_out;
21     mux32x1 u_mux (
22         .cnt (cnt),
23         .sel (SW),
24         .clk_out (clk_out)
25     );
26
27     wire [3:0] digit0;
28     wire [3:0] digit1;
29     bcd_up_down_counter u_bcd (
30         .clk (clk_out),
31         .rst_n (!rst_n),
32         .dir (BTN),
33
34         .digit0 (digit0),
35         .digit1 (digit1)
36     );
37     seg7_scan u_scan (
38         .clk (CLK),
39         .rst_n (!rst_n),
40         .digit0 (digit0),
41         .digit1 (digit1),
42         .seg (SEG),
43         .an (AN)
44     );
45
46     assign LED[4:0] = SW;
47     assign LED[8:5] = {digit1, digit0};
48     assign LED[9]   = clk_out;
49
50 endmodule
```


Putting everything together. The base clock on the board goes into the clock divider module, which goes into the 32x1 mux to select the speed of the clock outputted from the divider. This new clock is then input to the BCD increment/decrement counter, and the digit output from that counter as well as the second clock in our project are sent to the 7 seg display driver to return the signals required to send to our anodes/cathodes of the display to output the counter increment/decrementing depending on what mode we choose.

Simulation Waveform

Clock Divider



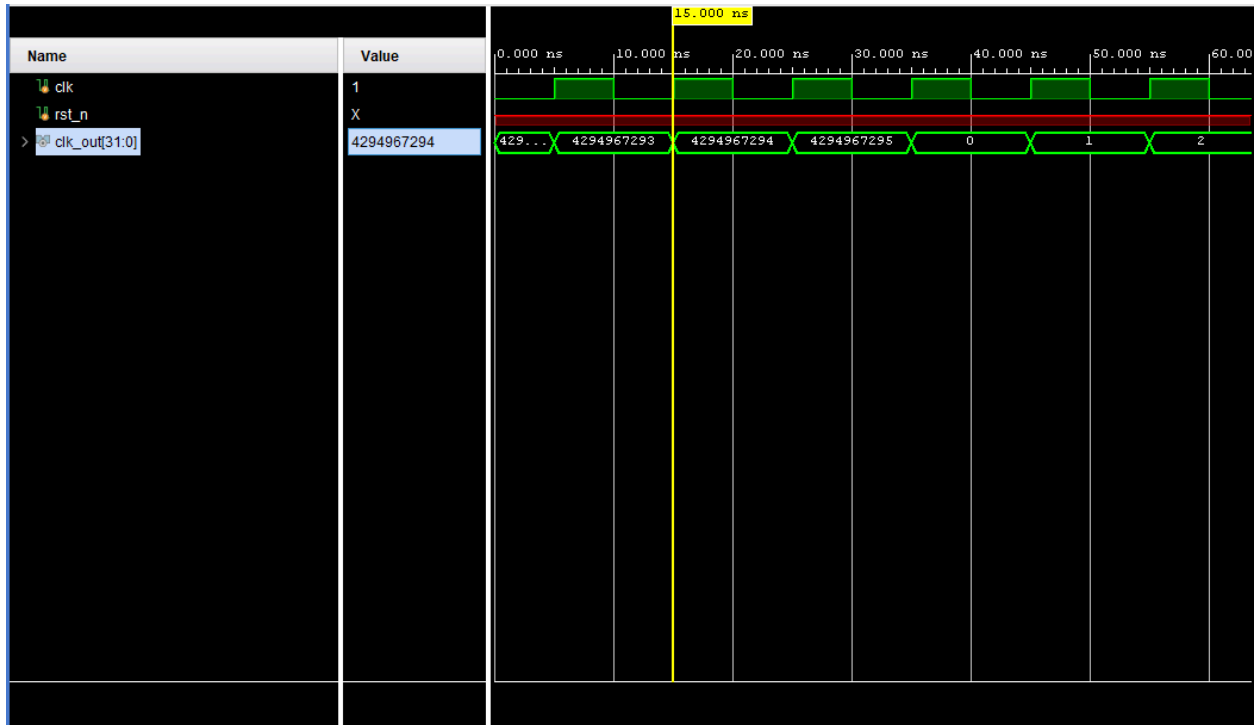Upon starting the program, the counter starts at 0



Once the counter reaches the value of $(2^{32}) - 1$, or 4,294,967,295, the counter is automatically reset to 0 to count all over again.

32x1 Mux



The following process I'll explain was done for every input, but to reduce redundancy, I will only explain selecting the LSB of cnt. To begin, I put the LSB of cnt on high and setting sel to 00001, selecting the LSB. This results in the clk_out being high. Then I put the LSB of cnt low. With the LSB of cnt selected, this results in clk_out being low.

bcd up down counter



NOTE: digit1 = tens place, digit0 = ones place
When dir = 0, the counter is decrementing.




When $dir = 1$, the counter is incrementing.


seg7_scan



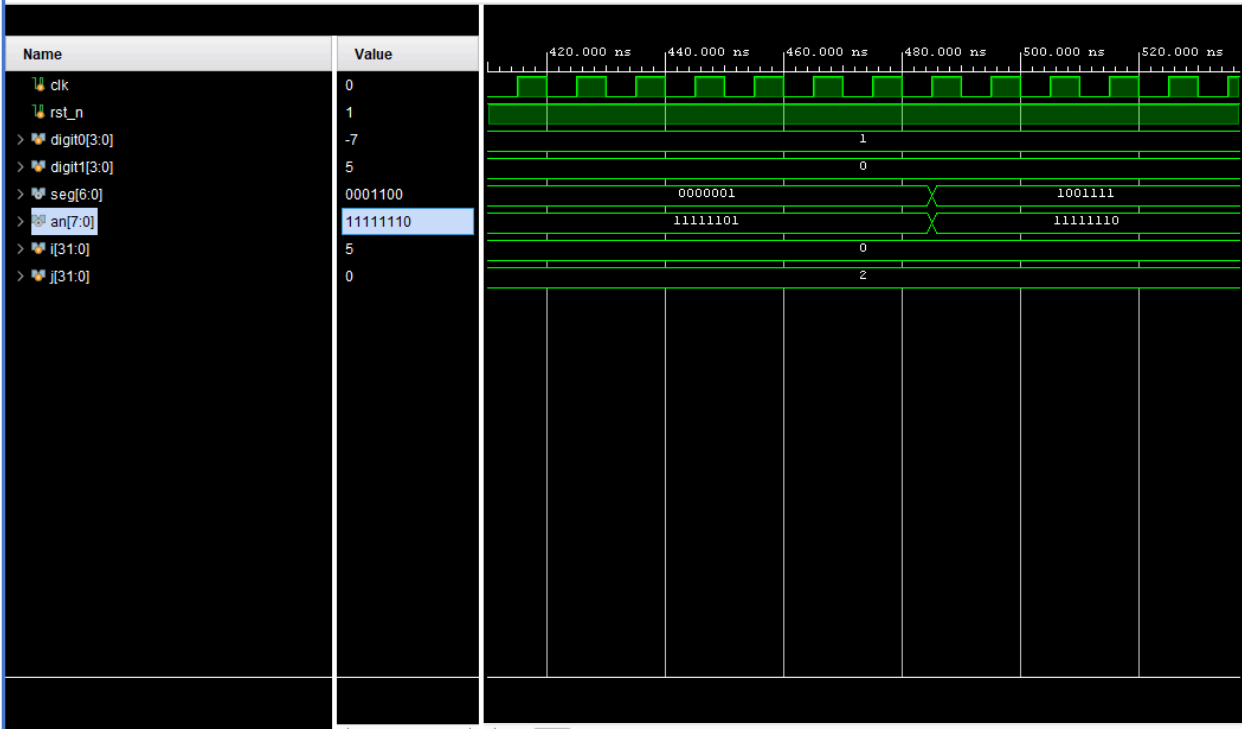When the rightmost digit is selected by AN and digit0 = 0, seg returns 000001 (the number 0).
When the leftmost digit is selected by AN and digit1 = 0, seg returns 000001 (the number 0).
“00” is displayed.



“01” is displayed.

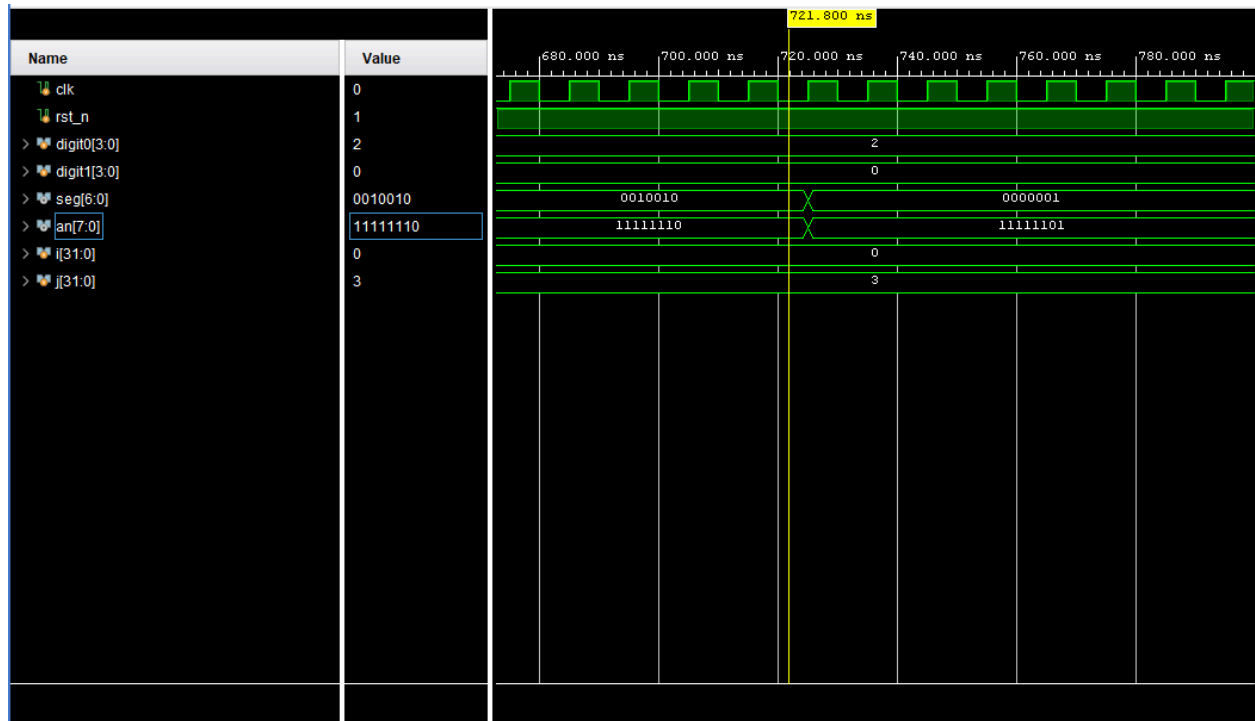


“02” is displayed.

Top Level


To simulate, I will show the counter decrementing 5 times and incrementing 5 times

Decrementing


Dir signal is low.

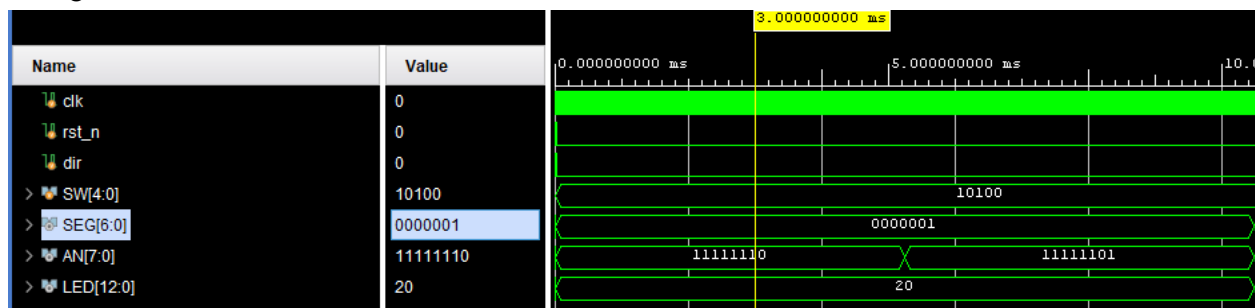


The counter begins at “00”

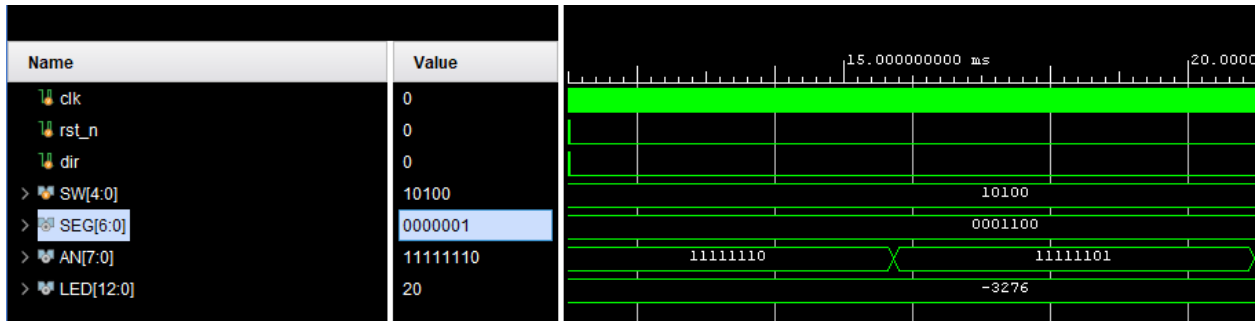


Counter decrements, wrapping to “99”

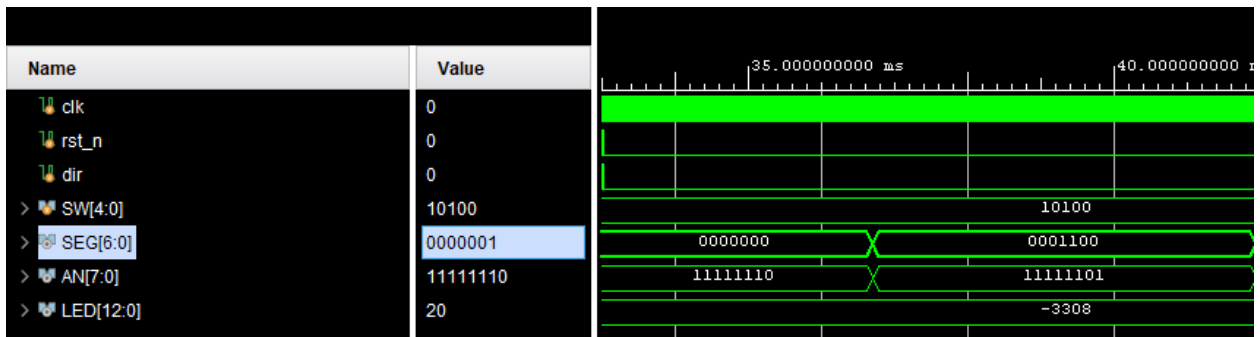

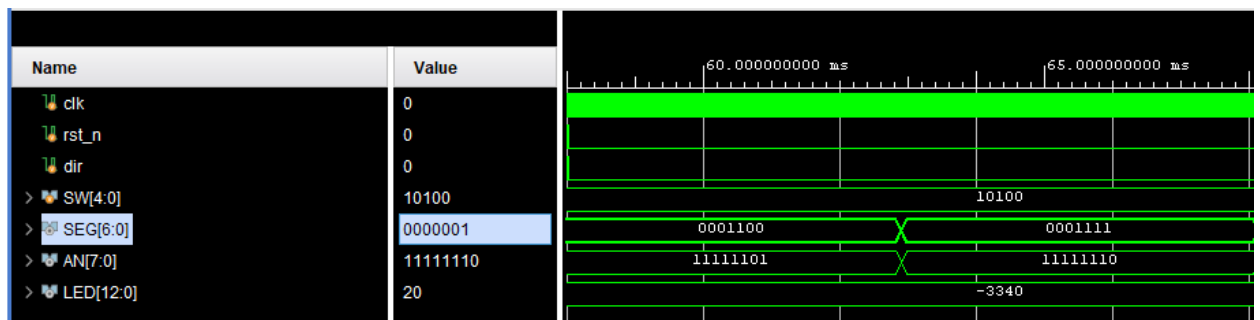
Counter decrements. Right digit displays “8”, left digit displays “9”, resulting in 97.



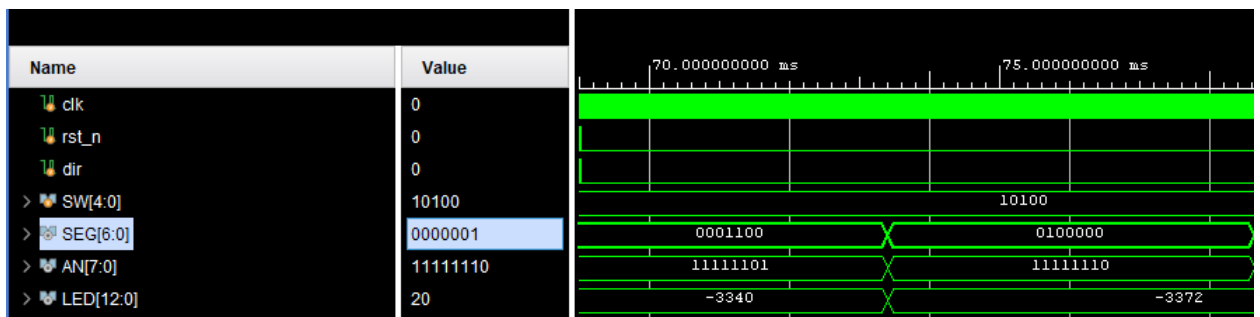Counter decrements. Left digit displays “9”, right digit displays “7”, resulting in “97”.



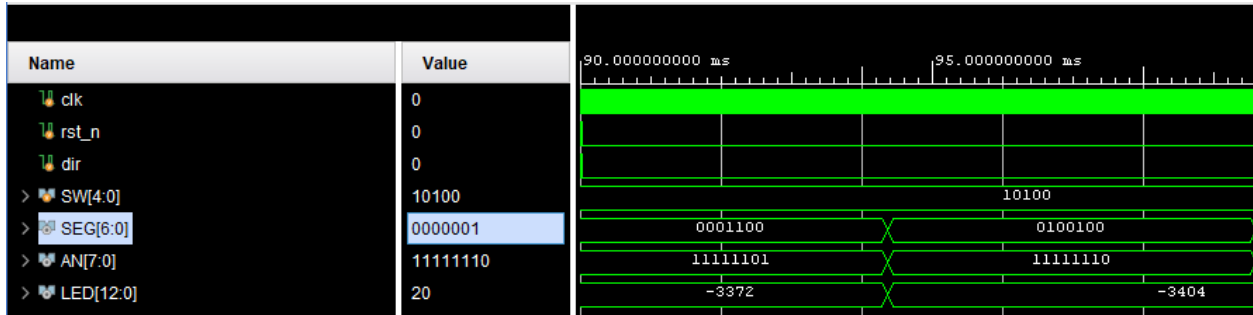
Counter decrements. Left digit displays “9”, right digit displays “6”, resulting in “96”.




Counter decrements. Left digit displays “9”, right digit displays “5”, resulting in “95”.

Incrementing


Dir signal is high.

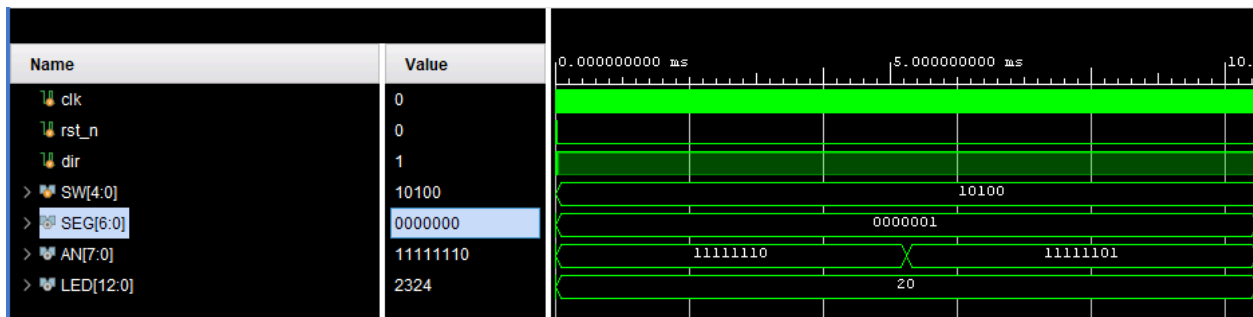

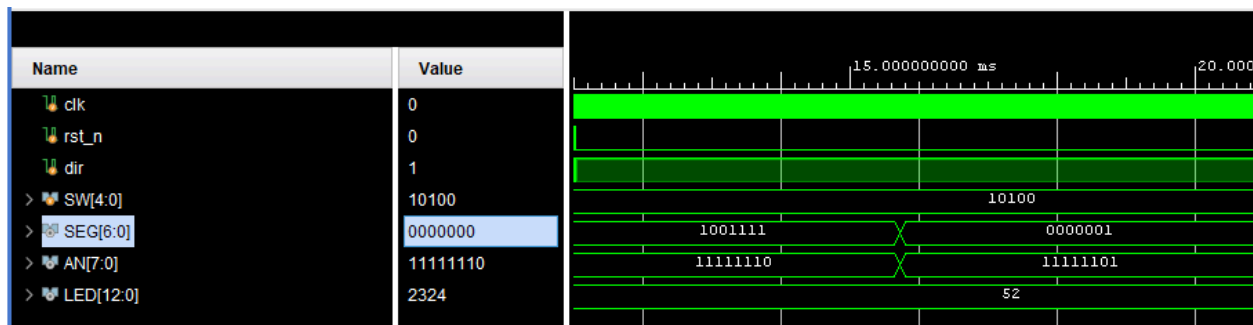
With the left and right digit being “0”, the counter starts at “00”.



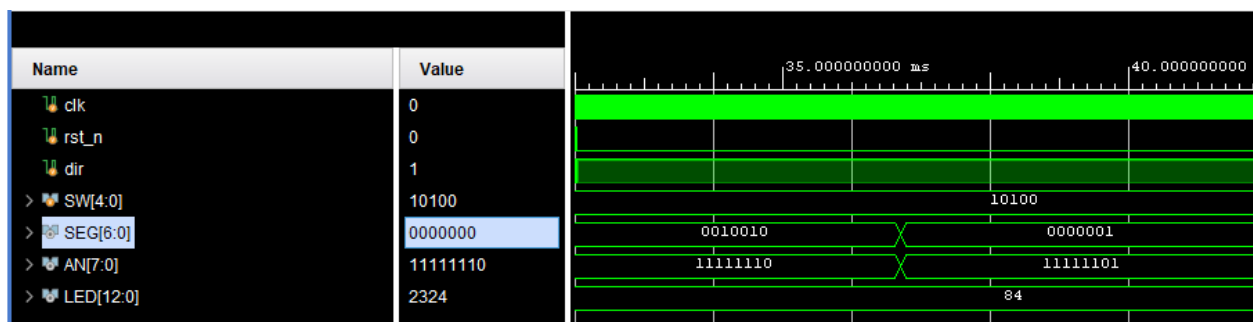
Counter increments. Right digit displays “1” and left digit displays “0”, resulting in “01”.



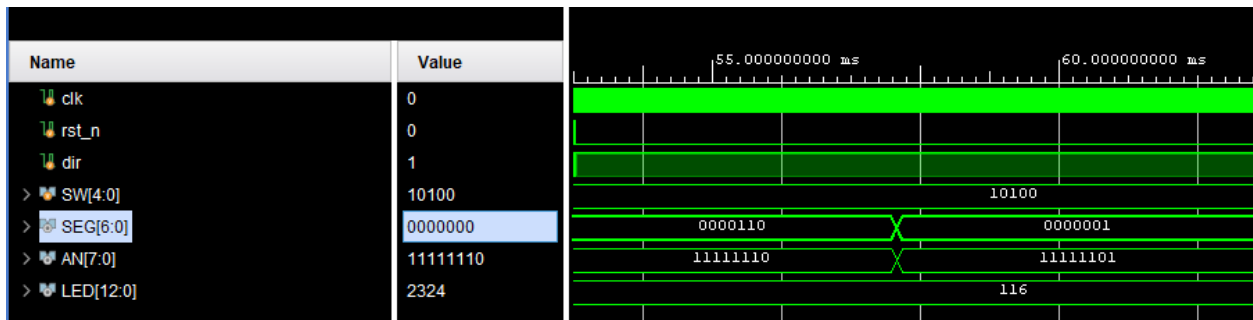
Counter increments. Right digit displays “2” and left digit displays “0”, resulting in “02”.



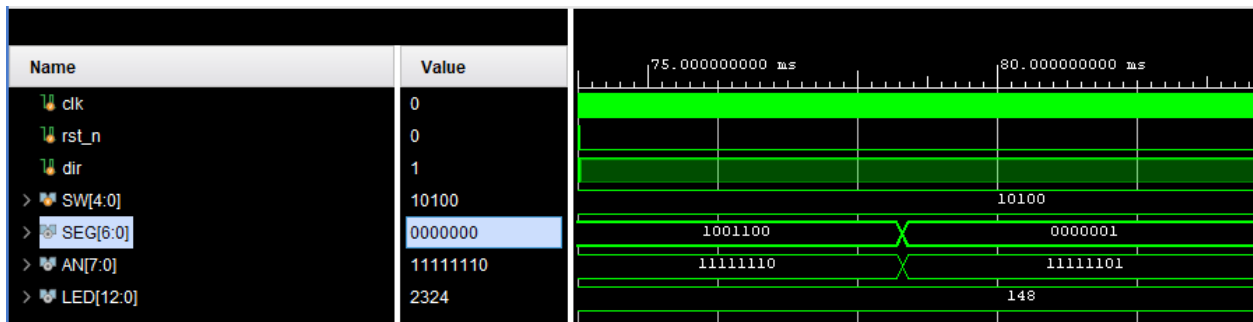Counter increments. Right digit displays “3” and left digit displays “0”, resulting in “03”.



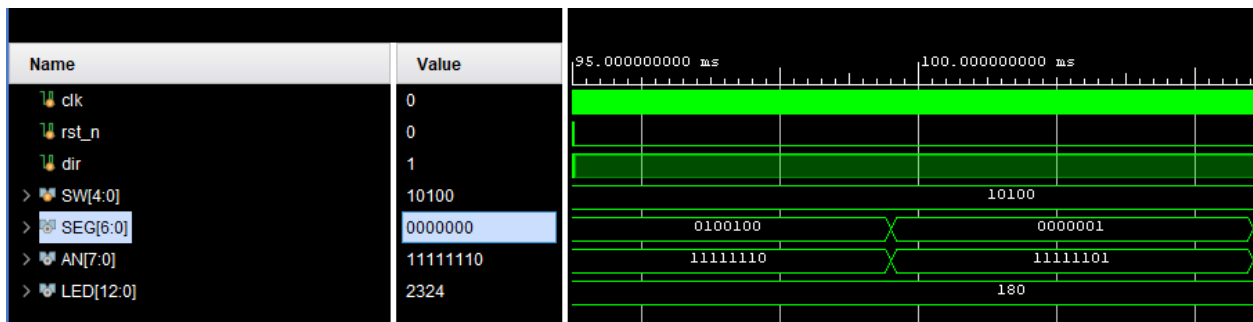Counter increments. Right digit displays “4” and left digit displays “0”, resulting in “04”.




Counter increments. Right digit displays “5” and left digit displays “0”, resulting in “05”.

Implementation

Utilization Table:

Summary

| Resource | Utilization | Available | Utilization % |
|----------|-------------|-----------|---------------|
| LUT | 26 | 63400 | 0.04 |
| FF | 60 | 126800 | 0.05 |
| IO | 33 | 210 | 15.71 |

 

Timing Summary:

Design Timing Summary

| Setup | Hold | Pulse Width |
|--------------------------------------|----------------------------------|---|
| Worst Negative Slack (WNS): 6.851 ns | Worst Hold Slack (WHS): 0.213 ns | Worst Pulse Width Slack (WPWS): 4.500 ns |
| Total Negative Slack (TNS): 0.000 ns | Total Hold Slack (THS): 0.000 ns | Total Pulse Width Negative Slack (TPWS): 0.000 ns |
| Number of Failing Endpoints: 0 | Number of Failing Endpoints: 0 | Number of Failing Endpoints: 0 |
| Total Number of Endpoints: 52 | Total Number of Endpoints: 52 | Total Number of Endpoints: 53 |

All user specified timing constraints are met.

Contribution

Michelle Lau (50%) - Implementation and board demo

Edwin Estrada (50%) - Programming, and test benching