

ECE 3300L

Lab Report #8

Group A

Edwin Estrada (#015897050)

Michelle Lau (#016027427)

August 14, 2025

## Design

### Fixed Clock Divider

```
1  module clock_divider_fixed #(
2      parameter integer INPUT_HZ = 100_000_000,
3      parameter integer TICK1_HZ = 1_000,
4      parameter integer PWM_HZ = 20_000
5  ) (
6      input wire clk_in,
7      input wire rst_n,
8      output reg clk_1k,
9      output reg clk_pwm
10 );
11     localparam integer DIV1H = (INPUT_HZ/TICK1_HZ)/2;
12     localparam integer DIVPMH = (INPUT_HZ/PWM_HZ)/2;
13     reg [$clog2(DIV1H):0] c1;
14     reg [$clog2(DIVPMH):0] c2;
15
16     always @(posedge clk_in or negedge rst_n) begin
17         if (!rst_n) begin c1 <= 0; clk_1k <= 0; c2 <= 0; clk_pwm <= 0; end
18         else begin
19             if (c1 == DIV1H-1) begin c1 <= 0; clk_1k <= ~clk_1k; end else c1 <= c1+1;
20             if (c2 == DIVPMH-1) begin c2 <= 0; clk_pwm <= ~clk_pwm; end else c2 <= c2+1;
21         end
22     end
23 endmodule
```

This module creates two clocks from the 100Mhz base FPGA clock: The 1kHz clock for the debounce button module and for handling the FSM.

## Debounce Pulse

```
1  module debounce_onepulse #(
2      parameter integer STABLE_TICKS = 20
3  ) (
4      input wire clk,
5      input wire rst_n,
6      input wire din,
7      output reg pulse
8  );
9
10 reg d0, d1;
11 reg stable, stable_q;
12 reg [$clog2(STABLE_TICKS+1)-1:0] cnt;
13
14 always @(posedge clk or negedge rst_n) begin
15     if (!rst_n) begin d0<=0; d1<=0; end else begin d0<=din; d1<=d0; end
16 end
17
18 always @(posedge clk or negedge rst_n) begin
19     if (!rst_n) begin cnt<=0; stable<=0; end
20     else if (d1 != stable) begin
21         if (cnt==STABLE_TICKS) begin stable<=d1; cnt<=0; end
22         else cnt<=cnt+1;
23     end else cnt<=0;
24 end
25
26 always @(posedge clk or negedge rst_n) begin
27     if (!rst_n) begin stable_q<=0; pulse<=0; end
28     else begin pulse <= (~stable_q) & stable; stable_q <= stable; end
29 end
30 endmodule
```

This module handles debounce in order to prevent multiple peaks and troughs generated throughout the button press. Additionally, the pulse effect is created so the cycle button has to be released and pressed again to execute the cycle process again.

## Load FSM Implementation

```
1  module load_fsm(  
2      input wire clk,  
3      input wire rst_n,  
4      input wire load_pulse,  
5      output reg [1:0] slot,  
6      output wire [3:0] slot_onehot,  
7      output reg wr_res, wr_r, wr_g, wr_b  
8  );  
9  
10     assign slot_onehot = 4'b0001 << slot;  
11  
12     always @(posedge clk or negedge rst_n) begin  
13         if (!rst_n) slot <= 2'd0;  
14         else if (load_pulse) slot <= slot + 2'd1;  
15     end  
16  
17     always @* begin  
18         wr_res = 0; wr_r = 0; wr_g = 0; wr_b = 0;  
19         case (slot)  
20             2'd0: wr_res = load_pulse;  
21             2'd1: wr_r = load_pulse;  
22             2'd2: wr_g = load_pulse;  
23             2'd3: wr_b = load_pulse;  
24         endcase  
25     end  
26 endmodule
```

This module handles the current state the circuit is in. There are four states: PWM resolution, Red, Green, and Blue. Depending on the current state of the board, the resolution, red, green, and blue are changed in a single state. When the right button is pressed, the state is cycled.

## PWM Core

```
23 module pwm_core(  
24     input wire clk,  
25     input wire rst_n,  
26     input wire [7:0] period,  
27     input wire [7:0] duty_r, duty_g, duty_b,  
28     output reg pwm_r, pwm_g, pwm_b  
29 );  
30  
31     wire [8:0] eff_period = {1'b0, period} + 9'd1;  
32  
33     function [8:0] clamp9(input [7:0] d);  
34         clamp9 = ( {1'b0,d} >= eff_period ) ? (eff_period - 9'd1) : {1'b0,d};  
35     endfunction  
36  
37     reg [8:0] cnt;  
38  
39     always @(posedge clk or negedge rst_n) begin  
40         if (!rst_n) cnt <= 0;  
41         else if (cnt == eff_period - 1) cnt <= 0;  
42         else cnt <= cnt + 1;  
43     end  
44  
45     always @(posedge clk or negedge rst_n) begin  
46         if (!rst_n) {pwm_r, pwm_g, pwm_b} <= 0;  
47         else begin  
48             pwm_r <= (cnt < clamp9(duty_r));  
49             pwm_g <= (cnt < clamp9(duty_g));  
50             pwm_b <= (cnt < clamp9(duty_b));  
51         end  
52     end  
53 endmodule  
54
```

PWM period is decided by PWM resolution. The higher the period input, the higher the period is. To control the impact the R, G, and B have on the LED, a duty is applied to each color, where the counter counts through the whole period and duty splits the period to produce the impact each color has on the LED.

## RGB LED Driver

```
1 module rgb_led_driver #(parameter ACTIVE_LOW=1) (  
2     input wire pwm_r, pwm_g, pwm_b,  
3     output wire led_r, led_g, led_b  
4 );  
5     generate  
6         if (ACTIVE_LOW) begin  
7             assign led_r = ~pwm_r;  
8             assign led_g = ~pwm_g;  
9             assign led_b = ~pwm_b;  
10        end else begin  
11            assign led_r = pwm_r;  
12            assign led_g = pwm_g;  
13            assign led_b = pwm_b;  
14        end  
15    endgenerate  
16 endmodule
```

Because the LED's are active low, the pwm signals need to be reversed to properly activate the RGB LED's.

## High Level Implementation

```

1 module top_lab8(
2     input wire clk100mhz,
3     input wire btnc_n,
4     input wire btnr,
5     input wire [7:0] sw,
6     output wire [3:0] led,
7     output wire rgb_r, rgb_g, rgb_b
8 );
9
10     wire rst_n = ~btnc_n;
11     wire clk_lk, clk_pwm;
12
13     clock_divider_fixed
14     u_div(.clk_in(clk100mhz), .rst_n(rst_n), .clk_lk(clk_lk), .clk_pwm(clk_pwm));
15     wire load_pulse;
16     debounce_onepulse #(.STABLE_TICKS(20))
17     u_db(.clk(clk_lk), .rst_n(rst_n), .din(btnr), .pulse(load_pulse));
18     wire [1:0] slot;
19     wire [3:0] slot_oh;
20     wire wr_res, wr_r, wr_g, wr_b;
21     load_fsm u_fsm(
22         .clk(clk_lk), .rst_n(rst_n), .load_pulse(load_pulse),
23         .slot(slot), .slot_onehot(slot_oh),
24         .wr_res(wr_res), .wr_r(wr_r), .wr_g(wr_g), .wr_b(wr_b)
25     );
26     assign led = slot_oh;
27
28     reg [7:0] reg_res, reg_r, reg_g, reg_b;
29     always @(posedge clk_lk or negedge rst_n) begin
30         if (!rst_n) begin reg_res<=8'd63; reg_r<=0; reg_g<=0; reg_b<=0; end

```

```


31     else begin
32         if (wr_res) reg_res <= sw;
33         if (wr_r) reg_r <= sw;
34         if (wr_g) reg_g <= sw;
35         if (wr_b) reg_b <= sw;
36     end
37 end
38
39 reg [7:0] res_q1,res_q2,r_q1,r_q2,g_q1,g_q2,b_q1,b_q2;
40 always @(posedge clk_pwm or negedge rst_n) begin
41     if (!rst_n) begin res_q1<=0; res_q2<=0; r_q1<=0; r_q2<=0; g_q1<=0;
42     g_q2<=0; b_q1<=0; b_q2<=0; end
43     else begin
44         res_q1<=reg_res; res_q2<=res_q1;
45         r_q1<=reg_r; r_q2<=r_q1; g_q1<=reg_g; g_q2<=g_q1; b_q1<=reg_b;
46         b_q2<=b_q1;
47     end
48 end
49
50 wire pwm_r, pwm_g, pwm_b;
51 pwm_core u_pwm(.clk(clk_pwm), .rst_n(rst_n),
52     .period(res_q2), .duty_r(r_q2), .duty_g(g_q2), .duty_b(b_q2),
53     .pwm_r(pwm_r), .pwm_g(pwm_g), .pwm_b(pwm_b));
54
55 rgb_led_driver #(.ACTIVE_LOW(1)) u_led(
56     .pwm_r(pwm_r), .pwm_g(pwm_g), .pwm_b(pwm_b),
57     .led_r(rgb_r), .led_g(rgb_g), .led_b(rgb_b));
58 endmodule

```

High level implementation connects all modules together to control the RGB LED. The center button resets the LED and controls. The right button toggles board states to select, R, G, B, or PWM resolution. When the right button is pressed, the element of whatever mode the board is on is set and the RGB LED reacts accordingly.

## Simulation Waveform

### Debounce Pulse

 

The screenshot shows the reset button being pressed, giving all output fields valid values. When the button is held for long enough, it is shown that a pulse is generated around 250ns into the simulation.




## Load FSM



The screenshot again shows the reset button being pressed, giving all output fields valid values. Every time load\_pulse is positive edge triggered (right button is pressed), the board cycles through the states of wr\_res, wr\_r, wr\_g, and wr\_b.

## RGB LED Driver

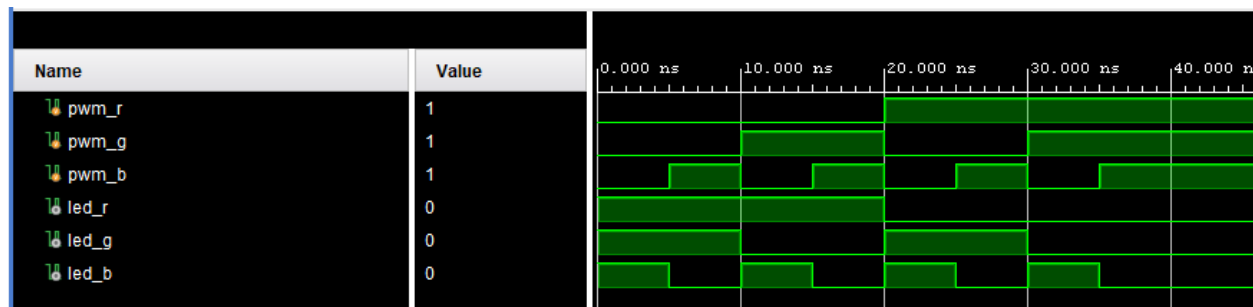


Because the LED's are active low, we need the input signals to be low to turn the LED on. For example, when RGB = 000, the LED is white (all segments of LED are on). When RGB = 111, however, the LED is off (all segments of LED are off).

# Implementation

## Utilization Table:

### Summary

Resource	Utilization	Available	Utilization %
LUT	116	63400	0.18
FF	152	126800	0.12
IO	18	210	8.57

 

## Timing Summary:

### Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 6.563 ns	Worst Hold Slack (WHS): 0.140 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 32	Total Number of Endpoints: 32	Total Number of Endpoints: 33

All user specified timing constraints are met.

# Contribution

Michelle Lau (50%) - Debugging, implementation and board demo

Edwin Estrada (50%) - Programming, debugging, and test benching