

California Polytechnic State University Pomona

DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING

Digital Circuit Design Verilog

ECE 3300L

Report #6

Prepared by

Heba Hafez 017353323

Sean Wygant 017376658

Group Y

Mohamed Aly

July 28, 2025

Objective: Design two BCD counters, one for the one's place, and one for the tens place, to count up and down based on the switch input. Connect the counters to an ALU to complete addition and subtraction. Results will display on a three-digit 7-segment display, with raw binary output displayed on the LEDs.

Code and Explanation:

Clock_divider.v:

```

23 module clock_divider(
24     input clk,
25     input rst,
26     input [4:0] speed_sel,
27     output clk_out
28 );
29     reg [31:0] count = 32'b0;
30
31     always @(posedge clk) begin
32         if (rst)
33             count <= 32'd0;
34         else
35             count <= count + 1;
36     end
37
38     assign clk_out = count[speed_sel]; // Output bit-slice as divided clock
39 endmodule

```

A clock is divided based on the inputted frequency working off a 32 bit counter that increments every clock cycle and resets (rst). Clk_out outputs a specific bit from the counter. The higher the bit, the slower the cycle.


Clock_divider Tb:

```

23 module clock_divider_tb();
24     reg clk;
25     reg rst;
26     reg [4:0] speed_sel;
27     wire clk_out;
28
29     clock_divider uut (
30         .clk(clk),
31         .rst(rst),
32         .speed_sel(speed_sel),
33         .clk_out(clk_out)
34     );
35
36     initial begin
37         clk = 0;
38         forever #5 clk = ~clk;
39     end
40
41     initial begin
42         rst = 1;
43         speed_sel = 5'd2;
44         #20;
45         rst = 0;
46         #500;
47         speed_sel = 5'd4;
48         #500;
49         speed_sel = 5'd6;
50         #500;
51
52         $finish;
53     end
54
55     initial begin
56         $monitor("Time = %0t , clk = %b , rst = %b , speed_sel = %d , clk_out = %b",
57             $time, clk, rst, speed_sel, clk_out);
58     end

```

 The Tesbench ensures different clock speeds are running by generating a toggling clock, then applying a rest and changing the speeds.



Time resolution is 1 ps
Time = 0 , ctrl_in = 0000 , ctrl_out = 0000
Time = 10000 , ctrl_in = 0001 , ctrl_out = 0001
Time = 20000 , ctrl_in = 0010 , ctrl_out = 0010
Time = 30000 , ctrl_in = 0011 , ctrl_out = 0011
Time = 40000 , ctrl_in = 0100 , ctrl_out = 0100
Time = 50000 , ctrl_in = 0101 , ctrl_out = 0101
Time = 60000 , ctrl_in = 0110 , ctrl_out = 0110
Time = 70000 , ctrl_in = 0111 , ctrl_out = 0111
Time = 80000 , ctrl_in = 1000 , ctrl_out = 1000
Time = 90000 , ctrl_in = 1001 , ctrl_out = 1001
\$finish called at time : 100 ns : File "C:/Users/Sean/Documents/Summer 25 CPP/ECE3300L/Lab 6 - 1/Lab 6 - 1.srcs/sim_1/new/control_decoder_tb.v" Line 59

BCD_counter.v:

```

23 module bcd_counter(
24     input clk,
25     input btn0,
26     input dir,
27     output reg [3:0] digit,
28     output reg rollover
29 );
30     always @(posedge clk or posedge btn0) begin
31         if (btn0) begin
32             digit <= 4'd0;
33             rollover <= 0;
34         end else begin
35             if (!dir) begin // up
36                 if (digit == 9) begin
37                     digit <= 0;
38                     rollover <= 1;
39                 end else begin
40                     digit <= digit + 1;
41                     rollover <= 0;
42                 end
43             end
44             else begin // down
45                 if (digit == 0) begin
46                     digit <= 9;
47                     rollover <= 1;
48                 end
49                 else begin
50                     digit <= digit - 1;
51                     rollover <= 0;
52                 end
53             end
54         end
55     end
56 endmodule

```

Based on the dir signal, the positive edge btn0 and clk resets if btn0 is high and if dir=0 it counts up . It increments to 9 then rolls over. If dir=1, it decrements and wraps around 9 with rollover=1.


BCD_Counter_Tb:

```

17 module bcd_counter_tb();
18
19 reg clk;
20 reg btn0;
21 reg dir;
22 wire [3:0] digit;
23 wire rollover;
24
25 bcd_counter uut (
26   .clk(clk),
27   .btn0(btn0),
28   .dir(dir),
29   .digit(digit),
30   .rollover(rollover)
31 );
32
33 initial begin
34   clk = 0;
35   forever #5 clk = ~clk;
36 end
37 initial begin
38   $display("Time\tclk\tbtn0\tldir\tldigit\tlrollover");
39   $monitor("%0t\t%b\t%b\t%b\t%d\t%b",
40     $time, clk, btn0, dir, digit, rollover);
41 end
42
43 initial begin
44   btn0 = 1;
45   dir = 0;
46
47   #20;
48   btn0 = 0;
49
50   repeat (10) @(posedge clk);
51
52   @(posedge clk);
53   dir = 1;
54
55   repeat (1) @(posedge clk);
56   repeat (9) @(posedge clk);
57   btn0 = 1;
58   @(posedge clk);
59   btn0 = 0;
60
61   repeat (3) @(posedge clk);
62   dir = 1; @(posedge clk);
63   dir = 0; @(posedge clk);
64   $finish;
65 end
66 endmodule

```

 A 10ns clock period is created to mimic counting up 0 to 9 and then 9 to 0. There is an initial reset with btn0 then resets again at 3.



```

Time resolution is 1 ps
Time   clk btn0   dir digit   rollover
0      0      1   0   0   0
5000   1   1   0   0   0
10000  0   1   0   0   0
15000  1   1   0   0   0
20000  0   0   0   0   0
25000  1   0   0   1   0
30000  0   0   0   1   0
35000  1   0   0   2   0
40000  0   0   0   2   0
45000  1   0   0   3   0
50000  0   0   0   3   0
55000  1   0   0   4   0
60000  0   0   0   4   0
65000  1   0   0   5   0
70000  0   0   0   5   0
75000  1   0   0   6   0
80000  0   0   0   6   0
85000  1   0   0   7   0
90000  0   0   0   7   0
95000  1   0   0   8   0
100000 0   0   0   8   0
105000 1   0   0   9   0
110000 0   0   0   9   0
115000 1   0   0   0   1
120000 0   0   0   0   1
125000 1   0   1   9   1
130000 0   0   1   9   1
135000 1   0   1   8   0
140000 0   0   1   8   0
145000 1   0   1   7   0
150000 0   0   1   7   0
155000 1   0   1   6   0
160000 0   0   1   6   0
165000 1   0   1   5   0
170000 0   0   1   5   0
175000 1   0   1   4   0
180000 0   0   1   4   0
185000 1   0   1   3   0
190000 0   0   1   3   0

```

Alu.v:

```

23 | module alu(
24 |     input [1:0] control,
25 |     input [3:0] a,
26 |     input [3:0] b,
27 |     output reg [7:0] result
28 | );
29 |     reg [4:0] math;
30 |     integer i;
31 |
32 |
33 |     always@(*) begin
34 |         if (control == 0) begin
35 |             math = a + b;
36 |         end
37 |         else if (control == 1) begin
38 |             math = a - b;
39 |         end
40 |         else begin
41 |             math = 0;
42 |         end
43 |         result[7:5] = 0;
44 |         result[4] = math / 4'd10;
45 |         result[3:0] = math % 4'd10;
46 |     end
47 | endmodule

```

The Alu performs the addition and subtraction based on the 2 bit control. It takes in two 4bit numbers for a and b to add or subtract, then stores the answer in math. The result is 8 bits and outputs the 2-bit encoding for the BCD.

Alu_Tb:

```

23 module alu_tb();
24     reg [1:0] control;
25     reg [3:0] a;
26     reg [3:0] b;
27     wire [7:0] result;
28
29     alu uut (
30         .control(control),
31         .a(a),
32         .b(b),
33         .result(result)
34     );
35
36     initial begin
37         $display("Time\tControl\tA\tB\tResult\tDecimal Value");
38         $monitor("%0t\t%b\t%d\t%d\t%08b\t%d",
39             $time, control, a, b, result, (result[4]*10 + result[3:0]));
40     end
41
42     initial begin
43         control = 2'b00; //add
44         a = 4'd3; b = 4'd6; // 3 + 6 = 9
45         #10;
46         a = 4'd7; b = 4'd8; // 7 + 8 = 15
47         #10;
48         a = 4'd9; b = 4'd7; // 9 + 7 = 16
49         #10;
50
51
52         // subtract
53         control = 2'b01;
54
55         a = 4'd9; b = 4'd3; // 9 - 3 = 6
56         #10;
57         a = 4'd12; b = 4'd7; // 12 - 7 = 5
58         #10;
59
60         a = 4'd3; b = 4'd8; // 3 - 8 = -5 wraps
61         #10;
62         a = 4'd0; b = 4'd0; //0
63         #10;
64
65         control = 2'b10; a = 4'd5;
66         b = 4'd5;
67         #10;
68         control = 2'b11;
69         a = 4'd9;
70         b = 4'd2;
71         #10; // result = 0
72
73         $finish;
74     end
75 endmodule
76

```

The test bench runs through different addition and subtraction combinations to ensure the proper answers are being outputted.

```

Time resolution is 1 ps
Time    Control A  B  Result  Decimal Value
0 00    3    6  00001001      9
10000  00    7    8  00010101     15
20000  00    9    7  00010110     16
30000  00    1    1  00000010      2
40000  01    9    3  00000110      6
50000  01    9    0  00001001      9
60000  01    0    2  00010000     10
70000  01    0    0  00000000      0
80000  10    5    5  00000000      0
90000  11    9    2  00000000      0
$finish called at time : 100 ns : File "C:/Users/Sean/Documents/Summer 25 CPP/ECE3300L/Lab 6 - 1/Lab 6 - 1.srcs/sim_1/new/alu_tb.v" Line 75

```

Control_decoder.v:

```

23 module control_decoder(
24     input [3:0] ctrl_in,
25     output reg [3:0] ctrl_out
26 );
27     always @(*) begin
28         ctrl_out = ctrl_in;
29     end
30 endmodule
31

```

This directly copies the 4-bit input to the output to demonstrate the switch inputs.

Control_decoder.v:

```

23 module control_decoder_tb(
24 );
25     reg [3:0] ctrl_in;
26     wire [3:0] ctrl_out;
27
28     control_decoder uut (
29         .ctrl_in(ctrl_in),
30         .ctrl_out(ctrl_out)
31     );
32
33     initial begin
34         $monitor("Time = %0t , ctrl_in = %b , ctrl_out = %b", $time, ctrl_in, ctrl_out);
35     end
36
37     // Stimulus
38     initial begin
39         ctrl_in = 4'b0000;
40         #10;
41         ctrl_in = 4'b0001;
42         #10;
43         ctrl_in = 4'b0010;
44         #10;
45         ctrl_in = 4'b0011;
46         #10;
47         ctrl_in = 4'b0100;
48         #10;
49         ctrl_in = 4'b0101;
50         #10;
51         ctrl_in = 4'b0110;
52         #10;
53         ctrl_in = 4'b0111;
54         #10;
55         ctrl_in = 4'b1000;
56         #10;
57         ctrl_in = 4'b1001;
58         #10;
59         $finish;
60     end

```

4-bit binary sequences are used to confirm that the output is proper and the same as the input.

Seg7_Scan.v:

```

module seg7_scan(
    input clk,
    input rst,
    input [3:0] control,
    input [7:0] bits,
    output reg [6:0] SEG,
    output [7:0] AN
);
    reg [19:0] tmp;
    reg [3:0] digit;

    always@(digit)
        case(digit)
            4'd0:SEG=7'b0000001; 4'd1:SEG=7'b1001111; 4'd2:SEG=7'b0010010;
            4'd3:SEG=7'b0000110; 4'd4:SEG=7'b1001100; 4'd5:SEG=7'b0100100;
            4'd6:SEG=7'b0100000; 4'd7:SEG=7'b0001111; 4'd8:SEG=7'b0000000;
            4'd9:SEG=7'b0001100; 4'd10:SEG=7'b0001000; 4'd11:SEG=7'b1100000;
            4'd12:SEG=7'b0110001; 4'd13:SEG=7'b1000010; 4'd14:SEG=7'b0110000;
            4'd15:SEG=7'b0111000; default:SEG=7'b1111111;
        endcase

    always@(posedge clk) begin
        if(rst)
            tmp<=0;
        else
            tmp<=tmp+1;
        end

    wire [1:0] s = tmp[19:18];

    always@(s, bits, control)
        case (s)
            2'd0:digit=bits[3:0]; 2'd1:digit=bits[7:4];
            2'd2:digit=control[3:0]; default:digit=4'b0000;
        endcase

    reg [7:0] AN_tmp;

```

The scan has all the case statements for the 7 segment displays to properly light all numbers. Based on the edge of the run the tmp would be set to 0 or increment to determine whether to apply case s or not.

Seg7 Scan Tb:

```

module seg7_scan_tb();
    reg clk;
    reg rst;
    reg [3:0] control;
    reg [7:0] bits;
    wire [6:0] SEG;
    wire [7:0] AN;

    // Instantiate seg7_scan
    seg7_scan uut (.clk(clk), .rst(rst), .control(control), .bits(bits), .SEG(SEG), .AN(AN));

    //Clock
    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end


    // Display header
    initial begin
        $display("Time\tclk\trst\tcontrol\tbits\tSEG\tAN");
        $monitor("%0t\t%b\t%b\t%h\t%h\t%b\t%b", $time, clk, rst, control, bits, SEG, AN);
    end

    initial begin
        // Initialize inputs
        rst = 1;
        control = 4'hF;
        bits = 8'h21;

        // Test reset
        #20 rst = 0;
        #500;

        // Try new input
        bits = 8'hA5;
        control = 4'h3;
        #500;
    end

```

 Time resolution is 1 ps

Time	clk	rst	control	bits	SEG	AN
0	0	1	f	21	0000001	xxxxxxx
5000	1	1	f	21	1001111	11111110
10000	0	1	f	21	1001111	11111110
15000	1	1	f	21	1001111	11111110
20000	0	0	f	21	1001111	11111110
25000	1	0	f	21	1001111	11111110
30000	0	0	f	21	1001111	11111110
35000	1	0	f	21	1001111	11111110
40000	0	0	f	21	1001111	11111110
45000	1	0	f	21	1001111	11111110
50000	0	0	f	21	1001111	11111110
55000	1	0	f	21	1001111	11111110
60000	0	0	f	21	1001111	11111110
65000	1	0	f	21	1001111	11111110
70000	0	0	f	21	1001111	11111110
75000	1	0	f	21	1001111	11111110
80000	0	0	f	21	1001111	11111110
85000	1	0	f	21	1001111	11111110
90000	0	0	f	21	1001111	11111110
95000	1	0	f	21	1001111	11111110
100000	0	0	f	21	1001111	11111110
105000	1	0	f	21	1001111	11111110
110000	0	0	f	21	1001111	11111110
115000	1	0	f	21	1001111	11111110
120000	0	0	f	21	1001111	11111110
125000	1	0	f	21	1001111	11111110
130000	0	0	f	21	1001111	11111110
135000	1	0	f	21	1001111	11111110

Top_lab6:

```
module top_lab6(
    input [8:0] SW,
    input clk,
    input btn0,
    output [6:0] SEG,
    output [7:0] LED,
    output [7:0] AN
);

    wire clk_div;
    wire [3:0] ones_digit, tens_digit, ctrl_nibble;
    wire rollover_ones, rollover_tens;
    wire [7:0] result;

    //instantiates clock_divder which contains both the clock divison and mux
    clock_divider clock(.clk(clk), .rst(btn0), .speed_sel(SW[4:0]), .clk_out(clk_div));

    //instatiates bcd_counter which are single digit binary coded decimal counters for each digit
    bcd_counter ones_counter(.clk(clk_div), .btn0(btn0), .dir(SW[7]), .digit(ones_digit), .rollover(rollover_ones));
    bcd_counter tens_counter(.clk(clk_div), .btn0(btn0), .dir(SW[8]), .digit(tens_digit), .rollover(rollover_tens));

    //instantiates the arithmetic logic unit which handles addition and subtraction
    //control as well as result mapping and underflow (0 to 18)
    alu alu_unit(.a(tens_digit), .b(ones_digit), .control(SW[6:5]), .result(result));

    //instantiates control_decoder to display the control settings on the left most 7-segment display
    control_decoder ctrl_dec(.ctrl_in({SW[8], SW[7], SW[6], SW[5]}), .ctrl_out(ctrl_nibble));

    //instantiates seq7_scan display the result of the ALU operation on the 7-segment displays
    seq7_scan scan_inst(.clk(clk), .rst(btn0), .bits(result), .control(ctrl_nibble), .SEG(SEG), .AN(AN));

    //binds the value of the LEDs to each value imported to the ALU for debugging
    assign LED = {tens_digit[3:0], ones_digit[3:0]};

endmodule
```

The top lab as always wraps together all of our files to integrate them together.

Top_lab6_tb:

```
// Clock 100MHz
initial begin
    clk = 0;
    forever #5 clk = ~clk;
end

// Monitoring
initial begin
    $display("Time\tclk\tbtn0\tSW[8:0]\t\tLED\t\tSEG\t\tAN");
    $monitor("%0t\t%b\t%b\t%b\t%b\t%b\t%b\t%b", $time, clk, btn0, SW, LED, SEG, AN);
end

initial begin
    // Initial values
    btn0 = 1;           // Reset
    SW = 9'b00000000;   // All inputs zero

    #20 btn0 = 0;       // Reset off

    // Set a speed select
    SW[4:0] = 5'b00001; // Slowest speed


    // Count up on both counters
    SW[7] = 0; // dir for ones_counter = up
    SW[8] = 0; // dir for tens_counter = up

    // ALU mode
    SW[6:5] = 2'b00;

    // Counters increment
    repeat (50) @(posedge clk);


    // Change direction for ones_counter
    SW[7] = 1;
    repeat (20) @(posedge clk);
```

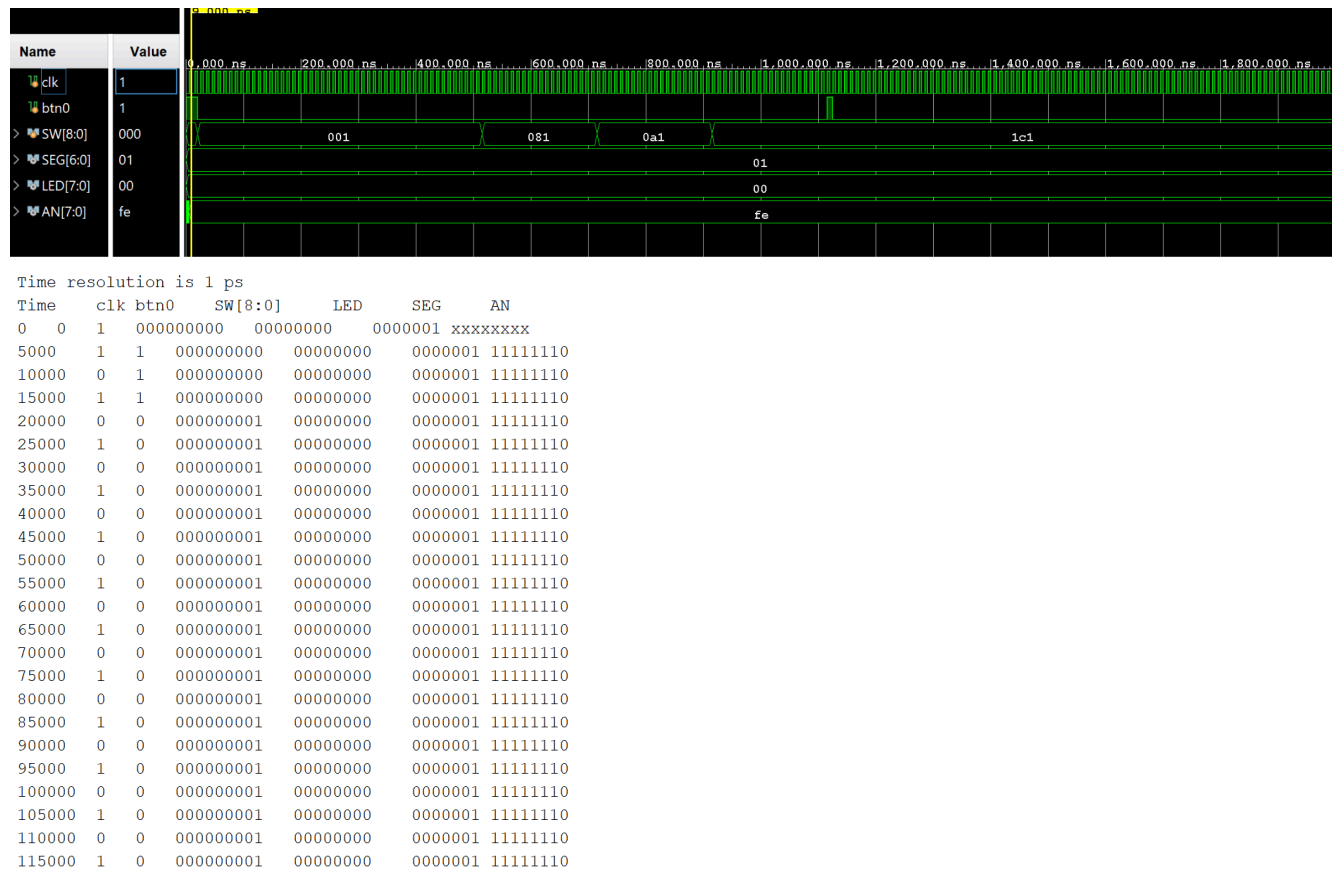This test bench was designed to test the function of the main inputs and outputs of the build. The top level module is initialized then some test settings are input along with a clock. These settings allow us to see what the total output of the program will look like based on the input. This simple test is supplemented by the other test benches we built for each module.



Vivado (LUTs, FFs, Power):

Resource	Utilization	Available	Utilization %
LUT	37	63400	0.06
FF	60	126800	0.05
IO	34	210	16.19

 

1. Slice Logic

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs	36	0	0	63400	0.06
LUT as Logic	36	0	0	63400	0.06
LUT as Memory	0	0	0	19000	0.00
Slice Registers	60	0	0	126800	0.05
Register as Flip Flop	60	0	0	126800	0.05
Register as Latch	0	0	0	126800	0.00
F7 Muxes	4	0	0	31700	0.01
F8 Muxes	0	0	0	15850	0.00

* Warning! LUT value is adjusted to account for LUT combining.

2. Slice Logic Distribution


Site Type	Used	Fixed	Prohibited	Available	Util%
Slice	25	0	0	15850	0.16
SLICEL	17	0			
SLICEM	8	0			
LUT as Logic	36	0	0	63400	0.06
using O5 output only	0				
using O6 output only	24				
using O5 and O6	12				
LUT as Memory	0	0	0	19000	0.00
LUT as Distributed RAM	0	0			
using O5 output only	0				
using O6 output only	0				
using O5 and O6	0				
LUT as Shift Register	0	0			
using O5 output only	0				
using O6 output only	0				
using O5 and O6	0				
Slice Registers	60	0	0	126800	0.05
Register driven from within the Slice	60				
Register driven from outside the Slice	0				
Unique Control Sets	2		0	15850	0.01

* * Note: Available Control Sets calculated as Slice * 1, Review the Control Sets Report for more information regarding control sets.

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.131 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 25.6°C
 Thermal Margin: 59.4°C (12.9 W)
 Ambient Temperature: 25.0 °C
 Effective θ_{JA} : 4.6°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

1. Summary

+-----+		
Total On-Chip Power (W)	0.131	
Design Power Budget (W)	Unspecified*	
Power Budget Margin (W)	NA	
Dynamic (W)	0.034	
Device Static (W)	0.097	
Effective TJA (C/W)	4.6	
Max Ambient (C)	84.4	
Junction Temperature (C)	25.6	
Confidence Level	Low	
Setting File	---	
Simulation Activity File	---	
Design Nets Matched	NA	
+-----+		

* Specify Design Power Budget using, `set_operating_conditions -design_power_budget <value in Watts>`

1.1 On-Chip Components

+-----+				
On-Chip	Power (W)	Used	Available	Utilization (%)
+-----+				
Clocks	<0.001	3	---	---
Slice Logic	<0.001	132	---	---
LUT as Logic	<0.001	36	63400	0.06
Register	<0.001	60	126800	0.05
CARRY4	<0.001	13	15850	0.08
F7/F8 Muxes	<0.001	4	63400	<0.01
Others	0.000	7	---	---
Signals	<0.001	115	---	---
I/O	0.032	34	210	16.19
Static Power	0.097			
Total	0.131			
+-----+				

Video Link:

https://youtu.be/D2C_ej10In0?si=xFRM62qPlkh71soX

Reflections:

The ALU proved to be a struggle, especially when it came to the display. Converting the addition and subtraction into two separate displays became an issue, specifically at the number 18. At 18 we needed it to correctly display on the BCD and wrap around. The division and modulo had to break the numbers down carefully in order to properly display. Since we worked on the counter and divider last week, it was easier to build this week, along with the test benches for them. As the semester continues, the testbenches are progressively becoming easier to write as we sometimes struggle with them.

Partner Contributions:

Heba initially started the code, then Sean looked at her code and edited it to get the proper displays. The test benches were evenly split, each working back and forth with each other to get the right outputs on the FPGA and simulation. The lab report was collaboratively worked on, with each person working on different sections. The work was 50/50.